

tone-burst generator

A (repetitive) tone-burst signal is an extremely useful aid for testing audio equipment. Basically, this type of test signal is obtained by switching the output of a sine-wave oscillator on and off at regular intervals. The generator described in this article utilises a novel design approach that simplifies the circuit considerably and only involves one minor reduction of the capabilities.

The sinewave is the most commonly used test signal. It is simple to analyse (both 'on sight' and mathematically) so that any distortion can usually be recognised quickly. Its very simplicity, however, is also its main disadvantage: it has very little in common with the signals that an audio system is normally expected to handle: music and speech. Audio signals are extremely 'dynamic': transients and other more-or-less rapid changes in level are actually the most important information in a speech signal. In order to test a system which is intended to handle this type of material, it seems reasonable to look for a 'dynamic' test signal. There is no way to measure 'transient response' with a signal that is as obstinately steady-state as DC. And that, regrettably, applies to sinewaves.


What about squarewaves? A good second in the list of commonly used test signals. It is definitely better than the sinewave when it comes to pointing out poor transient response. However, it is definitely inferior on several other counts. Just think: a digital NAND gate will pass a squarewave beautifully — but a NAND gate makes a very poor audio amplifier indeed . . .

A tone-burst signal can be considered as a combination of sinewave plus squarewave. It has the advantages of both: it is steady-state for a while, then suddenly changes to a new 'steady state' and so on. A typical tone-burst signal is shown


in figure 1. It consists of one or more sinewaves, then a gap (one or more sinewaves in length), then again one or more sinewaves and so on. That it is in some ways similar to a sinewave is obvious; the similarity with a squarewave is perhaps less apparent, until one realises that it is basically equivalent to the output from a sinewave generator that is being turned on and off by a squarewave generator of lower frequency.

All very well, but how does one obtain a 'tone-burst' signal? Apparently, a squarewave generator must 'gate' the output from a sinewave generator. One way of achieving this is shown in figure 2. The sinewave is fed to an electronic switch. As the switch is opened and closed, a succession of sinewave 'bursts' will appear at the output. Control of the switch is rather complicated (more than this simplified block diagram suggests!). The sinewave is fed to a zero-crossing detector; the output from the latter is used as 'clock' signal for two programmable counters. Only one of the counters is 'active' at any given moment — the other is held in the 'reset' position by a flip-flop. When the selected maximum count of the 'active' counter is reached, the flip-flop is triggered. The first counter is then reset and the other counter is enabled. Since the output of the flip-flop also drives the electronic switch, the final result is a number of sinewave periods determined by one counter, followed by a 'de-

1

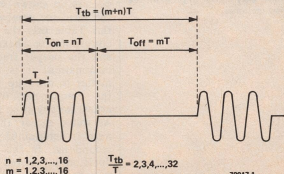


2

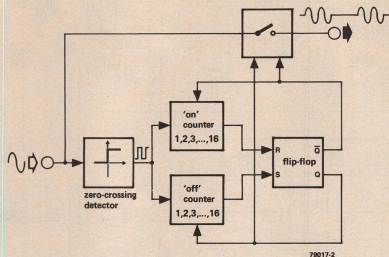

79017-2

3

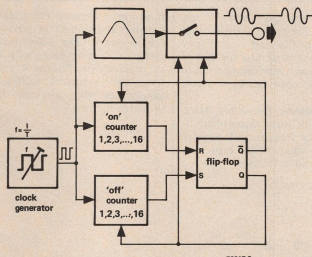

79017-3

'one' (no output) determined by the second counter.

A fool-proof system, one would think. However, there is at least one weak link in the chain: the zero-crossing detector. If the output tone-bursts are to start and stop in the zero-crossings of the sine wave, an accurate zero-crossing detector is required - not to mention zero phase-shift throughout the complete chain from detector through counters and flip-flop to switch.

These problems can be solved - witness the proliferation of commercial tone-burst generators that work according to this principle. However, why bother? A different approach obviates the whole problem. The results are certainly good enough for the home constructor - for

Figure 1. A tone-burst is basically equivalent to a sine wave that is switched on and off at regular intervals. Both the length of the burst and the period between bursts are a whole multiple of the sine wave period.

Figure 2. Block diagram of a conventional tone-burst generator.

Figure 3. Block diagram of a novel alternative.

that matter, they are good enough for professional use. The only problem is that they make for less sweeping advertisements ...

Why not?

The block diagram of a different approach is shown in figure 3. At first sight, it is very similar to the diagram shown in figure 2. However, there is one major difference: the clock pulses for the counters are not derived from the sine wave. The reverse is true: a selective filter is used to derive the output sine wave from the clock pulses. And it is easier to design - and, more importantly, build - a good selective filter than it is to obtain a good zero-crossing detector.



Any experienced designer who is conversant with the law of cussedness should, by now, be looking for the 'bug'. It's there all right. If the tone-burst is to be turned on and off at the correct moment - during the zero-crossings - the edges of the clock pulses must still correspond with those zero-crossings. Clock pulses and sine wave must be in phase. This implies that the centre frequency of the filter must coincide with the clock frequency, and a fixed centre frequency therefore leads to a fixed clock frequency. Tone-bursts with 'swept' sine wave frequency are no longer possible. So what ... who needs 'em, anyway?

The circuit

The complete circuit of the tone-burst generator is shown in figure 4. The burst length can be set, by means of S1, at anything between 1 and 16 complete sine wave periods. The interval between bursts is selected in the same way by S2. The clock generator, N1/N2, is a fairly standard circuit. Its output is not particularly 'clean', but suitable processing by the other four inverters in the same package (N3 ... N6) produces a good square wave. As illustrated in the block diagram (figure 3), this signal is fed to two counters, one of which (IC1/IC2) determines the length of the burst while the other (IC3/IC4) fixes the interval between bursts. One output of each counter is selected by S1 and S2, respectively, and used to set and reset the flip-flop (N9/N10). The Q and Q-bar outputs of the flip-flop are fed back to the counters in such a way that when the count selected by S1 is reached, toggling the flip-flop, the corresponding counter is reset and the other is enabled. In this way, the two counters are used alternately.

The flip-flop outputs are also used to operate the electronic switches S1 ... S4. When S1 and S2 are closed, the sine wave appears at the output; opening S1 and S2 and closing S3 and S4 blocks the sine wave and passes a DC level, corresponding to the zero level of the sine wave, instead.

5

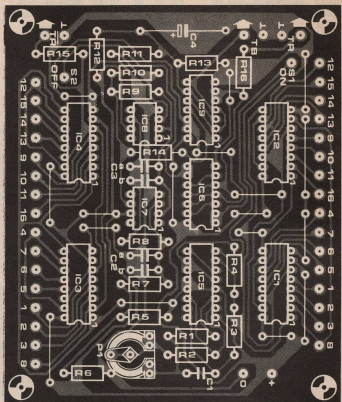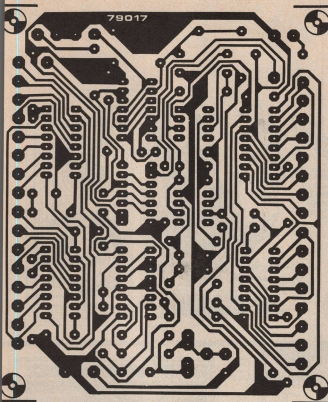

Parts list

Resistors:

R1 = 39 k
 R2, R6* = 8k2
 R3, R8 . . . R14 = 10 k
 R4 = 1 M
 R5 = 22 k
 R7 = 470 k
 R15, R16 = 27 k
 R17* = 100 k
 P1 = 10 k preset

Capacitors:

C1* = 33 n
 C2a/b*, C3a/b* = 15 n + 1 n
 C4 = 22 μ /16 V
 C5* = 10 μ /25 V

Miscellaneous:

S1, S2 = single pole, 16-way
 switch*

Semiconductors:

IC1 . . . IC4 = CD 4015
 IC5 = CD 4049
 IC6 = CD 4011
 IC7, IC8 = 741
 IC9 = CD 4066

* see text

