

Reducing a PLL's even-order harmonics

by R. P. Leck

Bell Laboratories, Crawford Hill, Holmdel, N. J.

In contrast to the clean output they produce when operated in their fundamental mode, phase-locked loops generate even-order harmonics of the input frequency and excessive sideband noise when used in frequency-divider or frequency-multiplier circuits. The spurious responses may be reduced, however, by adding an extra break or corner frequency to the PLL's low-pass filter response, in order to reduce the modulation index at the input to the loop's voltage-controlled oscillator.

A block diagram of a typical PLL frequency multiplier is shown in (a). Detector A_1 compares the phase of the input signal, f_1 , with the phase of the divided-down VCO signal. Thus A_1 generates a voltage proportional to the phase difference between its inputs. After passing through low-pass filter A_2 , the signal is applied to the VCO, A_3 , so altering its output frequency f_2 that the phase difference between f_2 and f_1 is minimized. The loop is in the so-called locked state when f_1 equals f_2 in frequency and phase.

As a result of placing divider N in the loop to make the PLL operate as a frequency multiplier, the output of the phase detector and thus the loop, which is picked off at A_3 , also contains unwanted harmonics of f_1 . The amount of sideband noise on each carrier signal, which is an indication of the modulation index (a relation too cumbersome to derive for most waveforms), is given by:

$$\theta_0(s) = NK_0F(s)V_d/s$$

where $F(s)$ is the transfer function of the loop's low-pass filter, V_d is A_1 's output voltage, and K_0 is the voltage-to-frequency control constant of A_3 . So, by reducing the numerical value of $F(s)$, $\theta(s)$ and the modulation index fall and harmonics are also reduced.

The transfer function of the active loop filter typically used in PLL circuits (b) is $F_2(s) = (s\tau_2 + 1)/s\tau_1$, where τ_1

$= R_1C$ and $\tau_2 = R_2C$. By adding capacitor C' across R_2 as shown in (c), the second-order filter previously shown is made a third-order network, whose transfer function is given by $F_3(s) = (s\tau + s\tau_3 + 1)/(s^2\tau_1\tau_3 + s\tau_1)$, where $\tau_3 = R_2C'$.

Note the corresponding curves of the filter's open-loop response. If the unwanted harmonics in question are all above the added pole frequency, $1/2\pi\tau_3$, they will be attenuated because the magnitude of $F_3(s)$ will be less than that of $F_2(s)$. At ω_{2f} in (b), there is no additional suppression beyond that which exists as a result of the integrating effects of the VCO and its low-pass filter. The attenuation is increased with the addition of C' as shown in (c).

Adding C' creates a network that, under some conditions, can be unstable. However, as long as the open-loop gain of the originally stable second-order loop is unchanged after C' is added, and the slope at which the loop's log-magnitude plot crosses the unity-gain axis does not exceed -40 decibels per decade, there will be no problem. Both of these conditions are normally found in practice.

Adding the additional break point affects the network's damping factor, δ , and the system bandwidth, B , two of the most important parameters of interest in designing a loop filter. The effects of damping start to become noticeable when τ_3 starts to move down from infinity to $\tau_2/30$. It should be understood that with a reduction in harmonic output also comes a decrease in the range over which the PLL will operate.

As an example of how to design a filter network, consider the case where a PLL multiplier is to be scaled to generate a frequency f_{out} equal to $(108/109)f_{in}$, having a damping factor of 1.2 and a bandwidth of 100 hertz. Thus the VCO is made to multiply f_{in} by 108, and a divider is used to provide $N = 109$. Along with the initial considerations, an additional requirement is to suppress the sidebands at the divider output by 50 dB. This corresponds to a phase jitter of 0.4° .


A standard second-order filter design can meet the damping and bandwidth criteria, but a third-order filter is required to meet the sideband suppression and phase jitter requirements.

It will be realized that it is necessary to reduce the

first-order sidebands at least 10 dB, if the sidebands at the output of the divide-by-109 unit are to be at least 50 dB below the peak output voltage. By using the well-known two-pole RC filter equations (this discussion assumes familiarity with the design procedures of basic PLL filters), and setting δ to 2.2 and B to 100 Hz to get $V_0 = 10$ dB below V_a , it is found that $\tau_1 = 6.7(10^{-2})$ and $\tau_2 = 5.09(10^{-2})$. R_1 , R_2 , and C can then be appropriately selected.

From (d), an experimental curve generated for use in designing the three-pole filter, it is found that an equivalent second-order damping factor of 1.1 is obtained for such a loop when $N = 21.2$ and $\tau_3 = \tau_2/N = 2.5(10^{-3})$. Thus $C' = \tau_3/R_2 = 0.5$ microfarad if $R_2 = 50$ kilohms, a typical value of resistance. □

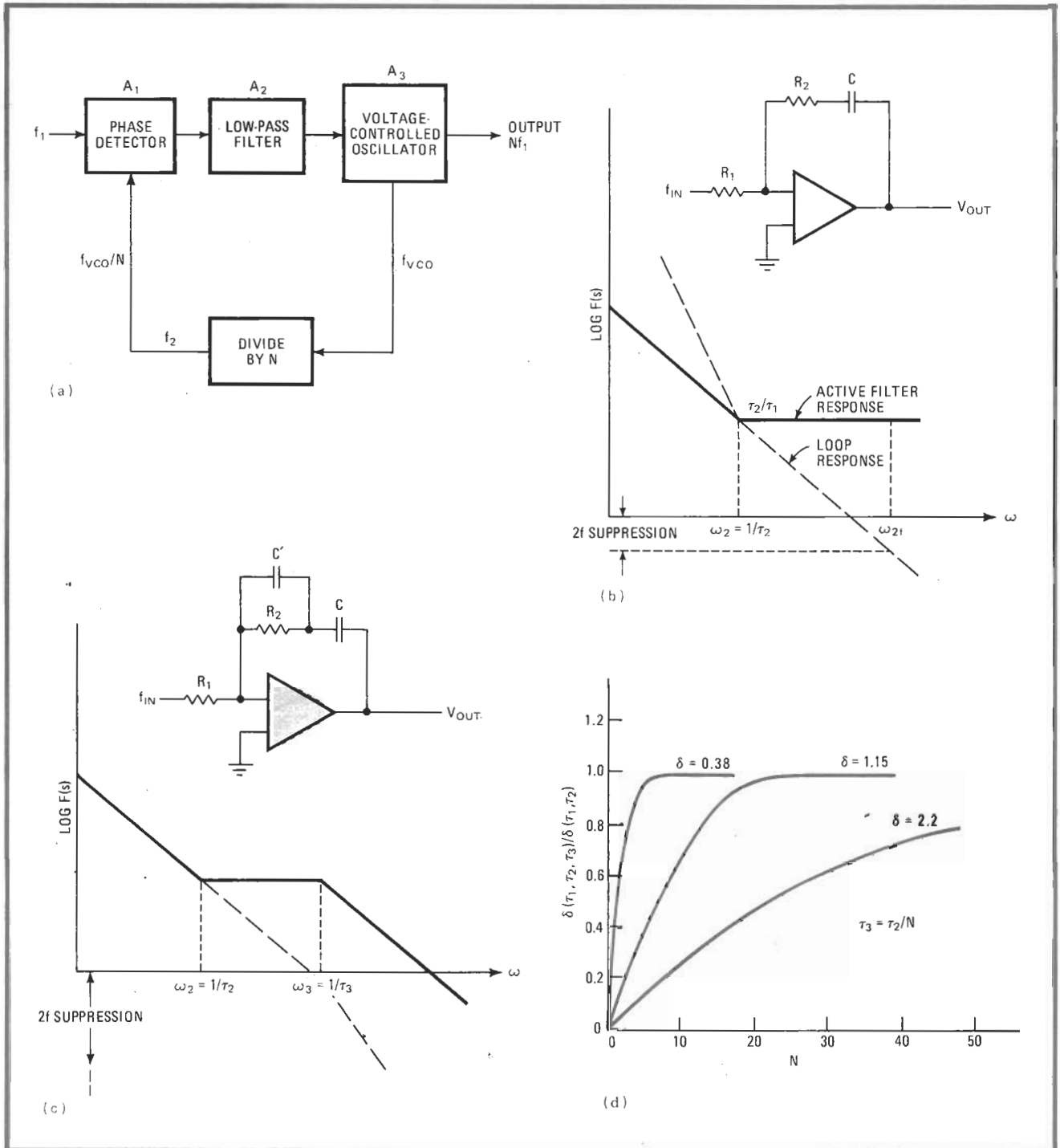Engineer's notebook is a regular feature in *Electronics*. We invite readers to submit original design shortcuts, calculation aids, measurement and test techniques, and other ideas for saving engineering time or cost. We'll pay \$50 for each item published.



Break point. Phase-locked loop (a) generates spurious energy when used in frequency-multiplying circuits. Low-pass filter (b) cannot provide sufficient input frequency harmonic suppression. Capacitor C' (c) adds break or corner frequency to filter response, enables increased rejection of even-order harmonics. Effects of τ_3 on equivalent second-order damping are plotted (d) to aid in design example discussed in text.