

# Digital logic multiplies pulse widths

by N. Bhaskara Rao  
U.V.C.E., Department of Electrical Engineering, Bangalore, India

Using logic elements to multiply the width of incoming pulses by a value selected by the user, this circuit is simple to build and provides a higher accuracy-to-cost ratio than its analog counterpart. It should therefore find numerous uses in synchronous systems, and although its prime function is to provide a multiplication factor of greater than unity, it can generate smaller values as well.

The figure will help make circuit operation clear. The multiplication factor is selected by presetting two 74S192 down counters,  $A_1$  and  $A_2$ . Initially, counter  $A_1$  is set to a value,  $M$ ;  $A_2$  is preset to a second value,  $N$ ;  $A_3$  is zero; and the  $Q$  output of flip-flop  $A_4$  is high.


An incoming pulse of width  $T_1$  (the signal to be multiplied) switches on the 7408 AND gate and enables

$A_3$  to count to a number determined by  $f_1$ , which is derived from an external clock having input frequency  $f$ . Thus, at the end of the pulse, the counter contains the number  $f_1 T_1$ . Note that  $f_1 = f/M$ .

When the trailing edge of the pulse arrives,  $A_3$  is triggered and presets  $A_6$  with the number contained in  $A_3$ . Meanwhile,  $A_4$  is cleared ( $Q=0$ ) by  $A_5$ , and the OR gate is thereby activated so that counter  $A_6$  can initiate counting from its preset value. Note that  $A_6$  is driven by  $A_2$ , the divide-by- $N$  down counter, and that  $f_2 = f/N$ .

The time taken for  $A_6$  to reach zero from its preset value is thus  $T_2 = (f_1/f_2)T_1 = (N/M)T_1$ . At this time, the output from  $A_6$ 's borrow port clears  $A_3$  and presets the flip-flop. Therefore the time between the flip-flop's move to logic 0 (at the trailing edge of the input pulse) and the time its  $Q$  output moves high again is  $T_2$ .

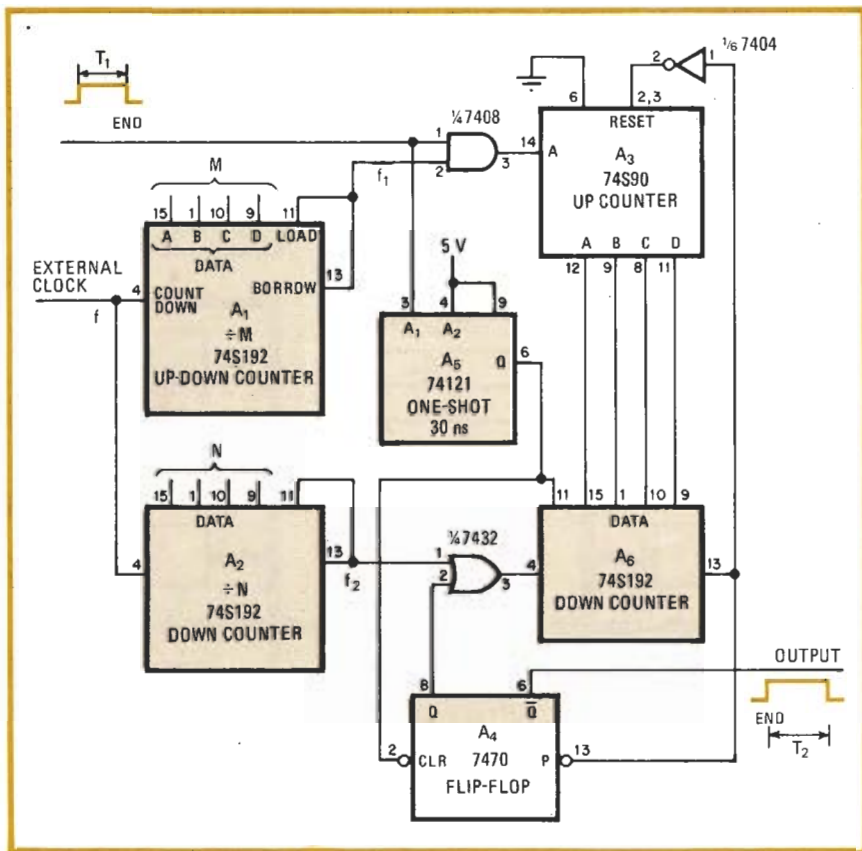The output signal is not derived until the input pulse's trailing edge arrives. The multiplication factor,  $N/M$ , can thus be set to any value greater or less than unity because the conversion is carried out after a delay. Needless to say,  $f$  should be much greater than  $T_1$  for accurate pulse-width multiplication. □



**Width multiplier.** Circuit has no analog elements. Multiplication factor is determined by ratio of  $N$  to  $M$ , set by user.  $A_6$  is preset to  $f_1 T_1$ ; stepped to zero at  $f_2$  rate, it signals flip-flop. Time between state changes of flip-flop is  $T_2 = (N/M)T_1$ .