

# sine-wave oscillator

very low distortion . . . .

L. Boullart

Nowadays, an entire function generator can be constructed from a few simple ICs. When measuring low-frequency equipment, such as audio amplifiers, it is highly desirable to use a low distortion, reliable sinewave generator.

This particular design is not at all complicated as far as construction is concerned and yet it boasts a distortion level of only 0,01%! Its frequency range extends from 10 Hz up to an inaudible 100 kHz and is very simple to operate.

Where modern HiFi equipment — especially the home-constructed kind — is concerned, accurate measurements are almost impossible to carry out. Although frequency characteristics and squarewave signals can be checked, there is little that can be done towards measuring the actual distortion level, that is, assuming the unit is properly built and the amplifier is working correctly. Fortunately, most up-to-date designs are so good, that the distortion level will be negligible. In any case, it is hardly worth buying an expensive oscillator with an extremely low distortion factor and a first-class distortion meter to carry out one or two measurements.

An oscillator can be built in a number of different ways, each particular design having certain advantages and disadvantages. For low-frequency measurements, where the frequency needs to be varied, it is best to use a 'Wien bridge oscillator'. This type of circuit provides low distortion and allows the frequency to be changed fairly easily with the aid of a stereo potentiometer or a dual-ganged capacitor. The design described here is quite compact and straightforward, but nevertheless it is eminently suitable for measuring frequency characteristics and distortion levels. In addition, a Schmitt-trigger has been included in the

circuit to provide squarewave output signals.

## The oscillator circuit

Although most readers will probably know how an oscillator containing a Wien network works and have reference books in which they can look it up, it might not be a bad idea to go into the matter here.

Figure 1a shows a network of two resistors and two capacitors. This constitutes the frequency-determining section of the Wien oscillator. If the transfer function is calculated as  $U_1/U_0$ , the result will show that there is only one frequency with no phase shift between  $U_1$  and  $U_0$ . This will be at the frequency:  $F = 1/(2\pi \cdot R \cdot C)$ . At this frequency the ratio of  $U_1$  to  $U_0$  will be exactly 1:3. If the  $U_1$  voltage is amplified by a factor of three and then fed back to  $U_0$ , as drawn in figure 1b, a perfect oscillator is obtained (since the  $U_1$  and  $U_0$  signals are in phase at that particular frequency). Unfortunately, however, there aren't any opamps available with a manufactured gain of three. As figure 1c shows, this does not matter, as the solution is to connect the RC network between the non-inverting input and the output of an ordinary opamp. A voltage divider ( $R_1$ ,  $R_2$ ) is


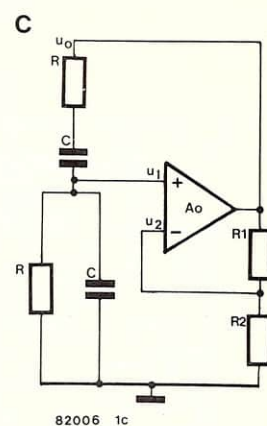
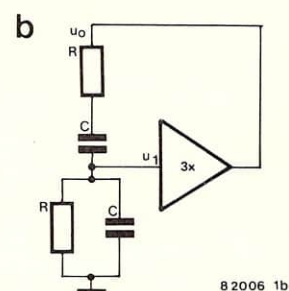


Figure 1. This drawing shows how a Wien bridge can be used to create an oscillator. The voltages  $U_1$  and  $U_0$  will only be in phase for one particular frequency, where  $U_1$  is but  $1/3$  of  $U_0$ . By amplifying the voltage  $U_1$  by a factor of three and feeding it back to  $U_0$ , an oscillator can be obtained.

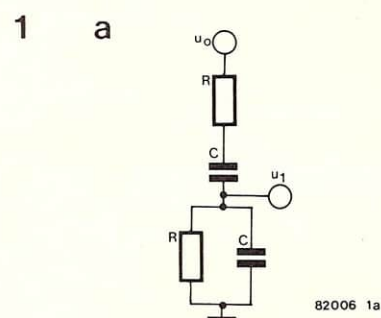

connected to the inverting input of the opamp. The R1/R2 ratio is calculated vice, so that the amplification factor will be:

$$A_u = \frac{R_1 + R_2}{R_2} = \frac{2 \cdot R_2 + R_2}{R_2} = 3.$$

There will now be a sine wave signal at the output of the opamp with a frequency based on the formula provided above. In practice, the amplification factor of three is rather critical, since it is very difficult to maintain both at the opamp side and at the RC network side.

If the amplification slightly exceeds a factor of three, the amplifier's output will produce an ever-increasing output signal until this is limited by the supply voltage. The opamp will then produce a square wave. If, on the other hand, the amplification factor drops slightly the oscillator will either stop operating or simply not start in the first place. When no output signal will be produced at all. Obviously, some sort of control system is needed to adapt the gain so that the circuit oscillates, without affecting the supply voltage. Only then will the output be able to produce a symmetrical sine wave signal.

Usually, such a control system can be set up by choosing a temperature-dependent resistor for either R1 or R2. When the output voltage increases, the

current passing through the temperature-dependent resistor will also rise, causing its resistance to be altered. As a result, the opamp's amplification will be reduced. If, however, the output voltage drops, less current will pass through the feedback resistors and so the resistance will change causing the gain to be increased. This method leads to an equilibrium, where the output voltage is constant.

### The circuit diagram

Figure 2 shows the circuit diagram for the sine wave oscillator. It looks quite different from the block diagram in figure 1. The opamp here is discrete in structure and consists of transistors T1...T4. The input stage is formed by a cascode circuit containing a bipolar transistor (T1) and a FET (T2). In order to obtain a considerable open loop gain, a Darlington transistor was chosen for T3. By means of the current source formed by T4, the collector is linked to the negative supply voltage.

The bridge section comprising the resistors and capacitors is connected between the collector of T3 and the base of T1. Use has been made of a stereo potentiometer with a logarithmic characteristic to regulate the frequency

continuously. Switch S1 acts as a range switch and provides other capacitor values. The four positions provide an overall frequency range of 10 Hz...100 kHz, which amply serves most audio purposes.

The amplitude is stabilised with the NTC resistor R19. The type chosen has a resistance of 1k5 at 25°C. This produces an output amplitude of about 1.5 VRMS. It is very important to use the right type of NTC here, for if the wrong one is used the distortion level will rise alarmingly. The one used here is housed in a glass package with a maximum power dissipation of 20 mW.

The latter is vital, as current passing through the NTC has to heat it. The output signal is fed to P3 by way of C13 and preset P2 (which presets the maximum output voltage). This output level control is followed by an attenuator which has been drawn separately.

Switching S2 connects a Schmitt-trigger in series with the output lead, so that square wave signals are also available. The Schmitt-trigger consists of transistors T5...T7 and the associated components. As readers can see, the circuit has a standard structure and could have been copied straight out of a text book. However, the square wave signals it produces are of a high enough quality


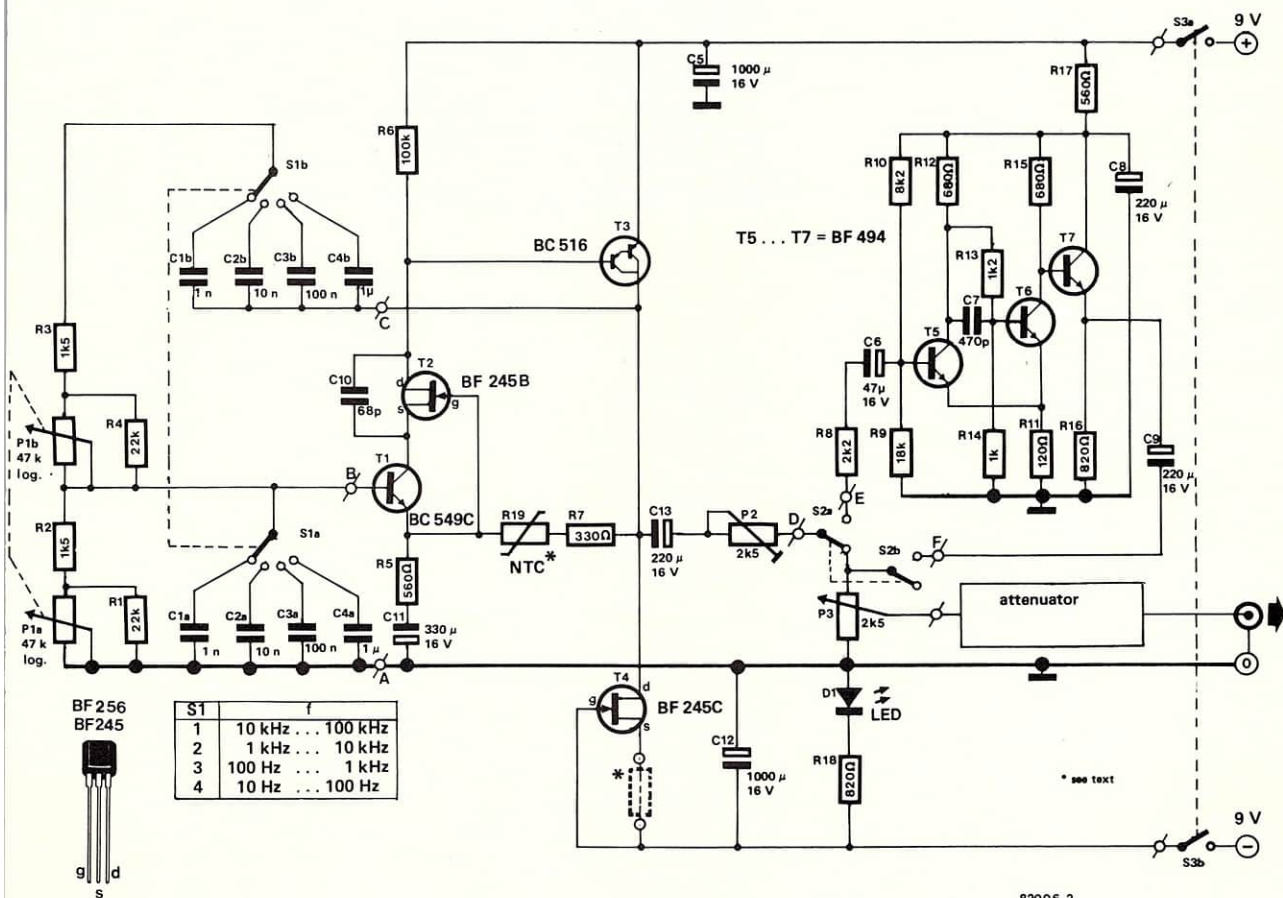


Figure 2. The circuit diagram of the sine-wave oscillator. On the right-hand side a Schmitt-trigger is shown which generates square wave signals. The attenuator is shown in figure 3.

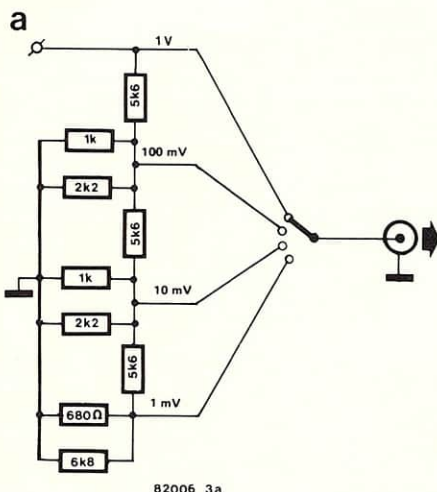

3



b

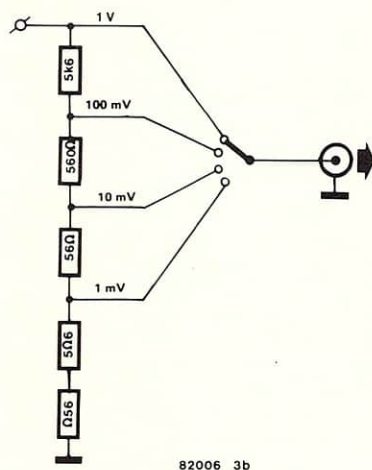


Figure 3. Two different ways in which to build an attenuator. The first version has a constant output impedance of  $565\ \Omega$  (except when it is set at 1 V), whereas the second has a variable output impedance. The latter version is much more straightforward.

for audio purposes. The only disadvantage involved in the circuit, is that the mark/space ratio is somewhat dependent on supply voltage, although this is really of minor importance in this particular application.

Figure 3 shows two attenuator circuits. Usually signal generators feature an output impedance of  $600\ \Omega$ . The same can be done here by using the attenuator in figure 3a. In order to obtain an output impedance of exactly  $600\ \Omega$  for every stage, the resistors will have to have rather "odd" values. If, on the other hand, a slightly irregular output impedance is acceptable, the standard values indicated in the circuit diagram will do. The output impedance will be around  $565\ \Omega$ . It is only at the highest output level that the impedance will be altered between  $0 \dots 5\ k$  (depending on

4

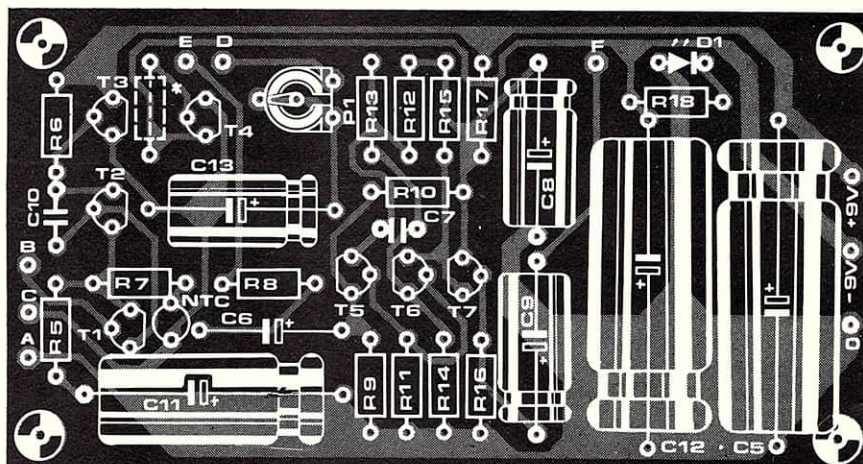
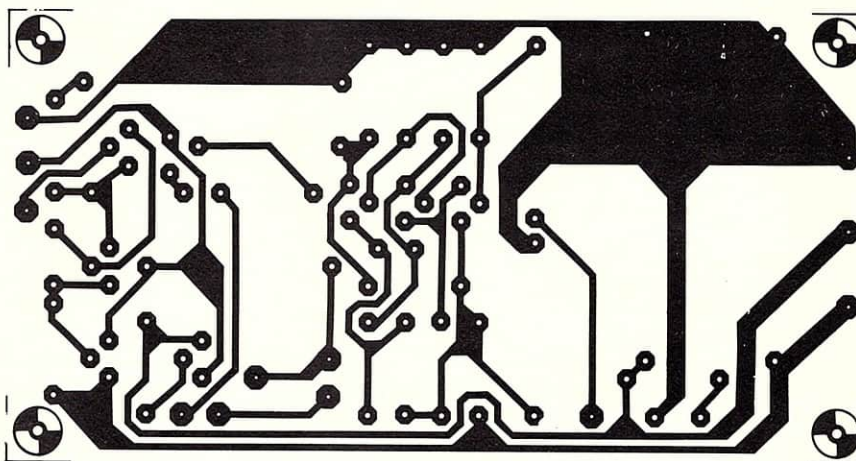


Figure 4. The printed circuit board and the component overlay for the sine wave oscillator circuit. Some of the resistors and capacitors shown in figure 2 are soldered directly to the various potentiometers and switches.

the position of P2 and P3). Provided readers do not require on a standardised output impedance, they can use the attenuator in figure 3b. The output impedance will then of course no longer be constant, but in most cases this does not really matter.

Finally, we still have to mention the LED D1 with its series resistor. This indicates when the oscillator is activated. At the same time, the LED ensures that the circuit's current consumption is equal for both the positive and the negative supply if it is battery-powered. (The current consumption of the LED has been chosen to be the same as that of the Schmitt-trigger circuit.)

### Construction and calibration

The easy way out is, of course, to buy

the board and the parts from your local retailer, solder the lot together and Bob's your oscillator. The device will indeed oscillate, but don't be surprised if it turns out to have a considerable distortion factor. Obviously, a little bit more is required. To start with R5...R7 should be metal foil type having a 1% tolerance. The stereo potentiometer P1 needs to be a good tracking type. Capacitors C1...C4 should also be 1% types, if available. This is not absolutely essential, but it does lead to an accurate scale division for every range. T1 must be a low-noise transistor. Nowadays, various Japanese transistors have an ever lower noise factor than the types mentioned in the parts list. A good example is the 2SC2546, but unfortunately this type is not yet readily available. In addition



## ts list

## sistors:

,R4 = 22 k  
 ,R3 = 1k5  
 = 560  $\Omega$   
 = 100 k  
 = 330  $\Omega$   
 = 2k2  
 = 18 k  
 0 = 8k2  
 1 = 120  $\Omega$   
 2,R15 = 680  $\Omega$   
 3 = 1k2  
 4 = 1 k  
 6,R18 = 820  $\Omega$   
 7 = 560  $\Omega$   
 9 = NTC 1k5 at 25°C Philips  
 /pe 2322 31152  
 = 47 k log stereo  
 = 2k5 preset  
 = 2k5 potentiometer

## pacitors:

a,C1b = 1 n  
 a,C2b = 10 n  
 a,C3b = 100 n  
 a,C4b = 1  $\mu$  (not an electrolytic type)  
 ,C12 = 1000  $\mu$ /16 V  
 = 47  $\mu$ /16 V  
 = 470 p  
 ,C9,C13 = 220  $\mu$ /16 V  
 0 = 68 p  
 1 = 330  $\mu$ /16 V

## micconductors:

1 = LED  
 = BC 549C, BC 550C  
 2 = BF 245B, BF 256B  
 3 = BC 516  
 4 = BF 245C  
 5,T6,T7 = BF 494

## iscellaneous:

= double pole, 4 position wafer switch  
 ? = double pole toggle switch  
 } = double pole switch

ie voltage at T2 will have to be  
 easured once the circuit has been con-  
 ructed. This transistor should be a  
 pe that has a drain current of 12  $\mu$ A  
 a gate-source voltage of -3 V (we will  
 me back to this later). For this reason,  
 might be a good idea to place a tran-  
 sor socket in this position on the  
 ard first.

o get back to building the circuit, part  
 f it is not mounted on the board. This  
 cludes the frequency-determining net-  
 ork at the circuit input (everything  
 required for connections A...C) and  
 ie switch S2 together with potenti-  
 eter P3 and the attenuator.

n the input circuit the capacitors are  
 ldered directly to switch S1 and  
 ewise the resistors R1...R4 to the  
 ereo potentiometer. This section is  
 en connected to the board by means

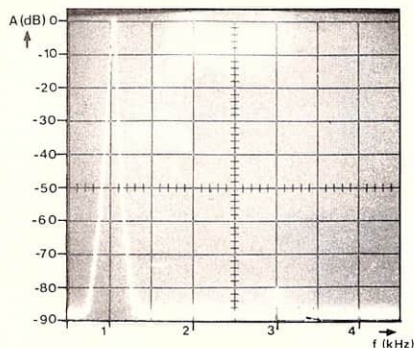


Photo 1. Shown on a spectrum analyser  
 are the oscillator's distortion residues at a  
 frequency of 1 kHz. The first large peak  
 represents the 1 kHz signal. The first even  
 harmonics are at a level of -85 dB with  
 respect to the 1 kHz signal, or rather at  
 0.006%. The first odd harmonics con-  
 tribute 0.01% (-80 dB).

of three wires, after the rest of the com-  
 ponents have been mounted. Points  
 D...F are then linked to switch S2  
 and potentiometer P3 is wired. Finally,  
 the resistors belonging to the attenuator  
 are mounted straight onto the switch.  
 Then the supply voltage has to be con-  
 nected up by way of switch S3.

The power supply may be a straight-  
 forward mains type, consisting of a  
 small transformer, a bridge rectifier, one  
 or two electrolytic capacitors and two  
 voltage regulators similar to those  
 published previously in Elektor. Current  
 consumption will be about 23 mA.

Seeing as the current consumption is so  
 low, the circuit may also be battery-  
 powered. Using four 'flat' 4.5 V bat-  
 teries, the lifespan during intermittent  
 use will be a reliable 100...200 hours.  
 Figure 4 shows the printed circuit board  
 for the sinewave oscillator. A resistor is  
 indicated by way of a dotted line next  
 to transistor T3. Once the entire circuit  
 has been built, in the manner described  
 above, a multimeter is connected  
 between the two connections of the  
 dotted resistor and the meter is  
 switched to current measurement (DC!).  
 After the supply voltage has been  
 switched on, the current measured  
 should be about 15 mA. If it is any  
 higher than this, a resistor should be  
 connected in series with the meter and  
 have a value that makes the meter indi-  
 cate 15 mA. Depending on the result,  
 the resistor or, if not required, a wire  
 link, is soldered onto the board.

The voltage is then measured at T2.  
 Initially this is measured between the  
 source and the gate and then the meter  
 is switched to current measurement and  
 connected to the drain. Several tran-  
 sistors of either the BF 245B or BF 256B  
 type should be experimented with and  
 the one that comes closest to meeting  
 the  $V_{GS} = -3$  V and  $I_d = 12 \mu$ A require-

ment is soldered onto the board.

After this the output voltage can be  
 measured. This is usually around  
 1.5 V<sub>RMS</sub> (measured at the junction  
 of R7 and C13). If necessary, the out-  
 put voltage can be altered slightly by  
 choosing another value for R7. Once  
 this has been done, P2 is adjusted so  
 that the output voltage at the wiper of  
 P3 is exactly 1 V<sub>RMS</sub> when the latter  
 is turned fully clockwise. The attenu-  
 ator can then be used to select a lower  
 output voltage, 100 mV, 10 mV or  
 1 mV, which can also be attenuated  
 with the aid of the potentiometer.

If the squarewave signal observed on an  
 oscilloscope screen looks slightly asym-  
 metrical, the solution is to alter the  
 value of R8. Finally a word of advice:  
 the output amplitude can be kept at  
 a constant level by covering the NTC  
 with a layer of insulating material, such  
 as foam rubber.

## Easier said than done...

This circuit is a perfect example of how  
 an effective device can be built without  
 the need for a lot of ICs or other fancy  
 components. All that the enthusiast has  
 to do is think carefully and decide what  
 the circuit is to achieve and then select  
 the best possible components. The  
 result is a compact design with excellent  
 features. That is exactly how the  
 designer created the prototype which  
 has a distortion level of 0.01% at 1 kHz.  
 The designer even maintains that dis-  
 tortion levels as low as 0.0014% at  
 1 kHz is possible! The frequency range  
 covers 10 Hz...100 kHz within  
 0.15 dB. These are very satisfactory  
 results by any standards. If such a cir-  
 cuit still is not capable of testing a par-  
 ticular audio amplifier, the amplifier  
 must be of such a high quality that  
 there isn't any point in measuring  
 anything anyway!