

ELECTRONIC TRANSIENTS

The Future Belongs to These Odd-Shaped Waves

PERIODIC waves of electrical energy may have many different shapes. Simplest of these is the pure sine wave. More complex waves may have a large number of harmonic frequencies—voice, music, or random noise. In most audio and radio work the exact shape of these waveforms is unimportant—provided the output of the operating device or equipment is not too distorted. Even so-called high fidelity allows for considerable distortion inaudible to the human ear.

In electronic applications — radar, television, and electronic timing, delay, and control circuits—the shape of these waves is very important. They control microsecond action of other circuits and components of the equipment, where accurate timing and measurement often depends entirely upon the wave shape.

Despite their apparent simplicity when viewed on a test oscilloscope, such control waves are usually extremely complex in composition. Simple-appearing waves—such as the saw-tooth, square, and peaked waves, rectangular pulses, and others (Figure 1)—are complex combinations of many waveforms.

Although not sinusoidal, such electronic waves are periodic. That is, they repeat themselves at regular time intervals, permitting examination with a synchronized test oscilloscope.

The composition of these periodic, nonsinusoidal waves is important to an understanding of the operation of all electronic circuits. Because these waves, under the guidance and control of the

special types of electronic circuits, perform the many functions of timing, modulation, measurement, and delay in radar, television, and general electronics work.

USE OF HARMONICS

All complex, periodic waves have their basis in the pure sine wave, the recurrent sine wave having the same frequency as the complex wave. This is called the fundamental or first harmonic.

Component waves of multiple frequency are known as second, third, fourth, fifth, etc. harmonics. And the waves are designated according to ratio of their recurrence frequency to the fundamental. That is, a frequency three times that of the fundamental is known as the third harmonic, a frequency six times the fundamental as the sixth harmonic, and so on.

By skillfully combining certain harmonics (of different amplitudes) with the fundamental, basic sine wave, a complex wave having almost any given shape can be created by electronic circuits.

The *saw-tooth wave*—familiar as a time base control in test oscilloscopes and certain radar applications—consists of the fundamental wave to which are added harmonics of lower amplitude. When only the second and third harmonics are combined with the basic sine wave, the resultant wave [Figure 2 (4)] begins to assume a saw-tooth form. But the positive and negative peaks are not sharp and the slope is irregular. To obtain an acceptable saw tooth wave [Figure 2 (5)] a great many other harmonics—often as many as eight or nine—must be combined with the fundamental.

A *perfect saw tooth wave*—with sharp edges and a perfectly flat slope—would have to consist of an infinite number of added harmonics. For most radar and electronic purposes, however, saw tooth waves with harmonics up to the eighth or ninth are acceptable.

A *square wave* consists of a fundamental and a number of *odd* harmonics only. When the fundamental is combined with a third harmonic of lower amplitude [Figure 2 (6)], the general "square wave effect" is illustrated. Addition of more *odd* harmonics—the fifth, seventh, ninth, and sometimes the 11th—results in a wave shape more nearly approaching a perfect square. However, a *perfect square wave* is impossible to obtain since it would have

(Continued on page 350)

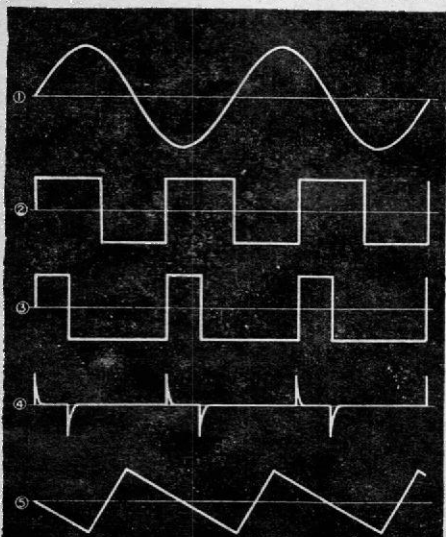


Fig. 1—Types of periodic waves. 1—Sine wave. 2—Square wave. 3—Rectangular wave. 4—Peaked wave-forms. 5—Saw-toothed wave.


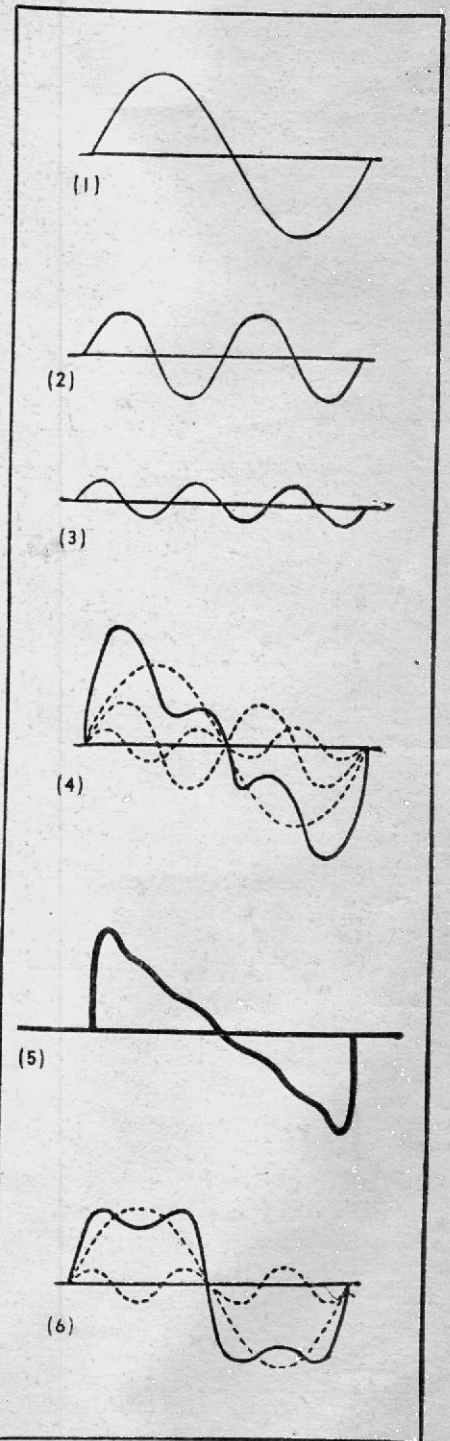



Fig. 2—Composition of complex wave forms: 1—Fundamental sine wave. 2—Second harmonic. 3—Third harmonic. 4—Fundamental and 2nd and 3rd harmonics. 5—Fundamental with 2nd, 3rd, 4th, 5th, 6th, 7th and 8th harmonics. 6—Fundamental with third harmonic.

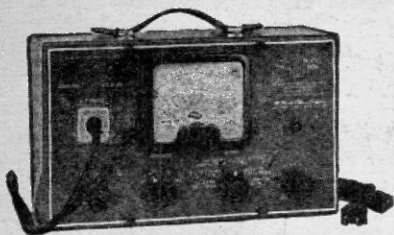for everything in
ELECTRONICS
and **EQUIPMENT**
follow
ARROW!
"VOMAX"



Choice of Electronic Engineers!
NEW POST-WAR V.T V-O-DB-MA METER
D.C. volts at 51 and 126 megohms A.C. and r.f. volts at 6.6 megs. Resistance .2 ohms to 2,000 megs. D.C. current 1.2 ma. through 12 amperes. D.B. — through + 50 . . . plus visual dynamic signal tracing. In our critical opinion these features establish "VOMAX" as standard of comparison. Prompt shipment. Your cost only..... **\$59.85**

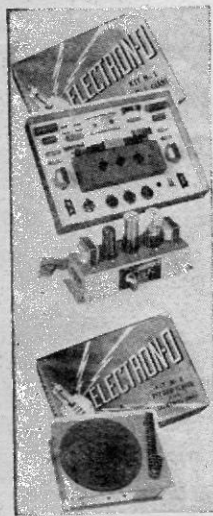ELECTRON-O "Make-it-Yourself"
ELECTRONIC & ELECTRICAL KITS




Little Giant AMPLIFIER
Parts and instructions for building the Little Giant Amplifier. Enough power to fill a large sized room. Easy to assemble—can be used in many instructive and entertaining experiments.
Your net cost complete **\$18.95**

RECORD PLAYER & CONTROL UNIT
Everything needed to build a real phonograph record player. A real electric turntable motor—a crystal reproducer arm—even parts for building the cabinet. Special switch to change from mike to record player.
Your net cost complete **\$17.95**

BRUSH TRANSCRIPTION TYPE CRYSTAL PICKUP

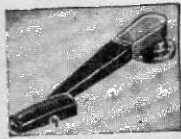Plays 16" records. Wide-range frequency response (flat within plus or minus 2.5 db. from 50 to 4,000 cps, slight rise to 10,000 cps.). Complete with high impedance amplifier used for commercial "Constant Velocity" recordings.



Your net price **\$26.46**

Write to us for anything in **ELECTRONIC PARTS and EQUIPMENT**. Get our mailing list and keep informed as merchandise becomes available.

ARROW
ELECTRONICS COMPANY
82 CORTLANDT ST., NEW YORK 7, N. Y.
Orl:landt 7-2935 — 2998

ELECTRONIC TRANSIENTS

(Continued from page 310)

to consist of an infinite number of odd harmonics.

Omitting certain odd harmonics in the series and changing the amplitudes of others, results in a variant of the square wave—the *rectangular wave*.

Countless other periodic wave shapes are encountered in electronics. But their shape always depends on the harmonics that are present, their relative amplitudes, and their relative phase relations with each other. The steeper the sides of the final wave shape, the more harmonics it contains.

All of the wave shapes shown in Figure 2 have equal alternations. That is, the positive portion of each wave has mirror symmetry with the negative portion. Sometimes waves are encountered that do not have equal alternations but which are periodic. Again, these waves are the result of combining a fundamental and certain harmonics of given amplitude.

Thus, any shape of recurrent wave may be produced by the careful selection and combination of a fundamental and harmonics of the basic frequency. And, in like manner, any existing wave may be broken down into a fundamental and certain harmonics.

DISTORTION

This represents distortion of the original, fundamental wave. But it is desirable distortion. The large number of harmonics present in the wave generally is necessary to obtain specifically shaped waves, without which certain types of electronic circuits—such as timing relays, delay and control devices, or others—could not function.

Steep-front waves are widely used in practically all phases of radar, television, and electronics. As such, they represent a highly distorted wave consisting of a great number of harmonics.

For this reason it is impossible to pass such a wave through an ordinary audio or radio circuit. To do so would introduce *unwanted* distortion and loss of shape.

When amplification of such a complex wave is required, the fundamental and *all* harmonics must be amplified equally. In radar and television this led to the development of wide-band or *video* amplifiers, capable of equal amplification of all frequencies from a few cycles to several megacycles. Most coupling stages, also, are required to pass complex waves without discrimination as to frequency, phase, or amplitude of the component harmonics.

In some electronic applications, however, just the opposite is true. Circuits are designed to introduce the intentional distortion. Particularly in radar, this *controlled* distortion is necessary for shaping control waves prior to their application to the final stage of some other component. A typical example of this is the very steep-front, narrow, rectangular pulse required to modulate a

radar transmitter during each "pulsing period" of the set's operation.

The behavior of these distortion circuits can best be understood as transient phenomena—or "transients." A measure of the introduced distortion is sometimes known as the *time constant*.

TIME CONSTANT

Ohm's law states that the voltage across a resistance is equal to the current through it times the value of the resistance. In other words, a voltage is developed across a resistor only when current flows through it. By controlling this flow of current the shape of the voltage wave (across the resistor) can be controlled.

Simplest method of current control is to utilize the charging and discharging properties of a condenser. In a simple

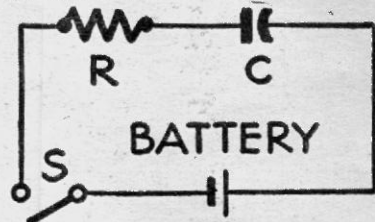


Fig. 3—The simplest wave-forming circuit.

R-C circuit [Figure 3], when the switch S is closed the rate of the condenser charge is limited by the amount of resistance R in the circuit. The charging of the condenser is not instantaneous, but of an exponential nature. It takes place within a measurable time, determined by the amount of resistance R and capacitance C.

The product of R and C is a measure of the time (in seconds) required for the condenser charge to reach 63 percent of its final or fully charged value. This product (RC) is known as the *time constant* where R is in ohms and C is in farads.

When the condenser [Figure 3] is discharged through the same resistance R, the discharge current will be limited by the resistance. The current decrease will again be exponential, the slope at any time depending upon the values of R and C. The time constant is again a measure of the time required to discharge the condenser.

When the time constant for a given

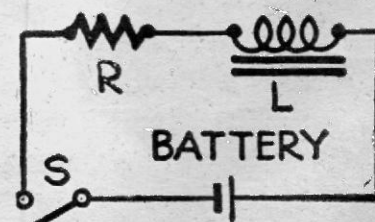


Fig. 4—An inductor changes the wave shape.

circuit equals 1 (or RC seconds), the charge on the condenser is considered to have reached 63 percent of its final value. When the time constant equals 5 (or 5RC seconds), the condenser is

considered, for all practical purposes, to be fully charged.

Conversely, in discharging, when the time constant equals 1 (RC seconds), the amount of charge on the condenser is considered to be 37 percent of its final voltage. And when the time constant equals 5 (or 5RC seconds), the condenser is considered to be fully discharged.

Current flow through a resistance can also be controlled by means of inductance-retarding effects. In a simple R-L circuit [Figure 4], when the switch S is closed the battery forces a current through the inductance L. The reactance of the coil retards any change in the flow of current, and the current increases exponentially—the rate depending upon the values of R and L.

The quotient L/R is a measure of the time required for the current to rise to 63 percent of its full value. And this quotient is known as the time constant (in seconds), where R is in ohms and L is in henrys. There is a similar exponential fall of current when the circuit [Figure 4] is discharged through the resistance R, the time constant again being a measure of the time required for current decay.

By utilizing transient current effects of either R-C or R-L circuits, it is possible to influence the distortion and formation of voltage waves—to any desired shape. For instance, the common saw-tooth wave used for the time base of most types of cathode ray tubes is but the charge-discharge wave taken from across a condenser.

Resistance-inductance circuits are occasionally used in electronic delay, timing and counting circuits. But the resistance-capacitance or R-C circuit has wider general use in radar, television, and electronics.

TRANSIENT EFFECTS

In a given R-C circuit [such as Fig. 3], if the value of either resistance or capacitance is increased, or if both are increased, the circuit will have a longer time constant because the condenser will take longer to charge.

Thus, the value of either R or C, or both, can be varied to obtain any desired value of charging time.

The terms *long* time constant and *short* time constant are purely relative evaluations.

A *long* time constant means that the time (expressed in RC seconds) is long compared with the time necessary for the impressed or signal voltage to complete half a cycle. If the product of R and C is large enough there will be little or no introduced distortion.

A *short* time constant means that the time (expressed in RC seconds) is short in comparison with the frequency of the impressed or signal voltage. A circuit possessing a short time constant introduces a particularly desirable form of distortion known as *peaking*.

The input wave applied to either R-C or R-L circuits may be of any shape. But the greatest amount of distortion can be obtained in the output when the

(Continued on following page)

HAM HEADQUARTERS FOR

Equipment and Information

15 YEARS of Service


to HAMS throughout the
U.S. and Canada.

Complete Line

of nationally famous
Radio and Electronic
Parts and Equipment.

Thousands of Items

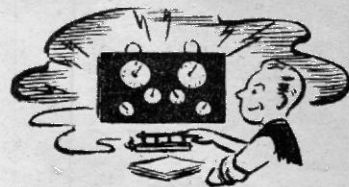in stock right now . . .
comprising every well
known brand of Component
Parts and Equipment.



Get Started on Your
"DREAM SET"
TODAY!

We have all the component parts and equipment and our HAM department, which is staffed by Engineers, will gladly help you with your problems. Write, 'phone, or visit us today.

FREE Write today for our current bulletins about extraordinary values in surplus Radio and Electronic Component Parts and Equipment.

Radio Product Sales Company

238 WEST 15TH STREET

LOS ANGELES 15, CALIFORNIA

PRospect 7471



UNIMETER


This unit fulfills an extremely important need for general utility portable service equipment. It has wide range coverage for both a-c and d-c measurements of voltage, current measurements on d-c and the popular ranges on resistance.

The UM-3 is designed to clearly indicate all the functions which aid in the prevention of application of high voltages when preparing for current or resistance measurements.

Other G-E units for better servicing include: Tube Checker TC-3, Unimeter UM-4, and Oscilloscope CRO-3A.

For details write: *Electronics Dept., Specialty Division, General Electric Company, Syracuse, New York.*

Electronic Measuring Instruments

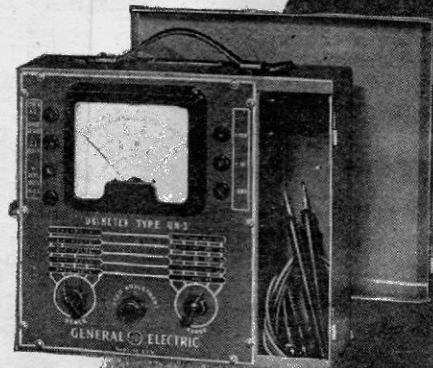

GENERAL ELECTRIC



177-E1

UM-3

FOR EVERYTHING IN RADIO

WRITE
Leo, W9GFQ
For Fast Delivery!



Get Leo's own personal, sudden service on your radio and electronic needs. Quick delivery, lowest prices, liberal trade-in allowances.

SERVICE DEALER NEEDS



WRL MULTITESTER

Steel case with 30-60% angle. Cat. No. 16-491 Less Leads.. **\$1875**

Handles AC DC Voltmeter, DO Milliammeter, high and low range Ohmmeter. 3" meter with sturdy D'Aronsalv movement. Size 5 1/2 x 8 x 3 1/4.

A complete stock of tools, replacement parts, test equipment, intercom and public address systems . . . everything for the progressive service dealer.

FOR EXPERIMENTERS

PHONO AMPLIFIER KITS

Complete with tubes, speaker, stamped chassis, and all resistors and condensers.

Cat. No. 7-271 \$9.50 ea. Lots of 3, ea. **\$915**

Crystal sets, Antenna Kits, Code Oscillator Kits, Transmitter Kits, and many other items for the experimenter and radio enthusiast.




HAM NEEDS

Transmitting tubes, condensers, mikes . . . everything for the Ham. One of the country's largest stocks of Ham equipment. Write Leo, W9GFQ, today, and be first with the latest. We invite inquiries for special equipment of all kinds.



TRANSMITTERS

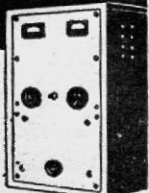For peak performance and more dollar for dollar value, get a WRL Transmitter Kit . . . designed in Leo's own laboratories . . . tested and proven. Available in 15, 35, 70, and 150 watt kits as well as kits custom built to your own specs. Write Leo today for complete details, prices and terms.



RECEIVERS

Here are just a few of the many well-known receivers offered by Leo:

- Hallerasters SX-25 \$ 94.50
- Hallerasters S-20R \$ 60.00
- Hallerasters SX-28A \$225.00
- Echophones EC-1A \$ 29.50
- Hammarlund HQ-129K \$129.00
- National NC-2-40C \$225.00

Write for details of our trade-in plan and easy terms



Free!

NEW POST WAR 52 PAGE FLYER

62 pages packed with real buys in radio, electronic, and general merchandise. Write for your free copy today.

- Send for these exclusive items:
- Tube and Circuit Book 10c
- Giant Radio Reference Map (size 3 1/2' x 4 1/4') 15c
- Gandy Tube-Base Calculator 25c

Address Dept. RC-2 Council Bluffs, Iowa

Wholesale RADIO LABORATORIES

ELECTRONIC TRANSIENTS

(Continued from previous page)

input wave consists of abrupt changes, that is, when the input wave has very steep sides. Most ideal type of input wave is the *asymmetrical square wave*.

Figure 5 illustrates such a signal voltage applied to two kinds of R-C circuits. By earlier definition, the upper circuit has a short time constant (RC=0.001 seconds), the lower circuit has a long time constant (RC=0.1 seconds), both with respect to the frequency of the applied square-wave voltage.

When the voltage E is applied to the short time-constant circuit [upper Figure 5], the condenser is charged to E volts according to the rate of charge permitted by the values of R and C. Polarity of the condenser charge is determined by the polarity of the applied square wave.

As the input voltage changes, the voltage across the condenser, e_c , follows the rate of charge and discharge. This wave form is known as the *integrated portion* of the original impressed square wave. Should such a sloping wave, e_c , be desired to operate or control an electronic circuit, the voltage wave could be tapped off from across the condenser and fed to other stages or components. This circuit is referred to as an *integrator circuit*.

Of more practical use, however, is the *peaked wave* appearing across the resistance, e_r . Such a circuit is referred to as a *differentiator circuit*.

Peaking is an important form of distortion, finding wide use as a trigger impulse. The output voltage, e_r , is often applied to limiting or other types of pulse-forming circuits to obtain extremely narrow and precise rectangular impulses.

Thus there are two principal types of distortion in the R-C circuit: integration and differentiation.

Distortion of the input square wave by a short time constant R-C circuit is due to the poor low frequency response of the stage. The square wave has steep sides, and therefore a large number of *odd harmonics*. The highest frequency harmonics cause the impressed wave to be even further removed from the shape of the fundamental sine wave. Reactance of the condenser is greatest for low frequency harmonics, causing an exaggeration of the high frequency harmonics in the resistor output wave, e_r .

Although both waveforms, e_c and e_r , are available for use, either but only one of the two are ever utilized because of loading effects on the stage. And of the two types of output waves, the voltage, e_r , is more generally used.

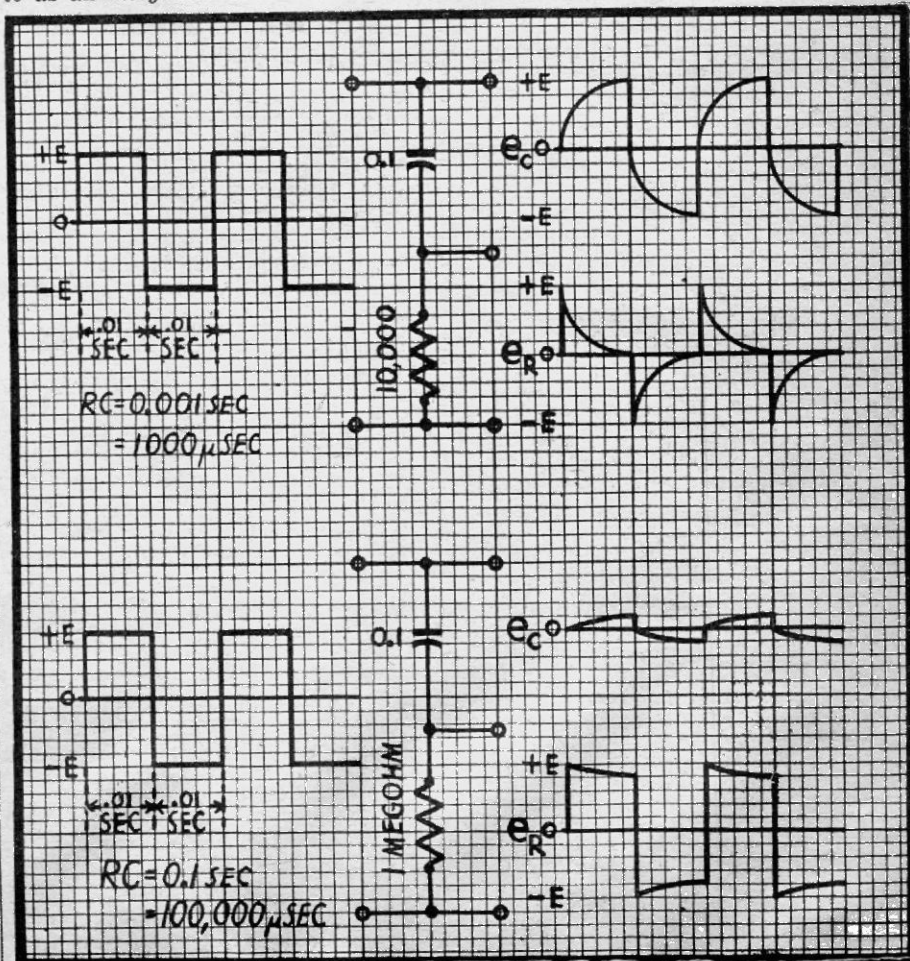


Fig. 5—Distorting circuits for shaping waves and the forms that may be produced by them.

A long time-constant circuit [lower Fig. 5] also provides two waveforms, but of somewhat different nature. In this circuit the time constant is ten times the required time for a half cycle of the impressed square-wave voltage. When this voltage E is applied to the circuit, the condenser does not charge to its full value during an alternation. Before it has time to charge fully, the polarity of the impressed voltage is reversed.

The wave across the condenser, e_c , is of little use because of its diminished amplitude.

The integrated voltage across the resistance, e_r , is almost a duplicate of the impressed square wave. If the time constant for this particular circuit were 40 or 50 times that of the signal frequency, the voltage across the resistor would be almost identical with the input voltage. And the condenser voltage, e_c , would have no perceptible change.

Since practically the entire voltage drop of the R-C circuit [lower Fig. 5] is across the resistance, this explains the wide use of long time-constant circuits as coupling devices between stages of resistance-coupled amplifiers. Careful selection of R and C values is necessary, since improper selection might result in a short time-constant circuit introducing unwanted distortion.

Wave shapes other than square waves may be applied to either long or short time-constant circuits, resulting in various wave forms in the differentiated or integrated output. For instance, a rectangular wave may be integrated to obtain a saw-tooth voltage wave.

However, a pure sine wave suffers no distortion when passing through either a long or short time-constant circuit, since one of the important mathematical properties of a sine wave is that it may be differentiated any number of times without changing its shape.

Besides the important distortion effects of R-C and R-L circuits, the time constant of such simple circuits is the basis for all electronic delay and timing circuits. The delay action depends upon the R-C or R-L values, and the time required for a current to build up or decrease. The retarding action of these circuits can be utilized to achieve either postponed control actions or to measure required time intervals.

These circuits permit delayed action of both electrical and mechanical devices, control of circuits during pre-scheduled intervals of time, and other electronic functions.

In radar and television applications, selected impulses containing very high-order harmonics are used to synchronize the operating of many components.

CORRECTION

An error occurred in the article "Elements of Radar" on page 169 of the December issue. In the 24th line, second column, the time for a pulse to travel 3270 yards should have been 10, not 50 microseconds. The time for the full circuit would of course be 20 microseconds instead of 100 as stated.

SERVICEMEN'S HEADQUARTERS FOR QUICK DELIVERY!

We carry a complete line of Standard

Test Equipment
Amplifiers
Recording Devices
Phono-pickups
Microphones

and the hard-to-get equipment you have waited so long to obtain. Please send us your order or write us what you need. We will show our appreciation by rendering any helpful service to you.



This month's specials are on Weston!

VOLT-OHM MILLIAMMETER

Model 697
Illustrated

24⁰⁰ NET

Weston Analyzer Model 772 type 6
\$49.50 net

Weston Tube Checker Model 777

\$49.50 net

Consult us on your many sound problems and requirements. Estimates and help cheerfully given. We have many standard systems now available, for immediate delivery. Priced from \$100.00 up, complete with tubes.

JACK GREENE

BE 3-9374

79 CORTLANDT ST. NEW YORK, N. Y.

ORDER NOW!



NEW ECHOPHONE EC-1A RADIO RECEIVER

Be one of the first to own this popular set for short-wave and regular broadcast reception. Order now for earliest delivery. Many new features! Covers entire tuning range from 550 Kc. to 30 Mc. (550 to 9.85 meters) in 3 bands. For 110-125 volts AC-DC. Automatic noise limiter. Built-in PM speaker. Complete with tubes. Net **\$29.50**

Other well-known receivers such as:

Hollicrafters S-20R.....\$60.00
Hollicrafters SX-25.....\$94.50
Hammerlund HQ-129X.....\$129.50

Net, F.O.B. Chicago (All prices subject to change)

ALLIED RADIO CORP.

833 W. Jackson Blvd., Dept. 2-B-6, Chicago 7

- Ship ECHOPHONE EC-1A
 Enclosed \$.....
 Send additional information on Echo-
phone EC-1A.
 Send information on other Communica-
tions Receivers and Time Payment Plan,
without obligation.

Name.....

Address.....

City..... Zone..... State.....

SPEED UP REPAIRS WITH THESE G-C AIDS!



FREE STEEL CABINET

G-C Dial Belt Kits

Every Serviceman needs a G-C Dial Belt Kit. Save money—be ready for that repair job. Finest woven fabric replacements. Easy to install—no stretch—no adjustments. Supplied in kits of 25, 50, 100, 200 or 300 Belts in sturdy metal box with slide-in drawer. Free Belt Guide and measuring device.



G-C Dial Drive Cables

G-C has a complete line of Dial Drive replacement cables. Available by the spool for prompt servicing of all sets. Every Serviceman should have a complete assortment. Best in quality—extra strength. Preferred by Radio Men everywhere.



G-C Radio Service Cement

The best Cement for Sinker and Radio Work. Especially suitable for cementing replacement cones and repairing rattling and torn cones. Also used on glass, to seal adjustments, hold wires in place, etc. Dependable, vibration proof, water-proof and fast drying.

Write for New G-C Catalog No. 146 and G-C Dial Belt and Service Book

Immediate Delivery on all G-C Products

Order From Your Radio Parts Jobber
ALWAYS ASK FOR G-C PRODUCTS



GENERAL CEMENT MFG. CO.
ROCKFORD, ILLINOIS

RADIO SERVICEMEN: RADIO PARTS—TUBES

BARGAIN PRICES—NO PRIORITIES

TUBES—12SK7, 12SQ7, 25L6, 50L6, 6V6GT...\$0.85
TREMOR 450 OHM SPEAKERS, 4 of 5 inch... 1.85
FILTER COND., 20-20 Mfd., 150 V... .39
BY PASS COND., .01, .02, .05, .1—600 V... .07
LOOP ANTENNA (High Gain)... .59
ANT. & OSCILL. or ANT. and RF COIL SETS... .63
RESISTOR KIT—50 Ass'd, 1/3 to 1 Watt... .99

Write Today for Bargain Bulletin
RADIO DISTRIBUTING CO., Pasadena 10, Calif.