

Waveform generator minimizes amplitude dependency

Marián Štofka, Slovak University of Technology, Bratislava, Slovakia

Engineers have long used function-generator circuits employing analog integrators and high-hysteresis comparators. The outputs of these circuits often depend on variations in temperature, power-supply voltage, load, and parts. However, you can pump new life into the classic triangular/rectangular-waveform generator using the circuit in **Figure 1**. This circuit uses a precision reference-voltage source and the diode network comprising IC₁, IC₂, and IC₆; dual analog SPDT (single-pole/double-throw) switch IC₃; integrator IC₄; and comparator IC₅. The result is a ramp- and square-wave generator that holds its output stable in the face of those variations. Comparator IC₅ uses a switching technique to achieve its stable high hysteresis. **References 1 and 2**

provide more details, including how the Schottky-barrier diodes of IC₆ suppress charge injection.

The output of IC₅, an ADCMP601 comparator, is initially low, forcing the ADG736 analog switch, IC₃, to connect a positive reference voltage, V_{REF+}, to IC₄'s inverting input. Simultaneously, the S₂ switch connects a negative reference voltage, V_{REF-}, to the integrator's R₁ resistor. As long as the comparator's output is low, the integrator's output, V_{INT}, increases linearly until it reaches V_{REF+}, the comparator's positive-threshold level. At that point, the output of the comparator changes to high, which turns on the B channels of both multiplexers as their A channels turn off.

When the switch positions change, the integrator integrates positive refer-

DI's Inside

54 Produce current from positive or negative high-voltage supplies

55 Arrange LEDs as seven-segment displays

57 Logic gates form high-impedance voltmeter

58 Measure resistance and temperature with a sound card

► To see all of EDN's Design Ideas, visit www.edn.com/designideas.

ence-voltage V_{REF+}, and V_{INT} decreases linearly until it reaches the negative threshold V_{REF-}, which the comparator sets. The cycle then repeats. A bipolar reference source comprising IC₁ and IC₂ creates V_{REF+} and V_{REF-}. This part

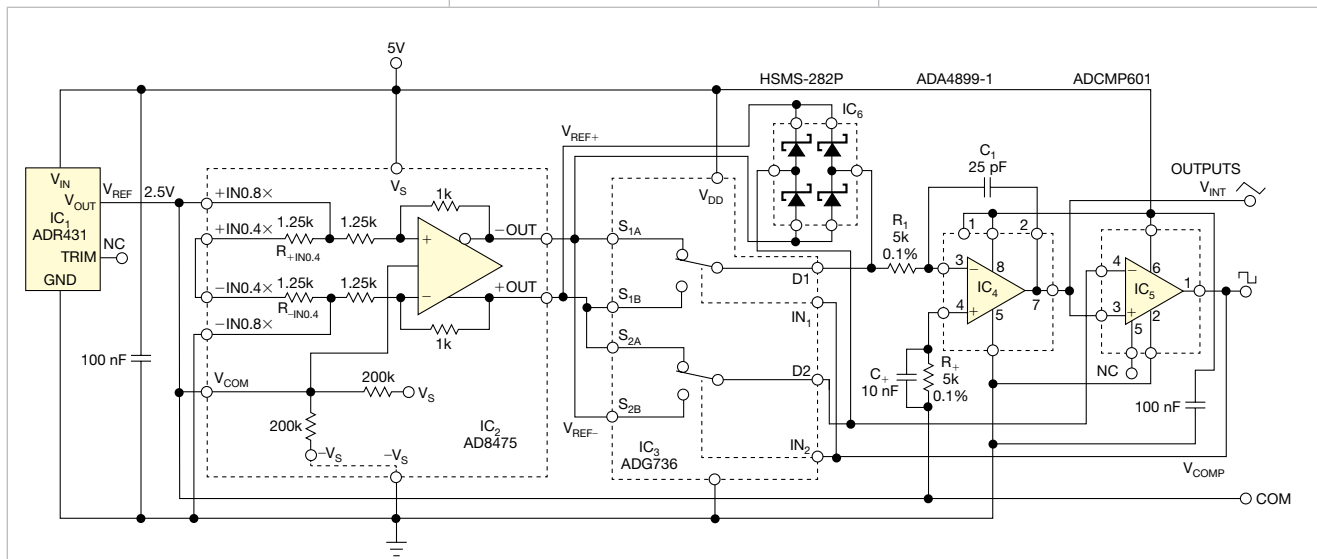


Figure 1 Creating hysteresis by switching precision reference voltages within the waveform generator ensures high insensitivity of the amplitude of triangular waveforms on supply-voltage variations.

designideas

of the circuit is a slight modification of the circuit in an earlier Design Idea (Reference 3).

As the ramp-up/ramp-down cycle repeats, the integrator produces a symmetrical, triangular waveform of V_{INT} , and a rectangular waveform, V_{COMP} , appears at the output of the comparator. The amplitude of V_{INT} is approximately $(V_{REF+} - V_{REF-})/2$. The duty cycle of the rectangular waveform is close to 50%. The thresholds of the comparator are independent of the output load, and you derive them from a precision source of reference voltages. Thus, the circuit has low sensitivity of the repetition frequency of its output to supply-voltage variations and to load variations. In a simplistic model of the generator, the amplitude of the triangu-

lar waveform at the output of the integrator no longer depends on variations of supply voltage.

Experimentally, increasing supply voltage V_S from 5.0365 to 5.437V increases the amplitude of the triangular waveform by 2.85 mV, representing 0.285% of full-scale. Under the same conditions, a classic triangular/rectangular-waveform generator typically shows an 8% increase in amplitude. Thus, this circuit reduces the dependence of amplitude on supply-voltage variation by a factor of about 28.

In testing this circuit, you can expect an output frequency of 1.366 MHz with a supply voltage of 5.0365V. When the supply voltage is 5.437V, the output frequency will be 1.368 MHz. The time constant sets the repetition

rate. In this case, the repetition rate is one divided by four times the time constant for an ideal comparator and ideal switches. The comparator's propagation delay and the on/off times of the switches lower the repetition rate to lower than the ideal value. **EDN**

REFERENCES

- 1 Štofka, Marián, "Circuit uses two reference voltages to improve hysteresis accuracy," *EDN*, Jan 7, 2010, pg 43, <http://bit.ly/g9GmAc>.
- 2 Štofka, Marián, "Schottky diodes improve comparator's transient response," *EDN*, Jan 21, 2010, pg 32, <http://bit.ly/el3N0d>.
- 3 Štofka, Marián, "Build an accurate bipolar reference," *EDN*, May 12, 2011, pg 42, <http://bit.ly/knjieC>.