

Build a precise dc floating-current source

D Ramírez, S Casans, C Reig, AE Navarro, and J Sánchez, University of Valencia, Burjassot, Spain

Although well-known to active-filter theorists and designers, GICs (generalized impedance converters) may be less familiar to analog generalists. Comprising a one-port active circuit typically comprising low-cost operational amplifiers, resistors, and capacitors, a GIC transforms capacitive reactance into inductive reactance and thus can substitute for an inductor in a filter that an RLC-transfer function describes. In addition, the flexibility of a GIC's input-impedance equation permits the design of virtual impedances that don't exist as physical components—for example, frequency-dependent resistance (Reference 1). The GIC, which its developers introduced 30 years ago, has seen its greatest application in ac-circuit and active-filter applications.

Figure 1 shows a classic GIC circuit

in which the input impedance, Z_{IN} , depends on the nature of impedances Z_1 through Z_5 . The following equation describes the circuit's input impedance:

$$Z_{IN} = \frac{V_{IN}}{I_{IN}} = \frac{Z_1 \times Z_3 \times Z_5}{Z_2 \times Z_4}$$

For example, if Z_1 , Z_2 , Z_3 , and Z_5 comprise resistors R_1 , R_2 , R_3 , and R_5 , and Z_4 comprises capacitor C_4 , then the input impedance, Z_{IN} , appears as a virtual inductor of value L_{IN} :

$$L_{IN} = \frac{R_1 \times R_3 \times R_5 \times C_4}{R_2}$$

Figure 2 shows the GIC circuit in its dc configuration. When you consider the GIC circuit in a purely dc environment, you can envision new applications. For example, you could replace impedances Z_1 through Z_5 with pure resistances R_1 through R_5 . Instead of an

DIs Inside

84 Frequency dithering enhances high-performance ADCs

86 Memory-termination IC balances charges on series capacitors

88 Voltage reference is software-programmable

ac input-voltage source, connect a precision temperature- and time-stable dc reference voltage to the input port. A simple circuit analysis using ideal op amps for IC₁ and IC₂ shows that the reference input voltage, V_{REF} , appears across resistor R_5 , and, as the following equation shows, a constant current, I_O , flows through R_5 .

$$I_O = \frac{V_{REF}}{R_5}$$

However, op amp IC₂'s noninverting input diverts a small amount of current from the junction of R_4 and R_5 , and I_O thus also flows through R_4 . Selecting

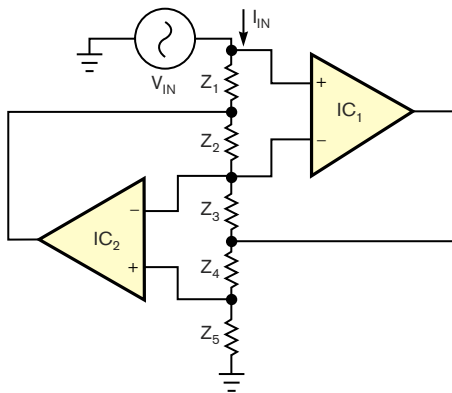


Figure 1 A classic generalized impedance converter provides a single-port impedance that appears at V_{IN} . The schematic omits power connections for clarity.

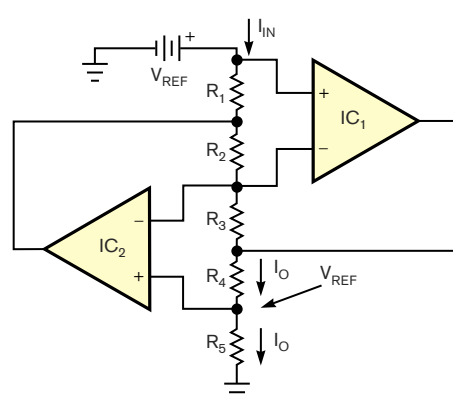


Figure 2 Replacing all of a GIC's impedances with resistors creates a constant-current source.

designideas

large values for R_1 , R_2 , and R_3 helps minimize current drawn from the reference voltage. For example, the circuit can supply 2 to 10 mA to R_4 and draw only a few tenths of a microampere from the reference source. Using tight-tolerance and low-drift components for V_{REF} and R_5 ensures the stability of I_O . Applications include providing constant-current drive for Wheatstone-bridge and

platinum-element sensors (**Reference 2**). In addition, you can replace R_4 with a series of resistive sensors as in an Anderson loop (**Reference 3**).**EDN**

REFERENCES

1 Franco, S, *Design with Operational Amplifiers and Analog Integrated Circuits*, Third Edition, ISBN 0072-320842, WCB-McGraw-Hill, 2001.

2 Ramírez, Diego, S Casans, and C Reig, "Current loop generated from a generalized impedance converter: a new sensor signal conditioning circuit," *Review of Scientific Instruments*, Volume 76, No. 1, January 2005.

3 Anderson, KF, "Looking under the (Wheatstone) bridge," *Sensors*, June 2001, pg 105.