

Analog Applications Journal

BRIEF

IC Powers Portable Photographic Flash

By Scot Lester • Portable Power DC/DC Applications

Introduction

Upper end photographic equipment, either optical film- or digital-based, requires Xenon flash tubes in order to photograph in low-light conditions. Xenon flash tubes can provide a burst of high-intensity light that is essential for photography of objects at a distance, moving at high speeds, or in low-light conditions. The light spectrum generated by a Xenon gas discharge tube closely replicates that of the sun, therefore providing very accurate color reproduction.

Xenon flash tubes require a high voltage across their electrodes in order to flash once a trigger signal is applied. This voltage is typically around 300 volts. All of the energy needed to flash the lamp is stored in a bulk capacitor called a photoflash capacitor. Once the lamp is triggered, all of the energy stored in the photoflash capacitor is discharged through the flash tube to produce light. The stored energy in the photoflash capacitor is provided by a specialized boost converter that charges the photoflash capacitor up to 300 V from a much lower battery input voltage. In the past, this converter was built of bulky discrete components that were difficult to incorporate into the space available in small devices such as a camera.

Texas Instruments' TPS65552A photoflash charger IC is a highly integrated photoflash charger that greatly simplifies and reduces the size of the photoflash charger circuit. Figure 1 shows a photoflash capacitor charger based on this device. The TPS65552A provides all the necessary charging controls,

Featured in the latest on-line issue

- Understanding and comparing datasheets for high-speed ADCs
- Powering today's multi-rail FPGAs and DSPs, Part 1
- TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)
- Practical considerations when designing a power supply with the TPS6211x
- High-speed notch filters
- Download your copy now at www.ti.com/aaj



output feedback, charge completion status, IGBT gate driver and circuit protections necessary to implement a small, efficient photoflash charger.

The TPS65552A is based on a flyback topology. The output voltage is sensed during the off period of the internal switch, at which time the output voltage is reflected back to the input through the transformer. This eliminates the need for a bulky, high-voltage feedback network on the output and also provides electrical isolation from the input to the output. Once the output voltage reaches its target value, the TPS65552A will automatically stop charging and an open collector output goes low, thus signaling a 'ready to flash' condition. This output can drive a status-indicating LED or an input to a microcontroller.

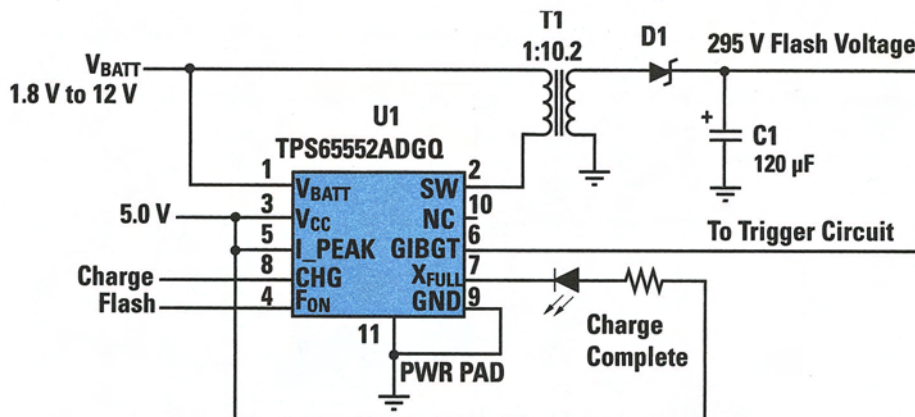


Figure 1 – TPS65552A photoflash charger

The I_PEAK pin of the TPS65552A controls the peak current that flows through the primary of the flyback transformer, T1, during each switch cycle. To adjust the capacitor charging time, the primary current can be dynamically adjusted from 0.9 amps to 1.8 amps by changing the voltage applied to the I_PEAK pin. This feature allows a microcontroller to dynamically control the current draw

The TPS65552A has an integrated high-current buffer to drive the gate of an IGBT used in the trigger circuit. The IGBT can be driven on and off during flashes to support functions such as red-eye reduction or Evaluated Through The Lens (E-TTL) flash modes.

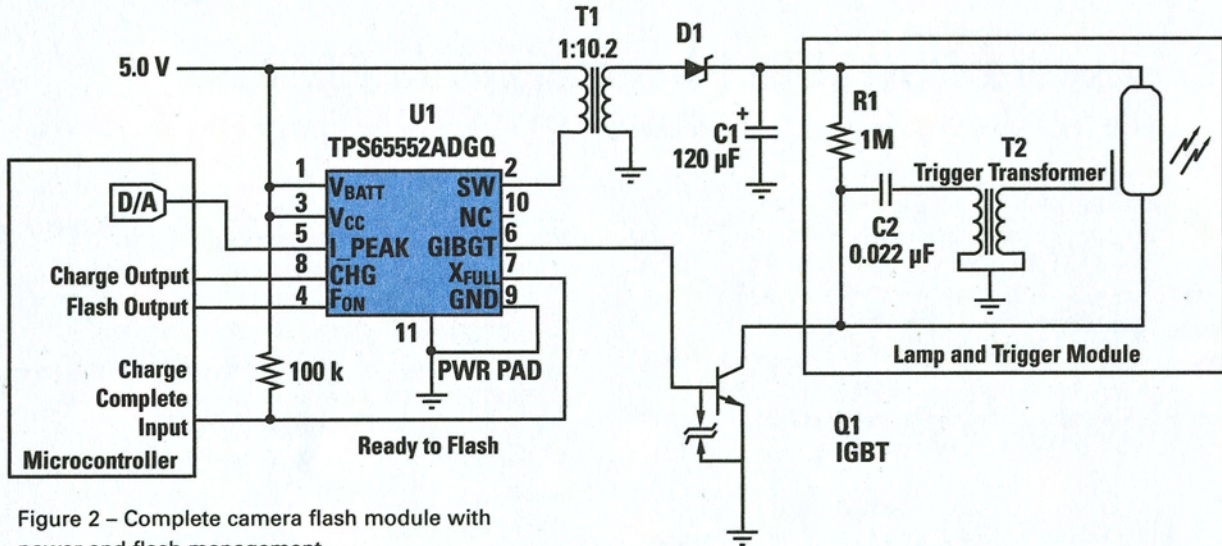


Figure 2 – Complete camera flash module with power and flash management

of the charger for power management. For example, in a digital still camera, a microcontroller can reduce the charger current when a high-current zoom motor is operating so that both can function at the same time and not exceed the maximum current capability of the camera's battery. This feature can also be used to extend battery run time. Reducing the peak currents during charging reduces the average current consumption so that a weak battery, with diminished current capability, can still charge the photoflash capacitor.

Historically, the flash has been triggered with a pushbutton switch or a Silicon-Controlled Rectifier (SCR). However, newer flash modes such as red-eye reduction use multiple bursts of the Xenon lamp. The lamp is triggered for a short flash that does not fully discharge the photoflash capacitor. Then, after a short delay, the lamp is retriggered for the main flash. The pushbutton and SCR cannot reliably start and stop the lamp mid-flash. The Insulated Gate Bipolar Transistor (IGBT) is capable of handling the currents, which are typically 150 amps during a flash. However, like a MOSFET, the gate of the IGBT requires a large current pulse in order to quickly turn on. Therefore, a high-current driver is required to drive the gate of the IGBT.

Device	RefDes	Description	MFR
330 FW 120A	C1	Capacitor, Aluminum, 120-uF, 330-VDC, ±20%	Rubycon
C3216X7R2J223KT	C2	Capacitor, Ceramic, 0.022-uF, 630-V, X7R, 10%	TDK
ES1G	D1	Diode, Rectifier, 1-A, 400-V	Diodes Inc.
36FT050	FL1	Flash Tube, 400v Max	Xicon
SSM25G45EM	Q1	Trans, NChan Insulated-Gate Bipolar, 450V, 150A	Silicon Standard
CTX16-17360	T1	Transformer, Flyback, 1:10.2	Coiltronics
422-2304	T2	Transformer, Trigger	Xicon

Reference:

1. TPS65552 Datasheet (SLVS567)