

3.3V converter delivers 3W from Li-ion battery

David Salerno, Unitrode Corp, Merrimack, NH

Lithium-ion batteries are rapidly gaining popularity in portable applications because of their superior energy density, low self-discharge rate, and high cell voltage. When you use one Li-ion battery to power a 3.3V dc/dc converter; however, you encounter a problem, because the battery

voltage can be higher or lower than 3.3V. When fully charged, a Li-ion cell has approximately 4.2V output; when fully discharged, the voltage is approximately 2.5V. Therefore, you cannot use a simple buck or boost topology with a single inductor to generate a regulated 3.3V output. Some designs

boost the voltage to approximately 4.3V and then use a low-dropout regulator to produce the 3.3V. This approach is inefficient, and efficiency is a crucial consideration in battery-powered applications. The circuit in **Figure 1** offers a solution to the problem.

The circuit works by referencing the

