

**Figure 2** Output voltage for the circuit in Figure 1 varies with output current.


which is also the node from which current is delivered to the load.

The circuit converts a  $-5.2\text{V}$  supply voltage to  $-3.6\text{V}$ . The boost converter,  $\text{IC}_1$ , regulates its output voltage to maintain its feedback voltage at  $-3.95\text{V}$ — $1.25\text{V}$  above  $-5.2\text{V}$ . Resistor  $R_8$  and capacitor  $C_8$  form a low-pass filter that stabilizes the voltage at FB. You must then select the  $R_4/R_6$  and  $R_5/R_7$  pairs to produce the desired out-

put voltage. Making  $R_4$  and  $R_5$  equal and making  $R_6$  and  $R_7$  equal improves the common-mode performance. The ratio of  $R_4$  to  $R_5$  determines the voltage level at the positive input of op amp  $\text{IC}_2$ , whose closed-loop configuration ensures that the same voltage appears at its negative input. Knowing  $\text{IC}_2$ 's output voltage,  $-3.95\text{V}$ , and its negative input voltage lets you determine the output voltage using the values of

$R_6$  and  $R_7$ :  $V_{\text{OUT}} = -V_{\text{REF}}(R_6/R_7)$ , where  $V_{\text{REF}}$  is the  $1.25\text{V}$  nominal reference voltage of  $\text{IC}_1$ ,  $R_4 = R_6$ , and  $R_5 = R_7$ .

The component values in **Figure 1**—for example,  $1.96\text{ k}\Omega$  for  $R_5$  and  $R_7$  and  $5.76\text{ k}\Omega$  for  $R_4$  and  $R_6$ —produce an output voltage of  $-3.76\text{V}$ . Graphs of output voltage versus output current (**Figure 2**) and efficiency versus output current (**Figure 3**) illustrate this circuit's performance. **EDN**

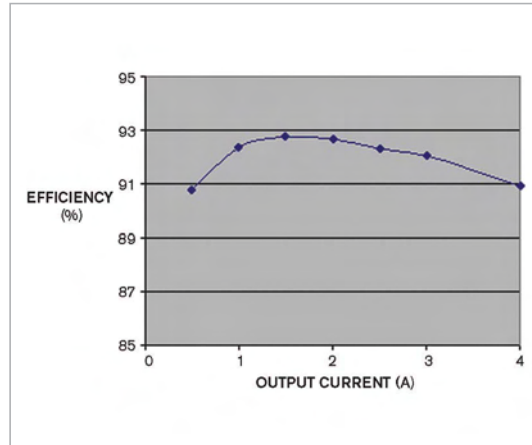

**Figure 3** Conversion efficiency for the circuit in Figure 1 varies with output current.