

EDITED BY BILL TRAVIS &amp; ANNE WATSON SWAGER

# Step-up/step-down converter takes 2 to 16V inputs

LUCIANO BORDOGNA AND LUCA VASALLI, MAXIM INTEGRATED PRODUCTS, MILAN, ITALY


The circuit in Figure 1 is a low-cost step-up/step-down dc/dc converter. By definition, its input can range above and below the regulated voltage. The circuit includes a simple switch-

mode boost converter ( $IC_1$ ) that contains a comparator normally used to detect low battery voltage. In this case, the comparator controls an external pnp transistor that operates as a linear regulator.  $IC_1$  steps up  $V_{IN}$  (2V minimum) to the level of  $V_X$ , as determined by the jumper block,  $J_1$ .

A 2-3 jumper selects the internal divider, producing  $V_X=12V$ . A 2-1 jumper selects feedback resistors  $R_1$  and  $R_2$ , producing  $V_X = 1.5V(R_1+R_2)/R_2$ . You should set  $V_X$  to 1 to 2V above the desired output voltage. The  $Q_1$  linear regulator steps  $V_X$  down to an output level determined by  $R_3$  and  $R_4$ :  $V_{OUT} = 1.5V(R_3+R_4)/R_4$ , where  $V_X > V_{OUT}$ . When  $V_{IN} > V_X$ , the switching regulator turns off, and the linear regulator alone controls  $V_{OUT}$ .  $C_6$  reduces output ripple. The circuit accommodates a wide range of input and output voltages and supplies output currents as high as 500 mA (Figure 2). (DI #2218) EDN

To Vote For This Design, Circle No. 418

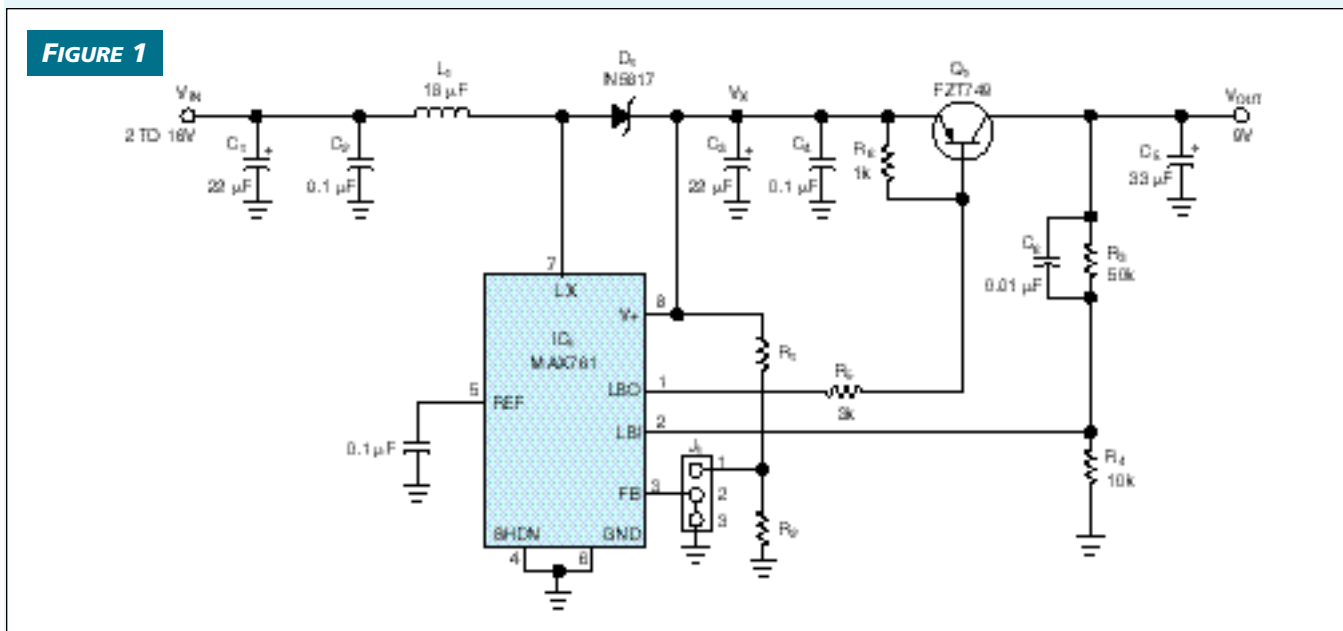Delivering more than 100 mA over its 2 to 16V useful input-voltage range, the regulator in Figure 1 provides 500 mA over an 8 to 13V range.



Toggleing between switching and linear operation, this regulator operates with input voltages above and below the desired output voltage.