

Pulsing charge pump drives capacitive loads

Paul J Rose, Mental Automation Inc, Bellevue, WA

The test circuit in **Figure 1** efficiently drives various capacitive loads, such as memory cells and simple capacitors, so that you can observe their leakage effects. Essentially, the circuit is a pulsed and variable current source acting as a charge pump. A pulsed voltage source drives a one-shot oscillator. This one-shot drives two MOSFET switches that convert the 10V rail-to-rail output of the oscillator to the desired rail-to-rail voltage drive—in this case, 15V—for the controlled current mirror with the same voltage-switching polarity. The current mirror

drives the variable load.

R_1 and C_1 determine the timing pulses that IC1's one-shot oscillator produces. When IC1's output is high, Q_1 is on, and Q_2 is off. The floating drain of Q_2 causes the emitter and base of Q_3 to have the same potential, so that Q_3 is off. Then, the pnp current mirror of Q_4 and Q_5 turns on to drive the variable load of R_2 and C_2 high. R_3 controls the charge rate of the load. As you make R_3 smaller, the current mirror provides more current to the load to charge it up faster, as required for testing.

When the output of the one-shot is low,

Q_1 is off, and Q_2 is on. In this case, the drain of Q_2 is at ground potential, and the base of Q_3 is at a lower potential than its emitter so that Q_3 turns on. Current through Q_3 flows through R_3 , causing a voltage rise at the bases of Q_4 and Q_5 , which turns them off. Turning off Q_4 and Q_5 disconnects the variable load from its power supply so that the load is free to bleed stored charge through R_2 .

This pulsing charge pump has three unique features: It can generate various pulse widths, the variable resistor in the coupled-collector circuit of the pnp cur-

