

---

## **It's easy to connect dc supplies in parallel**


by Shri D. Bhanumurty

*Defense Electronics Research Laboratory, Hyderabad, India*

---

Connecting the outputs of two direct-current power supplies in parallel is not as complicated as one might think. Moreover, the supplies may even have different voltage or current capabilities.

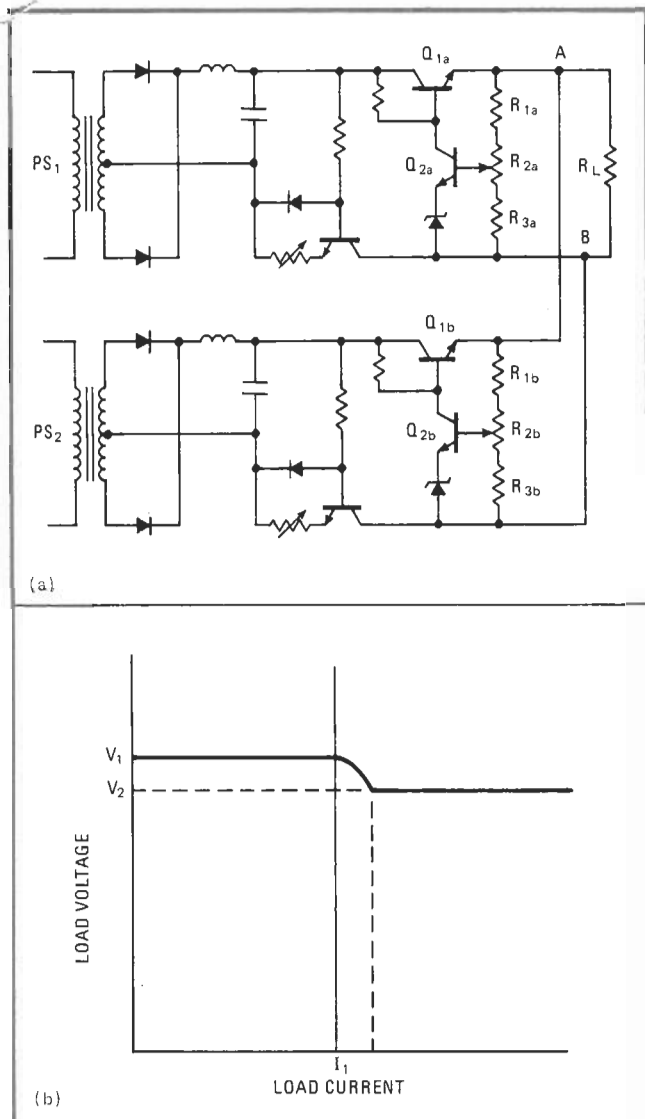The only criterion for parallel operation is that both sources be current-limited. Any such circuit can provide load currents up to the set limits of one supply. The second unit supplies any needed additional current at its rated output voltage, once it determines that the limits of




**1. Current takeover.** Parallel connection of dc supplies for shared current duties is permissible if both have current-limiting networks (a). Current to load is supplied solely by PS<sub>1</sub> until limit I<sub>1</sub> is reached. Then PS<sub>2</sub> supplies additional current needed at voltage V<sub>2</sub>(b).

the first source have been reached.

The outputs of two power sources PS<sub>1</sub> and PS<sub>2</sub> are connected as shown in Fig. 1a. They are set at voltages V<sub>1</sub> and V<sub>2</sub> and current limits I<sub>1</sub> and I<sub>2</sub>, respectively, where V<sub>1</sub> is slightly greater than V<sub>2</sub> at all times.

Under no-load conditions and until the set current limits of PS<sub>1</sub> are reached, the load voltage will be V<sub>1</sub>. This is easily explained. Suppose that because of a power-line voltage increase V<sub>2</sub> temporarily increases. The increase in output voltage will be detected by the current-sensing resistors R<sub>1b</sub> through R<sub>3b</sub>. Transistor Q<sub>2b</sub> will be biased more heavily into the conducting region and will bias Q<sub>1b</sub> into the back-biased region. Thus, a greater voltage drop will appear across Q<sub>1b</sub> than before. The output voltage will drop slightly, but will still be above V<sub>2</sub>, at V<sub>2</sub> + δ. This δ voltage is the result of compensation for the increase in input voltage at PS<sub>2</sub>; however, PS<sub>2</sub> will supply very little current to the load.

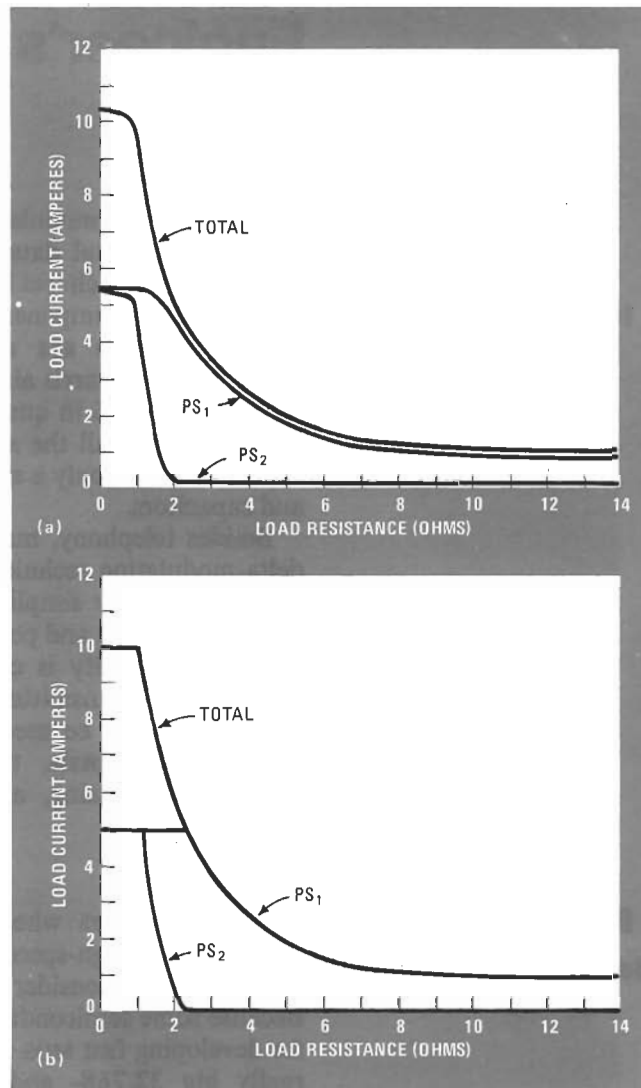As long as the current drawn by the load does not



**2. Supply characteristic.** If two 10-volt, 5-ampere supplies with 0.1% regulation are connected and placed in operation, the curve in (a) results. PS<sub>2</sub> begins heavy turn-on as PS<sub>1</sub> approaches 5 V. Curves of ideal power supplies connected in parallel (b) show that PS<sub>2</sub> turns on at precise moment the current limit of PS<sub>1</sub> has been reached.

exceed I<sub>1</sub>, the voltage across the load will be V<sub>1</sub>, and PS<sub>1</sub> will supply all the current. If the current demanded by the load should exceed I<sub>1</sub>, the voltage will drop to V<sub>2</sub>. R<sub>1b</sub> through R<sub>3b</sub> will detect this drop, back-biasing Q<sub>2b</sub> and forward-biasing Q<sub>1b</sub>. Thus PS<sub>2</sub> will contribute the additional current demanded by the load (Fig. 1b).

When two dc supplies conduct in parallel, the result is a system characteristic of the kind shown in Fig. 2a, which is a plot of load resistance to load current. Both supplies can deliver 10 volts at 5 amperes, and each has a regulation of 0.1%. PS<sub>1</sub> is set at 10 v, PS<sub>2</sub> to 9.99 v.

Compare Fig. 2a and Fig. 2b, where a plot of load resistance to load current has been made for two ideal supplies. As one may deduce from these plots, a nonideal PS<sub>2</sub> will begin to contribute current to the load before the PS<sub>1</sub> limits have been reached. □

Engineer's notebook is a regular feature in *Electronics*. We invite readers to submit original design shortcuts, calculation aids, measurement and test techniques, and other ideas for saving engineering time or cost. We'll pay \$50 for each item published.