

led me to develop the most elementary circuitry to fulfill the concept. When current is passed through the 2.5-volt winding a current will be induced into the 120-volt winding (now the secondary). After rectifying and filtering, the dc voltage is used to actuate the 24-volt dc relay. The variable resistor, R, can be adjusted to allow various ac currents to pass before the relay will trip and open the ac circuit.

This will not completely suffice, however, since the relay will buzz back and forth between on and off unless some form of lock-up is provided. The added components, shown by dotted lines, attend to this function. Lock-up is obtained with lower current than is required for pull-in, and simple half-wave rectification will serve. Reset is furnished by opening the switch, which is normally closed.

The system that finally evolved is shown in Fig. 2. The full-wave bridge rectifier furnished more voltage than the original half-wave circuit and allows the relay to trip out at a lower current. In a thorough search for a relay of better suitabilities, over a dozen relays were checked out experimentally. Finally, it was decided to opt for a relatively sensitive unit which has the added advantage of having three sets of contacts, all rated at 10 Amperes. To be on the safe side, these are wired in parallel.

My thoughts then were directed to the feasibility of obtaining a suitable variable resistor, in order to enable the relay to actuate at various current settings. Easier said than done!

The three principal calibrating resistors are used in place of a "nice to have" 3000-Ohm, 10-Watt wirewound potentiometer. The 5-Watt, 1000-Ohm size is a

fairly common item in all stores which cater to radio and TV servicemen. Additional resistors were added to cause the setup to kick out at 2.5, 5, and 10 Amperes. This 4-to-1 range is in line with what the commercial makers of such relays—Westinghouse for example—design into their products.

Other design factors worth mentioning are:

(a) The 100-uF electrolytic capacitor seems to be about right in this setup. A lower value may cause the dc relay to buzz, and a higher value can cause a time delay to take place—definitely undesirable in any form of protective circuitry where high power is involved; and (b) Avoid carbon resistors in the 1000-Ohm positions. Careful checks show that a 1000-Ohm, 2-Watt carbon resistor will be dissipating 1.6 Watts or 80% of its full value. This will cause upward change in the resistance, and, indirectly, "calibration creep" in the finished instrument.

Random thoughts at this juncture: Others have asked me whether simpler devices, such as the thermal overload units commonly found on the back of TV sets, would suffice. These have been tried and their use cannot be justified since the time delay is intolerable where an expensive unit requires protection. Personally, I almost lost a very nice Powerstat® while attempting to live with such protection.

Perhaps solid-state devices might be designed to furnish the same function? I would be disinclined to depend upon such a setup in view of the relatively high-voltage spikes which are encountered when a highly inductive component—such as the power transformer in a large amateur rig—needs to have its primary circuit interrupted. For that rea-

Parts List

T— 2.5-volt, 10-A filament transformer
 D— all diodes type 1N4007
 C— 100 μ F, 35 volts
 S1— Rotary switch with 3 positions
 S2— Momentary-contact switch, wired for normally-closed operation (Radio Shack 275-619)
 K— Potter & Brumfield type KUP 14D15 (Fair Radio Sales, Lima, Ohio, \$2.50)
 R1-R3— 1000 Ohms, 5-Watt, wirewound
 R4, R5— 330 Ohms, 1-Watt
 R6— 15k Ohms, 1-Watt
 R7— 2700 Ohms, 2-Watt
 Small cabinet or chassis, 3-wire ac cord, and 5-way output terminals

son, I chose 1000-volt silicon diodes, type 1N4007, for service in this unit.

So we have an ac overload relay which is simple, inexpensive, and dependable. Furthermore, it can be calibrated to kick out at several different amperages at the flick of a switch. I have yet to see such a simple item described in print, and I thought it would be nice to share this knowledge with other members of the amateur fraternity. So, why not try this out and

experiment at ease, without blowing box after box of fuses?

All of the foregoing calibrations were obtained with ac loads consisting of non-inductive heater coils. If your circuit to be protected is highly reactive, you may find the relay kickout points to be slightly different. ■

Reference

1. "Son of the Overload Relay," *73 Magazine*, January, 1977, p. 140.



ANNOUNCING



RF PRODUCTS announces production of 5/8 wavelength VHF telescoping antennas for 144-148 MHz (2M), 152-174 MHz and 220-225 MHz (1 1/4 M). These new antennas are intended for use on hand-held and base station transceivers. They are available with BNC connector, 5/16-32 stud, or PL-259 connector. A telescoping brass nickel-plated nine section radiator is used for lighter weight and less RF junctions than previously available 5/8 wavelength antennas. Maximum gain is achieved by the combination of a base spring for whip protection and a tuned matching network for minimum VSWR. Minimum 2-meter bandwidth for 1.5:1 VSWR is 3.5 MHz. Overall length with BNC connector is 45 3/4 inches (1162mm). The BNC connector and 5/16-32 stud models are intended for hand-held transceiver (HTs) use and the PL-259 model which includes a type M359 right angle adaptor is intended for direct rear mounting on base station transceivers. Suggested list price for all models is \$19.95 the most popular of which are listed below.

P/N	DESCRIPTION	P/N	DESCRIPTION
191-200	2 M, 5/16-32 stud	191-800	1 1/4 M, 5/16-32 stud
191-214	2 M, BNC connector	191-814	1 1/4 M, BNC connector
191-219	2 M, PL-259 connector	191-819	1 1/4 M, PL-259 connector

ELECTRICAL SPECIFICATIONS

Gain(ref. 1/4 wave helical) 6db min.
 Bandwidth(2M), 1.5:1 VSWR 3.5MHz min.
 Bandwidth(1 1/4 M), 1.5:1 VSWR 5MHz min.
 Maximum power(HT models) 10 watts
 Maximum power(PL-259 model) 30 watts

MECHANICAL SPECIFICATIONS (with BNC)

Length extended(2M) 45 3/4" (1162mm)
 Length extended(1 1/4 M) 32 1/8" (815mm)
 Length collapsed(2M) 8 1/16" (207mm)
 Length collapsed(1 1/4 M) 7 7/8" (200mm)
 Weight 2.2oz/80g

SPECIALIZING IN PORTABLE, FIXED STATION AND TEST EQUIPMENT ANTENNAS
 Check or M.O. only, postage prepaid in continental U.S.
 Florida residents add 5% sales tax
 DEALER INQUIRES INVITED

RF PRODUCTS

P.O. BOX 33, ROCKLEDGE, FL.32955 (305) 631-0775