

# Shunt regulator provides overvoltage protection

ROBERT N BUONO, MAHWAH, NJ

The circuit in **Figure 1** uses a typical technique for varying the output voltage of a power supply via a programmable control voltage. Although the topology and schematic details of the power supply are not critical, the protection technique is novel.

The control IC is a UC3843AN PWM controller. This IC applies 2.5V to the noninverting input of an internal error amplifier but does not bring this input out to a pin (node B). The inverting input of the error amplifier is available at an external pin (node A). To regulate  $V_{OUT}$ , the control IC must maintain the voltage at Node A equal to the 2.5V at Node B. The component values in the **figure** allow the dc output voltage of the power supply to vary between a minimum of 5V and a maximum of 75V, as a function of  $V_{CONTROL}$ , which can vary from 0 to 3V (corresponding to a  $V_{OUT}$  of 5V and 75V, respectively).

In the absence of  $Q_1$ ,  $V_{OUT}$  and the voltage division of  $R_3$  and  $R_4$  determine the voltage at Node A. The circuit compares this voltage with the 2.5V at Node B. The power supply's output-voltage control loop keeps the voltage at Node A equal to Node B by appropriately controlling  $V_{OUT}$ .


The circuit provides programmability of  $V_{OUT}$  by sinking current from Node A.  $V_{OUT}$  must source any current that flows from this node. Also, the current must flow through  $R_3$ , which causes the voltage drop across  $R_3$  to increase.  $V_{OUT}$

is then always equal to the voltage drop across  $R_3$  plus a current set by  $V_{CONTROL}$ .  $IC_1$ 's op amp forces the voltage across  $R_2$  to equal the voltage at Pin 3 of  $IC_1$ .

The addition of just one component,  $IC_2$ , adds precise overvoltage protection to the variable-output power supply.  $IC_2$  is a low-voltage shunt regulator that incorporates an internal 1.24V precision reference. This low reference voltage allows you to use this protection circuit with conventional power-supply control ICs for which 2.5V is a common internal reference voltage. Under normal operating conditions (for output voltages between 5 and 75V),  $IC_2$  does nothing. The voltage at  $IC_2$ 's reference (Pin 1) is less than its internal 1.24V reference, so its cathode (Pin 3) draws no current. In this case,  $IC_1$  solely controls the voltage at the base of  $Q_1$ . For example, if  $V_{CONTROL}$  is 3V, then the voltage across  $R_2$  is 1.13V and  $V_{OUT}$  equals 75V. Note that, to simplify this example, the beta of  $Q_1$  is assumed to be infinite.

However, in the event of any kind of fault that might cause the voltage across  $R_2$  to rise above 1.24V (which corresponds to a maximum  $V_{OUT}$  of 81.7V), the shunt regulator begins to function. As the voltage at Pin 1 of  $IC_2$  begins to exceed the internal 1.24 reference voltage, the cathode of  $IC_2$  begins to conduct. The cathode of  $IC_2$  then pulls down on the base of  $Q_1$  to maintain 1.24V at Pin 1 of  $IC_2$ . As this happens,  $IC_2$  through  $Q_1$  controls the voltage across  $R_2$ . This con-

FIGURE 1

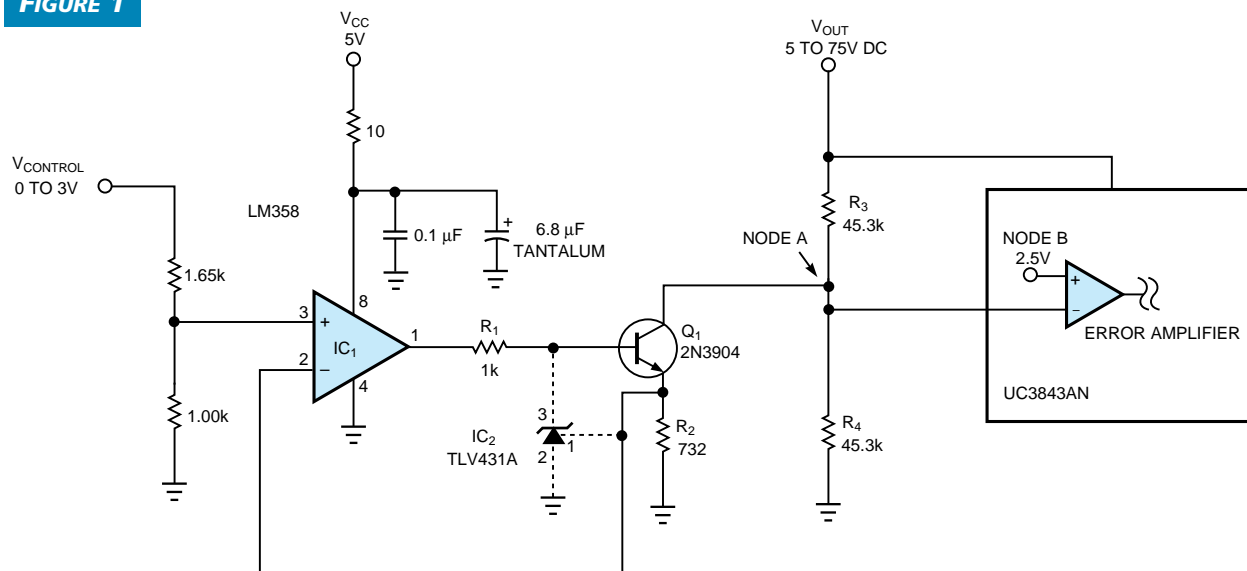

Adding one shunt regulator,  $IC_2$ , to an otherwise typical programmable power supply provides precise overvoltage protection.

trol causes the output of IC<sub>1</sub> to saturate at a positive voltage of approximately 3.7V because IC<sub>1</sub> can no longer keep the voltage across R<sub>2</sub> equal to the voltage at its input (Pin 3). The benefit to circuit operation is that IC<sub>2</sub> now operates with a constant-cathode current determined by the voltage across R<sub>1</sub>, which equals 3.7–1.8V/1kΩ=1.9 mA. This level of cathode current ensures that IC<sub>2</sub> regulates properly.

This protection circuit is immune to any potential failure

mode of IC<sub>1</sub>'s op amp or the programming voltage source, V<sub>CONTROL</sub>. IC<sub>1</sub> operates only from 5V. If its output (Pin 1) shorts to ground, the minimum V<sub>OUT</sub> results. If its output shorts to V<sub>CC</sub>, IC<sub>2</sub> sinks 5–1.8V/1 kΩ=3.2 mA, and V<sub>OUT</sub> clamps at the maximum of 81.7V. (DI #2146)



**To Vote For This Design, Circle No. 360**