

UPDATES

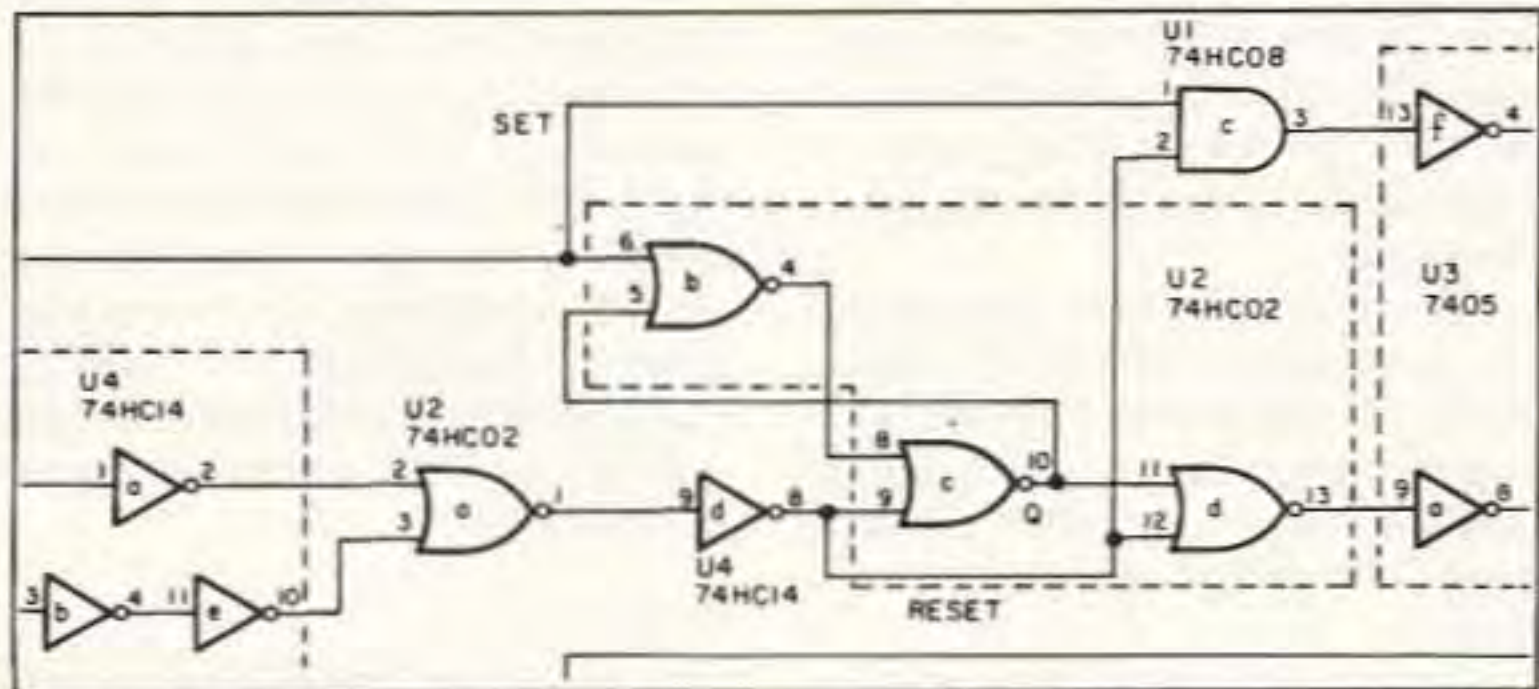


Figure. Partial schematic of the GaAsFET preamp sequencer showing new IC pin numbers corresponding to the PC board layout.

GaAsFET Preamp Sequencer

See the above article on page 8 of the March 1992 issue by Ron Klimas WZ1V. Although the schematic is cor-

rect as printed, if you build the circuit using the PC board the IC pin numbers will be different. See the Figure for a schematic that reflects the pin number changes on the PC board layout. **73**