



BUILD AN Autoranging Digital Capacitance Meter

BY DAVID H. DAGE

**Autoranges from 1 pF to 1 μF and from 1 μF to 4000 μF.
Updates readings automatically.**

THE DIGITAL-READOUT capacitance meter described here is a most useful instrument when one has to determine values of unmarked capacitors or those with unknown codes, or when checking the tolerances of marked components. Its autorange function greatly simplifies what would ordinarily be a measurement chore without this feature. Moreover, the meter's accuracy of over 1% (dependent on the tolerances of a few passive components) from 1 pF to 4000 μF enhances its utility. The project is easy on the budget, too, as low-cost 7400 series logic and 555 timer IC's are used throughout.

To operate, simply turn on the unit, connect a capacitor to the test terminals, and read the digital value displayed for any capacitor up to 1 μF. Switching a mode switch from nF to μF extends the autorange function to 4000 μF and beyond, limited only by the leakage characteristics of the test capacitor.

How it Works. Traditionally, capacitance has been measured on an ac bridge by balancing known components against the reactance of an unknown capacitance at a given, fixed frequency. However, instruments are now appearing which employ a different method to determine capacitance—they measure time. Here's how.

Mathematically, the voltage across a capacitor discharging through a resistor

in a simple RC network can be expressed by the equation:

$$V_C = V_0 (1 - e^{-t/RC})$$

where V_0 is the voltage across the capacitor when fully charged, R the resistance in ohms, C the capacitance in farads, t the time in seconds, and e the exponential constant or base for natural logarithms (approximately equal to 2.718). If we let a capacitor that has charged to a known voltage discharge through a fixed, stable resistance to some given voltage, the discharge time will be directly proportional to the component's capacitance, which then can be readily determined.


The meter described here employs this method of measurement, which readily lends itself to use with a digital readout and eliminates null adjustments. As shown in Fig. 1, the capacitance to be measured is charged through R_A and R_B . When the voltage across the capacitor equals V_{REF} , comparator A sets the flip-flop, turning on the transistor. The capacitor then discharges through R_A until the voltage across it drops to one-half V_{REF} . At this point, comparator B resets the flip-flop, which in turn cuts off the transistor. The capacitor then starts to charge up to V_{REF} , and the cycle is repeated.

A reference oscillator output at a fixed frequency is gated by the flip-flop output signal. The gated reference pulses are counted by a digital counter, decoded,

and displayed directly as capacitance. The two comparators, flip-flop, transistor, reference voltage sources, and an output driver are all contained in one package—the common 555 timer IC.

The meter's autorange circuit functions during a single capacitor discharge cycle. If the three-decade counter overflows, the reference frequency input is automatically divided by ten. Simultaneously, the decimal point in the digital display is shifted one position to the right. If necessary, the process is repeated once

Interior photo of prototype.

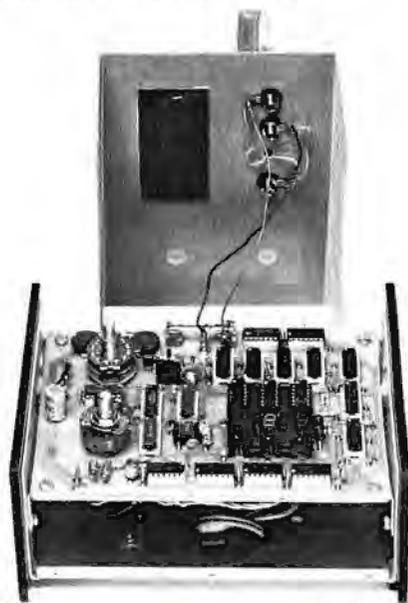

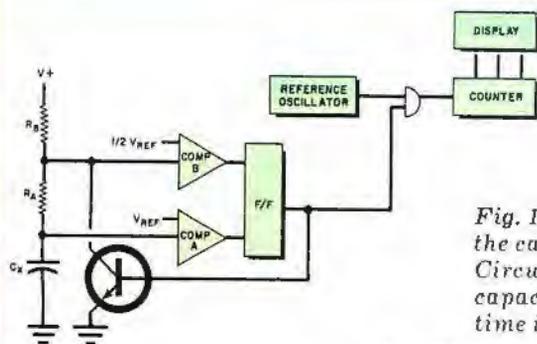


Fig. 1. Block diagram of the capacitance meter. Circuit determines unknown capacitance by measuring time it takes to discharge.

PARTS LIST

- C1—4000- μ F, 16-V electrolytic capacitor
 C2, C4, C8 through C16, C23—0.01- μ F disc ceramic capacitor
 C3—0.0033- μ F, 10% Mylar capacitor
 C5—0.1- μ F disc ceramic capacitor
 C6, C17—4.7- μ F, 16-volt tantalum capacitor
 C7—220- μ F, 16-volt electrolytic capacitor
 C18—0.01- μ F, 5% polystyrene capacitor
 C19—820-pF, 5% polystyrene capacitor
 C20—470-pF, 5% polystyrene capacitor
 C21—220-pF, 5% polystyrene capacitor
 C22—0.005- μ F, 10% Mylar capacitor
 D1, D2—1N4002 silicon diode
 D3 through D5—1N4154 or HEP R0600 silicon fast-recovery diode
 DIS1 through DIS3—DL707 common-anode, seven-segment LED display
 F1, F2— $\frac{1}{4}$ -ampere fast-blow fuse
 IC1, IC2, IC3, IC17, IC18, IC19—7490 decade counter
 IC4, IC15—7404 hex inverter
 IC5—74125 Tri-State quad buffer
 IC6, IC20—555 timer
 IC7, IC8, IC22—7400 quad Two-input NAND-gate
 IC9, IC10, IC11—7447 BCD to seven-segment decoder/driver
 IC12, IC13—7474 dual D edge-triggered flip-flop
 IC14, IC21—74121 monostable multivibrator
 IC16—7493 4-bit binary counter
 IC23—LM309K 5-volt regulator
 L1—13- μ H inductor
 LED1, LED2—20-mA light emitting diode
 R1—100,000-ohm pc mount trimmer potentiometer
 R2—1-megohm, 1% tolerance, 50 ppm/ $^{\circ}$ C metal film resistor

- R3—100-ohm pc mount trimmer potentiometer
 R4—1000-ohm, 1% tolerance, 50 ppm/ $^{\circ}$ C metal film resistor
 R10—25,000-ohm, panel mount linear taper potentiometer
 The following are $\frac{1}{4}$ -watt, 5% tolerance carbon composition resistors.
 R5—1000 ohms
 R6, R7—100,000 ohms
 R8, R9—1500 ohms
 R11, R12, R13—100 ohms
 R14, R15—3300 ohms
 R16 through R20—470 ohms
 R2:1, R1:2, R3:3, R5:4, R4:6, R7:5, R6:7 (one set for each of three decades)—330 ohms

- S1—3-pole, 3-position rotary switch
 T1—16-volt center-tapped transformer
 Misc.—Suitable enclosure, banana jacks or binding posts for C_X terminals, printed circuit board, fuseholders, knobs, hook-up wire, IC sockets or Molex Soldercons, hardware, solder, etc.

Note—The following items are available from Dage Scientific Instruments, Box 1054, Livermore, CA 94550: CM-6 complete kit of parts, including tested IC's, cabinet, hardware, miscellaneous items, calibration capacitor, and assembly manual, \$69.95 in U.S. and Canada. CM-68 partial kit includes etched and drilled double-sided pc board, 13- μ H inductor, polystyrene capacitors (C18 through C21), calibration capacitor, and assembly manual for \$20 in U.S. and Canada. U.S. residents add \$1 postage and handling, Canadians add \$2. Californians add sales tax.

or twice, resulting in four automatically selected ranges. Additional overflow pulses are displayed by two LED's located to the left of the display.

Circuit Details. Refer to the appropriate schematic (Figs. 2 through 6) for the following detailed circuit description. Free-running 555 timer IC20 (Fig. 2) is the basic capacitance measuring circuit, comprising the comparators, reference voltages, flip-flop, and discharge transistor described previously. The timer's discharge period is used to measure the component under test. When MODE switch S1 is in the nF position, the discharge period is determined by R1, R2, and C_X . In the μ F position, the interval is determined by R3, R4, and C_X .

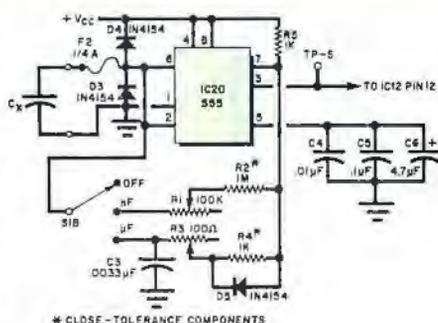


Fig. 2. Input stage has free-running 555 timer.

A second free-running 555 timer, IC6 (Fig. 3), is employed in an autocycling circuit which automatically updates the capacitance measurement. The reference frequency (about 1.4 MHz) is sup-

plied by a Colpitts oscillator made up of IC4, L1, and C18 through C21. Signals from the reference oscillator and timers IC6 and IC20 are combined by dual-D flip-flops IC12 and IC13. One half of IC12 synchronizes the output of IC20 with the 1.4-MHz reference frequency, providing dual-phase (Q and \bar{Q}) outputs. The other half of IC12 and IC13 select one discharge pulse from IC20 after the output of autocycle timer IC6 goes high. The flip-flops disable IC6 until the discharge pulse is completed.

The reference oscillator output is gated by IC7 so that it passes to the counting stages during one discharge period of C_X per measuring interval. Monostable multivibrator IC14, when triggered by

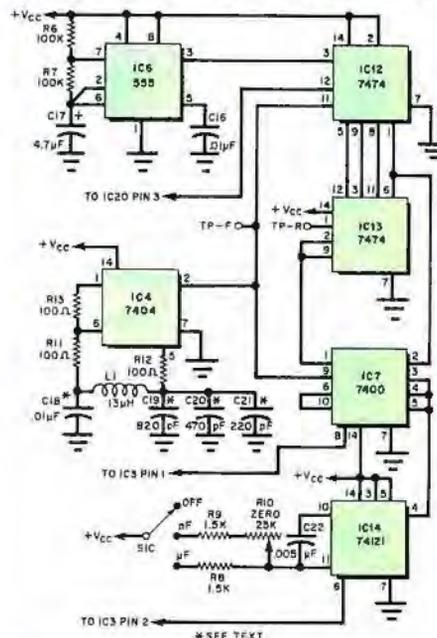


Fig. 3. Oscillator, sync, and reset circuits.

the leading edge of the synchronized discharge pulse, resets decade counters IC16 through IC19 and dividers IC1 through IC3. When S1 is in the nF position, the width of the reset pulse generated by IC14 is controlled by the setting of ZERO trimmer potentiometer R10. This allows the user to keep stray capacitance out of the measurement.

The gated reference signal is divided by decade counters IC1, IC2 and IC3. Output signals from these counters, at 1/1000th, 1/100th, and one-tenth the input frequency, are applied to Tri-State logic switch IC5 (Fig. 5), which passes the appropriate pulse train to decade counter IC19. Overflow pulses from this BCD decade counter are applied to Tri-State logic switch IC5 (Fig. 5), which passes the appropriate pulse train to decade counter IC18, whose overflow pulses in turn are counted by IC17. Binary coded decimal outputs from these three decade counters are decoded by IC9, IC10

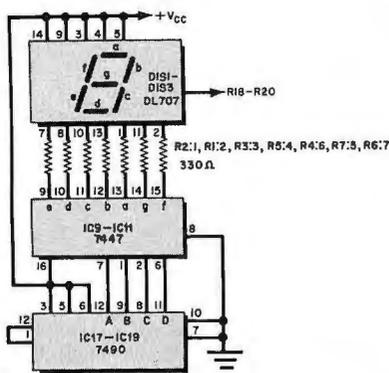


Fig. 4. Display and drivers.

and IC11 (Fig. 4), which also drive seven-segment displays DIS1, DIS2, and DIS3. Current limiting for each display is performed by resistors R2:1, R1:2, R3:3, R5:4, R4:6, R7:5, and R6:7. (This method of identifying the resistors is discussed in the Construction section of the article.)

Now we'll examine the capacitance meter's autorange circuitry (Fig. 5). Overflow pulses from the last BCD decade counter (IC17) are applied to 4-bit binary counter IC16. This IC has four weighted binary outputs, A, B, C, and D, which are inverted by IC15. Lines A, \bar{A} , B, and \bar{B} are decoded by the NAND gates in IC8 to provide control signals for the Tri-State logic switches in IC5 and selection of the proper display decimal point. Outputs C and \bar{C} either sink or block current from overrange indicators LED1 and LED2.

Assume that counters IC17 through IC19 have counted 999 pulses and the display reads ".999." Upon receipt of the next pulse, the decimal point is shifted one position to the right and the display reads "0.00." Tri-State switch IC5 then passes the $\div 10$ reference output of IC3 to decade counters IC17 through IC19. One-shot IC21 and IC22 then produce a pulse which advances the most significant counter and (leftmost) display by one so that the displays now read "1.00." If necessary, this process is repeated once or twice, resulting in an autorange function of 1000:1. After the third counting sequence, the overflow pulses cycle the two overrange LED's to indicate a count of 1000 pulses.

The 7400 series IC's require +5 volts, which is provided by the project's power supply (Fig. 6). Transformer T1 re-

duces the line voltage to a convenient value. The low-voltage ac is rectified by D1 and D2 into pulsating dc and smoothed by C1. A regulated dc output at +5 volts is provided by IC23. Although the regulator IC can provide a 1-ampere output, the capacitance meter circuitry requires only about 700 mA.

Construction. For the most part, the circuit is not critical and any assembly technique can be used to reproduce it. However, the measuring circuit comprising IC20 and its associated components is critical, and should be properly shielded and decoupled from the other stages. Etching and drilling and parts placement guides for a suitable printed circuit board are shown in Figs. 7 and 8.

The pc board holds all components of

feed-through pads are accessible to the sides of the sockets. Molex Soldercons present no problem, as they can be soldered on both sides of the board. The 42 feedthrough points are identified by circles on the component placement guide (Fig. 8).

Sockets or Molex Soldercons are mandatory for the LED displays and decoder/drivers. By cutting a socket lengthwise or using Molex Soldercons on the outside pin rows, as shown in Fig. 9A, a trough is provided under the displays and decoder/drivers into which the current-limiting resistors are placed. Numbering the holes from the center both up and down will allow quick resistor placement. For example, the leads of R2:1 occupy the second hole up and the first hole down. (See Fig. 9B.) Use small, 1/4-

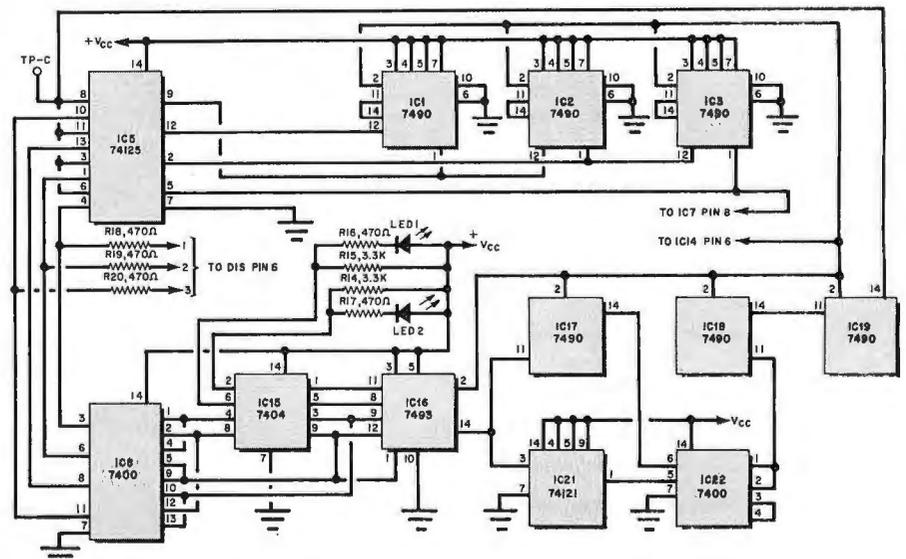


Fig. 5. Schematic of meter's autorange circuit.

the capacitance meter, less those in the power supply. It is a double-sided board on which many connections must be made between the top and bottom foil patterns. If you cannot make plated through holes, you must use wire feed-throughs to make the necessary connections. Component leads must be soldered on both sides of the board when pads are available.

Sockets or Molex Soldercons should be used to hold the integrated circuit and display packages. However, it is impossible to solder leads to pads on the component side of the board when they are under an IC socket. Because of this, all

watt resistors and, where necessary, insulate leads with sleeving.

The critical components on the board are L1, C18 through C21, which determine the frequency of the reference oscillator, and R1 through R4 which with IC20 form the basic capacitance measuring circuit.

High-quality polystyrene capacitors and metal-film fixed resistors with temperature coefficients of less than 50 ppm/°C should be used. These components, together with IC20, will determine the long-term accuracy of the meter and measurement error as a function of temperature. If high-quality components are used and the meter is properly calibrated, its accuracy will be at least 1% at room temperature.

Checkout and Calibration. A properly functioning unit will respond as follows, and should then be calibrated. Rotate R1, R3, and R10 fully counterclock-

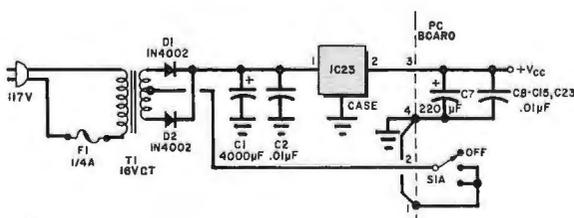


Fig. 6. Power supply circuit has a voltage regulator IC.

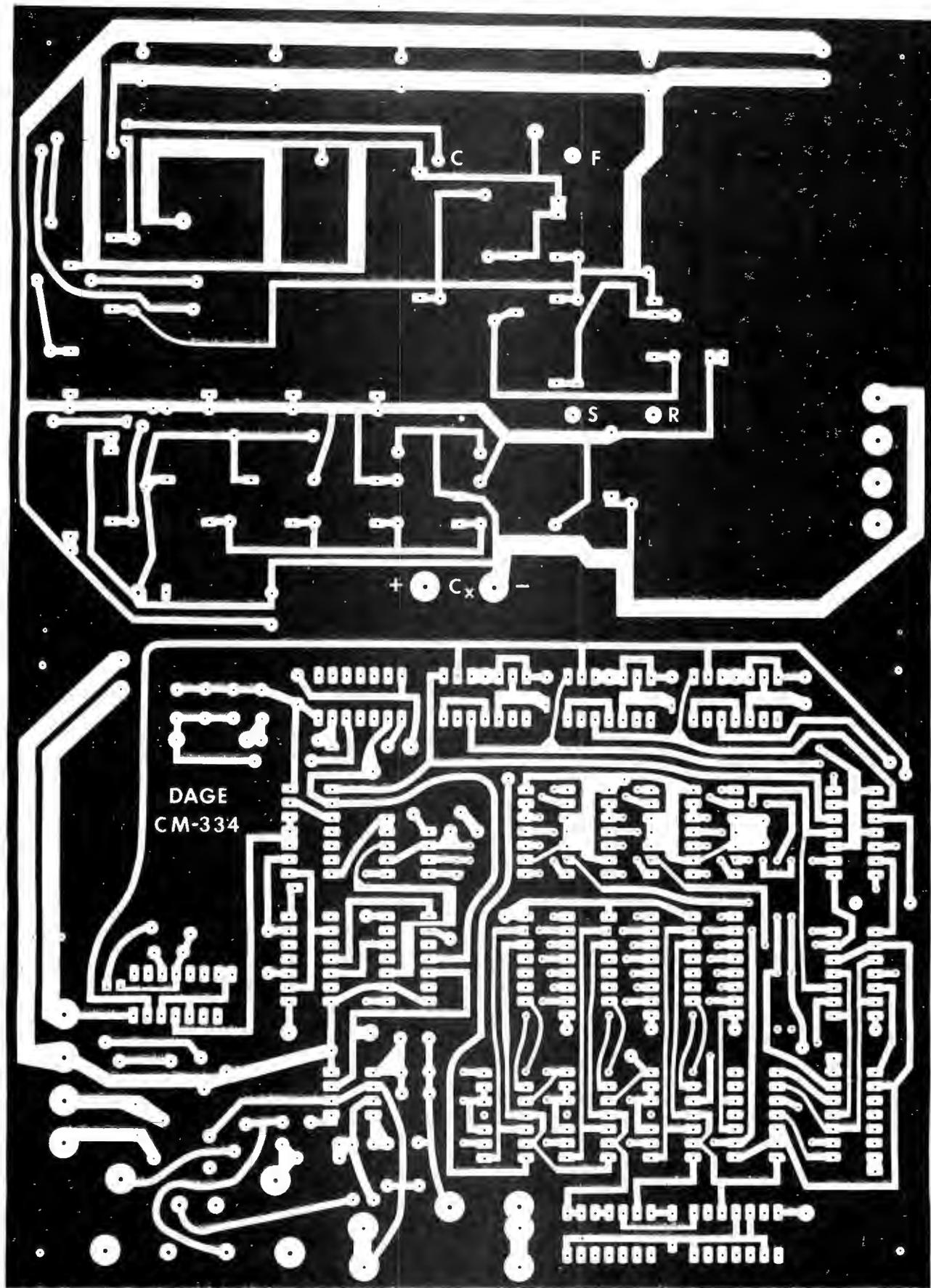


Fig. 7. Actual-size etching and drilling guides for the double-sided pc board.

wise, set *S1* to the *nF* position and apply power to the project. The display will light and within 2 seconds will reset to ".000." Rotate *ZERO* potentiometer *R10* fully clockwise. The display will indicate

a few picofarads (.003 to .030 nF). Slowly rotate the *ZERO* potentiometer counterclockwise until the display reads ".001." Rotate the control slightly counterclockwise until it reads ".000."

Connect a reference capacitor with a known value of 0.68- μ F to the *C_X* terminals of the meter. The display will count up for about one-half second and stop at some value which is not critical at this

time. Place $S1$ in the μF position. The display will read a similar value, but will not appear to flicker. Finally, place a 5000-to-8000- μF capacitor across the C_X terminals. Within a few seconds, the display will advance and the overrange LED's will cycle top on only, bottom on only, both on, both off, and repeat the sequence. The meter is now ready for calibration.

The most direct method of calibration is to measure a reference capacitor whose value is about 0.7 μF . A precision capacitor will be very expensive, so if you have access to a precision (0.1% or better) capacitance bridge, measure the value of a good-quality Mylar capacitor on it. If the capacitor is used at approximately the same temperature as the bridge environment, it will be a suitable reference component.

The 0.7- μF capacitor will be used as a reference for both the nF and μF switch positions. Setting one point for each position is all that is required, as absolute linearity is provided by the project circuitry. The reference oscillator's mean output frequency is designed to be slightly high when only $C18$ and $C19$ are included in the circuit. If trimmer potentiometers $R1$ and $R3$ cannot be adjusted to bring the display reading into agreement with the value of the reference component, install $C20$ and/or $C21$. Calibration is now a matter of merely connecting the reference capacitor to the C_X terminals, placing $S1$ in the μF position, and adjusting $R3$ until the display

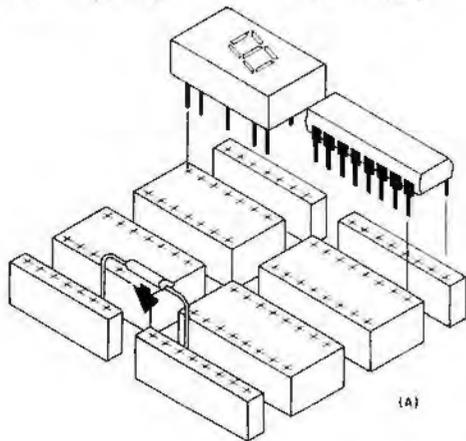


Fig. 9. A trough is provided for the current-limiting resistors as shown in (A). Diagram at (B) shows how numbering the holes allows quick resistor placement.

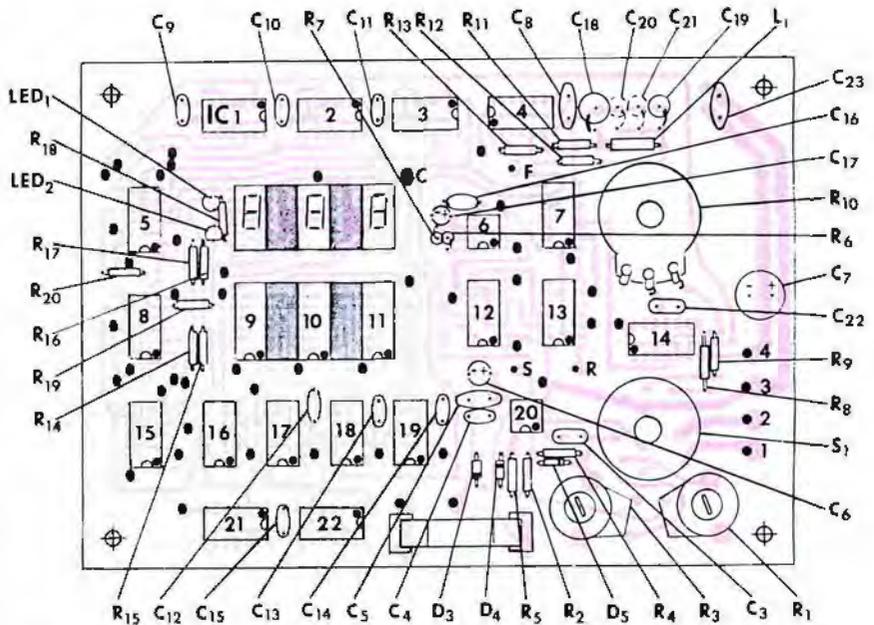
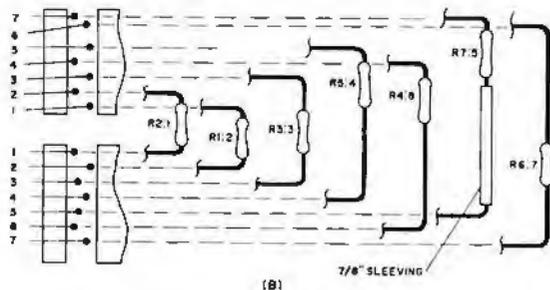


Fig. 8. Component placement guide. Numbered circles are feedthroughs.

matches the value of the reference component. Then, $S1$ should be placed in the nF position and $R1$ adjusted for the same displayed capacitance.

Using the Meter. Apply power to the project by placing $S1$ in the nF position. Zero the display by slowly rotating the shaft of $R10$ counterclockwise until the display reads, ".001," advancing the control slightly more until a ".000" reading is obtained. Once zeroed, no further adjustments are necessary. The μF position does not require zeroing.

Connect the capacitor to be measured across the C_X terminals. Polarized capacitors must be oriented positive to positive, negative to negative. Do not connect charged capacitors to the project. Although the input circuitry is protected with clamping diodes and a fuse, charged capacitors might damage the project.

Capacitance is displayed in either nF or μF , depending on the setting of $S1$. Values greater than 1000 nF should be read in the μF position. Capacitance greater than 1000 μF is determined by observing the overrange LED's to the left of the display. Because these two LED's cycle every $\frac{2}{3}$ second, they are easily observed. If the top LED glows, 1000 μF is indicated; if the bottom LED glows, 2000 μF ; if both, 3000 μF .

This sequence will then repeat, with two dark LED's representing 4000 μF ; the top LED glowing, 5000 μF ; the bottom LED, 6000 μF ; both on, 7000 μF ; both dark, 8000 μF ; and so on until the cycling stops. Values up to several thousand microfarads can be measured. The upper limit is determined mainly by capacitor leakage, and to a lesser extent by your patience! Capacitors, with high leakage will never charge to V_{REF} , and thus will not trigger the discharge cycle.

When using the capacitance meter with $S1$ in the nF position, treat the reading as if it were in picofarads if the decimal point is to the left. That is, ".084" should be read as 84 pF, and ".003" as 3 pF. With a little experience, you will quickly become familiar with the auto-range function and the behavior of the overrange LED's.