

designideas

READERS SOLVE DESIGN PROBLEMS

Simple fixture statically tests programmable-gain amplifiers

Marián Štofka, Slovak University of Technology, Bratislava, Slovakia

The advent of instrumentation amplifiers with digital gain switching offers obvious advantages, such as board-space saving, higher reliability because of fewer solder joints, and lower total cost. These valuable features stem from the fact that the gain-setting networks are integral parts of the monolithic ICs. This feature makes these IC amplifiers much less sensitive to stray electromagnetic fields because the area of internal resistors is a negligible fraction of the previously used discrete gain-setting resis-

tors. Moreover, the value of the relative permittivity of the plastic package and that of the silicon chip are higher than that of the air. As a consequence, the field strength of the electrical component of any stray field penetrating into the chip is lower than that in the surroundings.

Because the gain-setting circuitry is inaccessible directly, a digitally gain-programmable amplifier is a black box. However, the simple fixture in Figure 1 can help to evaluate some of the static characteristics of these ICs. The fix-

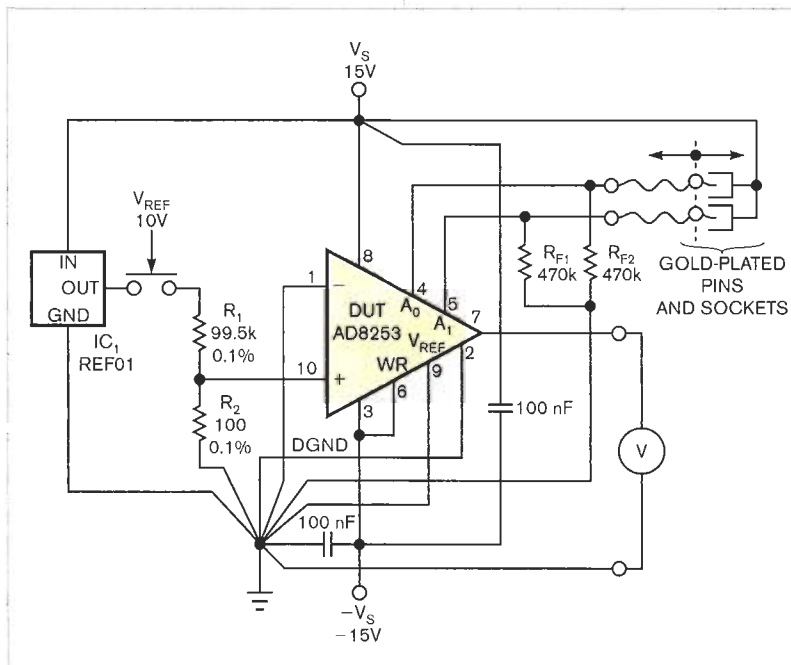


Figure 1 Comprising a handful of components, this circuit allows you to perform your own, independent testing of basic static properties of digitally gain-programmable amplifiers.

DIs Inside

80 Control system uses LabView and a PC's parallel port

84 General-purpose components implement USB-based data-acquisition system

88 Small, simple, high-voltage supply features single IC

90 CMOS DACs act as digitally controlled voltage dividers

► What are your design problems and solutions? Publish them here and receive \$150! Send your Design Ideas to edndesignideas@reedbusiness.com.

ture comprises Analog Devices' (www.analog.com) 10V REF01 voltage-reference cell, IC₁, the elderly but still excellent industry standard, and a high-precision fixed resistive divider. These components provide a millivolt-range output voltage.

Multiplying the ratio of the resistive divider by the maximum voltage gain of the tested programmable-gain amplifier should give a value of one. The circuit uses tablet-type film resistors having tolerances of 0.1% maximum, yielding a voltage of 10.02 mV at the output of the divider. The two gain-setting logic inputs of the DUT (device under test), an Analog Devices AD8253, connect to short-stranded conductors, which gold-plated pins terminate. Resistors R_{F1} and R_{F2} force the logic level at gain-programming inputs A₀ and A₁ to be low when you disconnect these pins. To set a high level on either or both pins, insert them into the gold-plated counterparts. Two such counterparts interconnect mechanically and elec-

trically and remain at the V_s potential. The DUT uses all permutations of the binary values at A_0 and A_1 logic (Reference 1). The corresponding voltage gains are one, 10, 100, and 1000.

The evaluation procedure involves measuring the output voltage of the DUT with resistor R_1 both connecting to and disconnecting from the output of IC_1 . Thus, you obtain an output voltage of the gain times 10.02 mV and 0V for all voltage gains. The 0V output voltage has a nonzero value because of the input-voltage offset; this voltage might seem high at first glance. However, any fraction of a millivolt of the input-volt-

age offset times a gain of 1000 yields a fraction of a volt at the output.

When you calculate the differences of the 10.02-mV and 0V output voltages for the respective values of gain, you get a pleasant surprise: These values differ from the ideal values of 10.02 mV times the gain by less than 0.05%. Using this test, you can confirm the precision of the laser-trimmed gain settings. The relatively low value of R_2 ensures that the additional input-offset error arising from input bias current of the DUT has a value of less than 3 μ V, whereas the typical value is 0.5 μ V. Because proper grounding

is an absolute necessity when dealing with tens-of-millivolts scale and high-voltage gains, you must connect supply grounds, digital ground, and other rough grounds with the fine signal grounds in one common junction. **Figure 1** illustrates this approach by using unusual slanted lines for grounding leads. **EDN**

REFERENCE

1 "AD8253 10 MHz, 20V/ μ s, G=1, 10, 100, 1000 iCMOS Programmable Gain Instrumentation Amplifier," Analog Devices, www.analog.com/pr/AD8253.