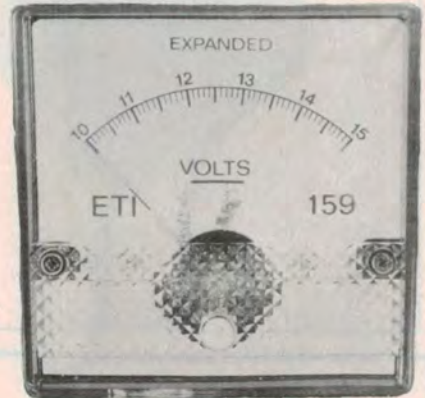


# Expanded scale voltmeter covering the 10 - 15 V range

A simple, low-cost instrument that can be built into power supplies or used as a portable or fixed 'battery condition' monitoring meter.

**Simon Campbell**  
**Roger Harrison**



COMMON STORAGE BATTERIES to power nominal 12 Vdc electrical systems have a terminal voltage that ranges from a little over 10 volts when discharged to around 15 volts when fully charged, the operating voltage being somewhere in the range 11.5 V to 13.8 V. Lead-acid batteries, for example, may have a terminal voltage under rated discharge that commences at around 14.2 V and drops to about 11.8 V. A 12 V (nominal) nickel-cadmium battery may typically have a terminal voltage under rated discharge that starts at 13 volts, dropping to 11 volts when discharged.

Equipment designed to operate from a nominal 12 Vdc supply may only deliver its specified performance at a supply voltage of 13.8 V — mobile CB and amateur transceivers being a case in point. Other dc operated equipment may perform properly at 12.5 V but 'complain' when the supply reaches 14.5 V.

To monitor the state of charge/discharge of a battery, a battery-operated system or the output of power supplies, chargers, etc, a voltmeter which can be easily read to 100 mV over the range of interest, i.e: 10 to 15 volts, is an invaluable asset. This project does just that.

Some readers may note that our Expanded-scale LED Voltmeter, Project ETI-316, published in the September 1980 issue, does much the same job. However, the function of each is somewhat different. The ETI-316 has 10 LEDs indicating each half volt between 10.5 V and 15 V and is intended to be read 'at a glance', giving a general


indication of battery condition or whatever. Its main application is in vehicles or other areas where operation is only checked periodically.

This instrument, being of the true analogue type, is intended for more exacting measurement and is better characterised as a test instrument.
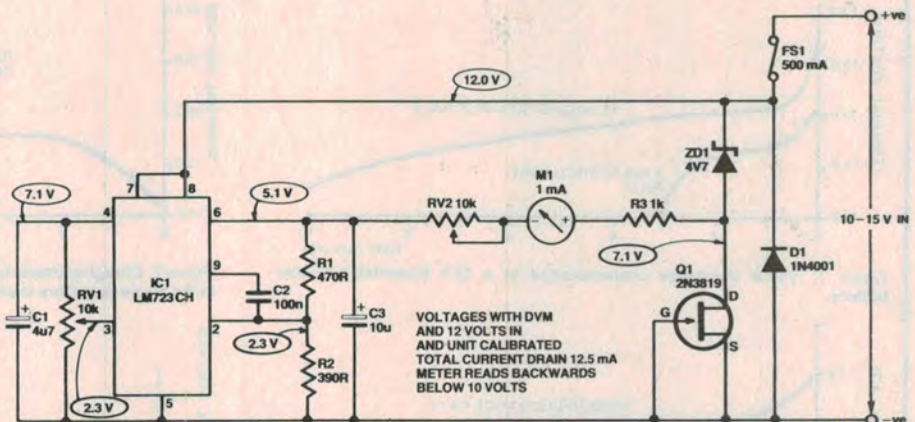
## The circuit

We originally came across this circuit in an article by Danny Apted (then VK7ZDA) published in 'QRM', the newsletter of the Northern Branch of the Wireless Institute of Australia, Tasmanian Division.

An LM723 variable voltage regulator IC is employed to set an accurate 'offset' voltage of 5 V, and the meter (M1) plus the trimpot RV2 and R3 make up a 5 V meter, with the trimpot allowing calibration. The negative terminal of the meter is connected to the output of the



## HOW IT WORKS — ETI 159


The meter, M1, is a 1 mA meter with series resistance — made up of R3 and RV2 — so that it becomes a 0-5 V voltmeter. The negative end of the meter is maintained at 5 V above the circuit negative line by the output of IC1, a 723 adjustable regulator. The positive end of the meter is connected to the circuit positive line via ZD1, a 4V7 zener diode. Thus, no 'forward' current will flow in the meter until the voltage between the circuit negative line and the circuit positive line is greater than  $5 + 4.7 = 9.7$  volts.

Bias current for the zener is provided by a FET, Q1, connected as a constant current source so that the zener current is accurately maintained over the range of circuit input voltage. This ensures the zener voltage remains essentially constant so that meter reading accuracy is maintained.

The trimpot RV1 sets the output voltage of the 723. This determines the lower scale voltage. Trimpot RV2 sets the meter scale range. More resistance increases the scale range, less resistance decreases it.

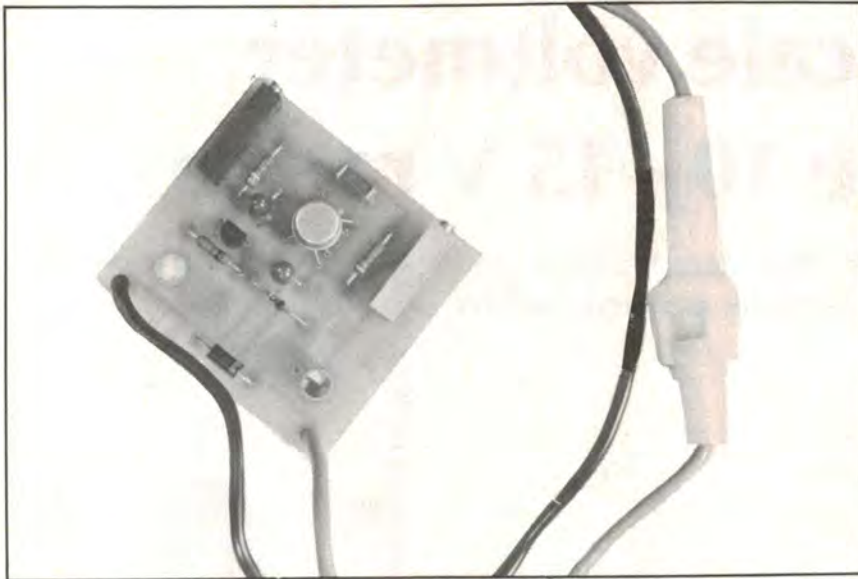Diode D1 protects the circuit against damage from reverse connection.





723 so that it is always held at 5 V 'above' the circuit negative line. The positive end of the meter goes to a zener which will not conduct until more than 5 V appears between the circuit +ve and -ve lines. Thus the meter will not have forward current flowing through it until the voltage between the circuit +ve and -ve rails is greater than 10 V, and will read full scale when it reaches 15 V (after RV2 is set correctly).

The meter scale limits may be adjusted by setting the output of the 723 higher or lower (adjusted by RV1) and setting RV2 so that the meter has an increased or decreased full-scale deflection range.

A variety of meter makes and sizes may be used.

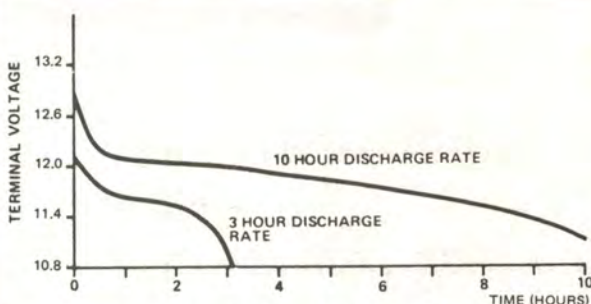


Figure 1. Typical discharge characteristics of a 12 V (nominal) lead-acid battery.

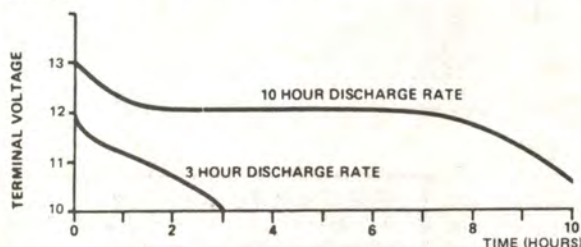


Figure 3. Typical discharge characteristics of a 12 V (nom.) nickel-cadmium battery (usually consisting of 10 cells in series).

### Battery condition and terminal voltage

The 12V battery, in its many forms, is a pretty well universal source of mobile or portable electric power. There are lead-acid wet cell types, lead-acid gel electrolyte (sealed) types, sealed and vented nickel cadmium types, and so on. They are to be found in cars, trucks, tractors, portable lighting plants, receivers, transceivers, aircraft, electric fences and microwave relay stations — to name but a few areas.

No matter what the application, the occasion arises when you need to reliably determine the battery's condition — its state of charge, or discharge. With wet cell lead-acid types, the specific gravity of the electrolyte is one reliable indicator. However, it gets a bit confusing as the recommended electrolyte can have a different S.G. depending on the intended use. For example, a low duty lead-acid battery intended for lighting applications may have a recommended electrolyte S.G. of 1.210, while a heavy-duty truck or tractor battery may have a recommended electrolyte S.G. of 1.275. Car batteries generally have a recommended S.G. of 1.260.

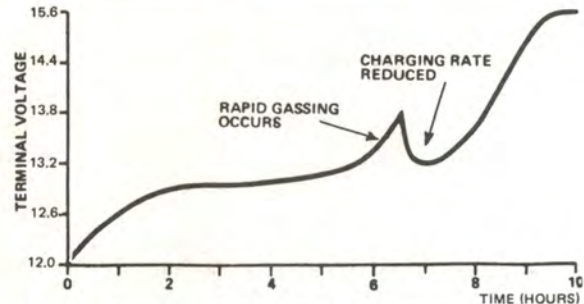


Figure 2. Charging characteristics of a 12 V (nom.) lead-acid battery. The 'kink' in the curve near 6 hrs is explained in the text.

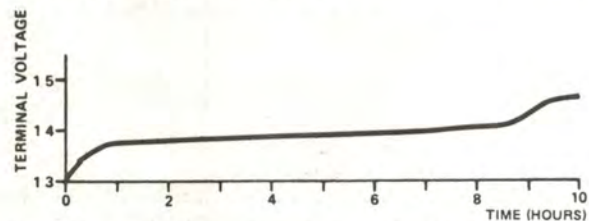


Figure 4. Typical charging characteristics of a 12 V NiCad battery (10 cells) charged with a constant current at one-tenth rated capacity (0.1C).

That's all very well for common wet cell batteries, but measuring the electrolyte S.G. of sealed lead-acid or nickel-cadmium batteries is out of the question.

With NiCads, the electrolyte doesn't change during charge or discharge.


Fortunately, the terminal voltage is a good indicator of the state of charge or discharge. In general, the terminal voltage of a battery will be at a defined minimum when discharged (generally between 10 and 11 volts), and rise to a defined maximum when fully charged (generally around 15 volts). Under load, the terminal voltage will vary between these limits, depending on the battery's condition.

Hence a voltmeter having a scale 'spread' to read between these two extremes is a very good and useful indicator of battery condition. It's a lot less messy and more convenient than wielding a hydrometer to measure specific gravity of the electrolyte!

The charge and discharge characteristics of typical lead-acid and sealed NiCad batteries are given in the accompanying figures.



# 10-15 V meter

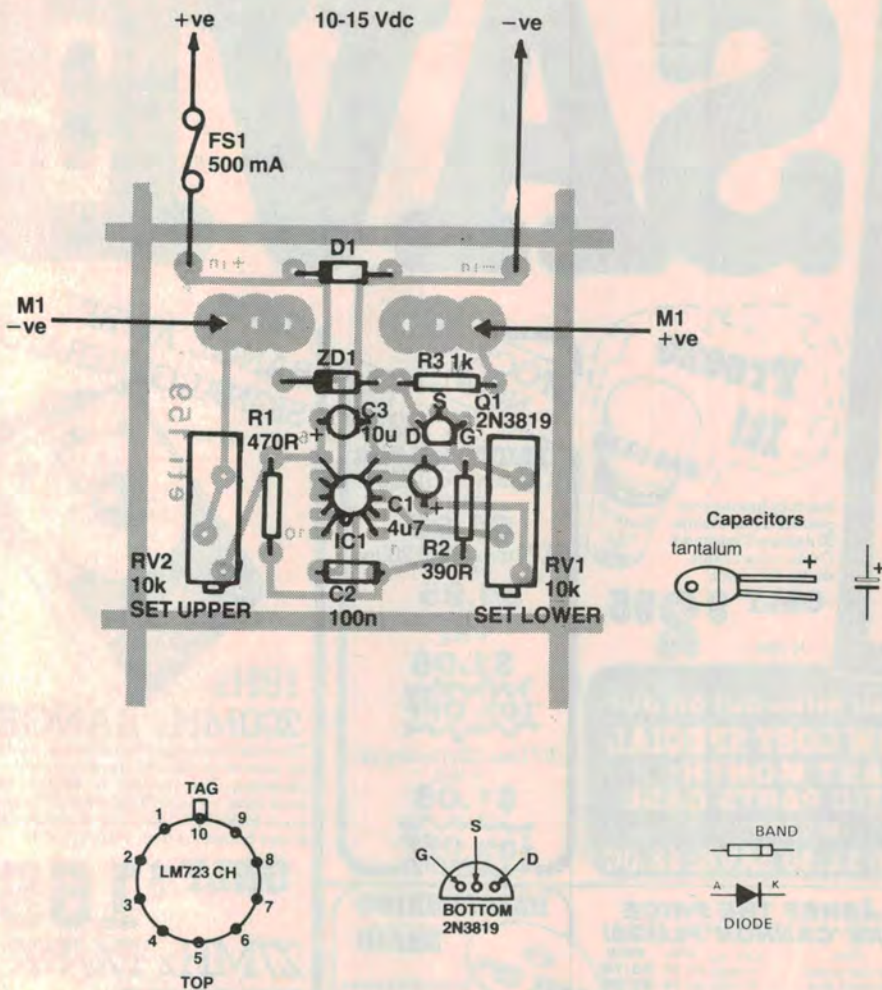

## PARTS LIST — ETI 159

**Resistors** ..... all ½W, 2% metal film  
 R1 ..... 470R  
 R2 ..... 390R  
 R3 ..... 1k  
 RV1, RV2 ..... 10k cermet multiturn horizontal trimpot

**Capacitors**  
 C1 ..... 4u7/10 V tant.  
 C2 ..... 100n greencap or ceramic  
 C3 ..... 10u/10 V tant.

**Semiconductors**  
 IC1 ..... LM723CH  
 ZD1 ..... 4V7, 400 mW or 1 W zener  
 Q1 ..... 2N3819  
 D1 ..... 1N4002 or similar

**Miscellaneous**  
 M1 ..... 1 mA meter (see text)  
 FS1 ..... 500 mA fuse and in-line fuse holder  
 ETI-159 pc board; meter scale to suit meter; colour-coded (red & black) 'figure-8' cable, etc.

## Price estimate

We estimate the cost of purchasing all the components for this project will be in the range:

**\$20—\$23**

Note that this is an **estimate** only and **not** a recommended price. A variety of factors may affect the price of a project, such as — quality of components purchased, type of pc board (fibre-glass or phenolic base), type of front panel supplied (if used), etc — whether bought as separate components or made up as a kit.

The pc board and meter scale artwork are on page 147.

## Construction

Mechanical construction of this project has been arranged so that the pc board can be accommodated on the rear of any of the commonly available moving coil meter movements. We chose a meter with a 55 mm wide scale (overall panel width, 82mm). A meter movement with a large scale is an advantage as it is considerably easier, and more accurate, to read than meters with a smaller scale. It also pays to buy a 'Class 2' meter (2% fsd accuracy) for best accuracy.

Having chosen your meter, drill out the pc board to suit the meter terminal spacing first. The components may then be assembled to the board in any particular order that suits you. Watch the orientation of the 723, ZD1, the FET and particularly D1. The latter is an 'idiot diode'. That is, if you have a lapse of concentration or forethought and connect your project backwards across a battery, the fuse will blow and not the project. Fuses are generally found to be cheaper than this project!

Seat all the components right down on the pc board as the board may be positioned on the rear of the meter with the components facing the meter. The size of C2 may give you a little trouble. Greencaps are generally too large and therefore unsuitable. We used a 'Monobloc' type capacitor — as commonly used on computer pc boards as bypasses. Alternatively, a 100n tantalum capacitor (+ve to pin 2 of IC1) may be used. The actual value or type of capacitor is not all that critical.

We have used multiturn trim pots for RV1 and RV2 as they make the setting up a whole lot easier.

Note that the fuse (to protect the project) is inserted in an in-line holder in the external connecting leads. For these leads we used 'automotive' figure-8 cable, colour-coded red (for +ve) and black (for -ve).

## Calibration

For this you will need a variable power supply covering 10 to 15 volts and a digital multimeter (borrow one for the

occasion).

First set the 10 V point. Connect the digital multimeter across the power supply output and adjust the power supply to obtain 10.00 volts. Set the mechanical zero on the meter movement to zero the meter's pointer. Connect the unit to the power supply output and adjust RV1 to zero the meter needle.

Next, set the power supply to obtain 15.00 V. Now adjust RV2 so that the meter needle sits on 15 V (full scale). Check the meter reading with the power supply output set at various voltages across the range. We were able to obtain readings across the full scale within ± half a scale reading (±50 mV). With a Class 2 meter the worst error may be about ± one scale division.

When set up, our unit drew 12.5 mA maximum current drain, which is probably typical, but current drain may be around 20 mA or so maximum. Note that, when the input voltage is below 10 V, the meter needle will move in the reverse direction. ●