

# Make a low-cost benchtop power meter

JIM TODSEN, BURR-BROWN CORP, TUCSON, AZ

With a few inexpensive ICs and passive components, you can easily make a multirange power meter suitable for use on your benchtop. The circuit in **Figure 1** measures currents from microamps to amps and voltages as high as 100V. The voltage at  $V_{OUT}$ , which you can monitor with a DVM, indicates the load's power. Two 9V batteries can run the circuit ( $\pm V = \pm 9V$ ), which has a current drain of 10 mA.

The circuit performs an analog multiplication of current and voltage to calculate the power. The load that you want to measure connects between +OUT and -OUT. The supply to the load connects between +IN and -IN. The PGA amplifier (IC<sub>1</sub>) produces a voltage proportional to the load current ( $I_{LOAD}$ ) sensed across  $R_{SENSE}$ , which sits on the ground side of the supply.  $R_1$ ,  $R_2$ , and IC<sub>3D</sub> generate a scaled version of the load voltage equal to  $V_{LOAD}/20$ . The output of IC<sub>1</sub> and  $V_{LOAD}/20$  are the inputs to IC<sub>2</sub>'s precision analog multiplier. IC<sub>2</sub> has a built-in scale factor of  $1/10$ .  $R_4$ ,  $R_5$ , and  $R_6$  provide additional gain. A

**TABLE 1—POWER METER RANGES AND SETTINGS**

$S_0$	$S_1$	PGA GAIN	$I_{MAX}$	$V_{MAX}$	$P_{MAX}$	$V_{OUT}$ scale
Open	Open	1000	10 mA	100V	50 mW	10 mW/V
Closed	Open	100	100 mA	100V	500 mW	100 mW/V
Open	Closed	10	1A	100V	5W	1W/V
Closed	Closed	1	10A (see note)	100V	50W	10W/V

NOTE:  $I_{MAX}$  may be lower, depending on the rating of  $R_{SENSE}$ .

lowpass filter at the output helps reduce noise and provides protection to IC<sub>2</sub> in case  $V_{OUT}$  accidentally shorts to ground. Combining all the scaling factors gives

$$V_{OUT} = (I_{LOAD} R_{SENSE}) \left( \frac{R_2}{R_1 + R_2} \right) \text{PGA}_{GAIN} \left( \frac{1}{10} \right) \left( \frac{R_6 + R_4}{R_5} \right) = I_{LOAD} V_{LOAD} \frac{\text{PGA}_{GAIN}}{10}$$

The circuit works equally well for positive and negative

load currents and voltages. If the load is producing rather than dissipating power,  $V_{OUT}$  reads negative. The scale of  $V_{OUT}$  is the same for positive and negative power readings. **Table 1** shows the ranges.

The maximum load-current setting ( $I_{MAX}$ ) limits the output of  $IC_1$  to 5V to meet head-room requirements when using 9V supplies.  $D_1$  through  $D_5$ ,  $R_3$ , and an LED provide a positive-current-overload warning. When the LED turns on, you should decrease the PGA's gain. A similar string of diodes with opposite polarity can monitor negative-current overloads. Make sure  $R_{SENSE}$  has a sufficient rating to handle the maximum current you use. Also, remember that for high  $I_{LOAD}$ , there is a significant voltage drop across  $R_{SENSE}$ .


The maximum load voltage ( $V_{MAX}$ ) of this circuit is 100V, limiting the voltage at  $IC_2$ 's input to 5V. You can adjust the ratio of  $R_1$  and  $R_2$  for a different  $V_{MAX}$ . Keep the sizes of  $R_1$  and  $R_2$  large to minimize current through them. Their currents add to  $I_{LOAD}$  and cause an error in the power reading.  $IC_{3D}$  prevents  $IC_2$ 's input-bias current from flowing through  $R_1$  and  $R_2$ . The maximum power ( $P_{MAX}$ ) setting limits  $IC_2$ 's output to 5V.

$IC_{3A}$  through  $IC_{3C}$ ,  $IC_{4A}$  and  $IC_{4B}$  and potentiometers  $R_7$  through  $R_{10}$  provide offset cancellation.  $R_6$  provides gain calibration. The circuit must remove various offsets and gain

errors to achieve the best accuracy, which is better than 1/2% of full-scale over most of the ranges. If lower accuracy is acceptable, you can remove some or all of the offset cancellation circuitry. To fully calibrate the circuit:

1. Short the load (place a short between +OUT and -OUT) with  $V_{IN}=0$ . Adjust  $R_{10}$  until  $V_{OUT}=0$ , which nulls the offset of the output of  $IC_2$ .
2. Remove the short, set  $PGA=1$ , and apply a large  $V_{IN}$  with no load. Adjust  $R_7$  until  $V_{OUT}=0$ , which nulls the offset of the  $I_{LOAD}$  input to  $IC_2$ .
3. Set  $PGA=1000$  and continue applying  $V_{IN}$  with no load. Adjust  $R_8$  until  $V_{OUT}=0$ , which nulls the offset of the front end of  $IC_1$ . If the PGA gain remains the same,  $R_8$  is unnecessary because  $R_7$  cancels the offset.
4. Short the load. Apply  $V_{IN}$ , and increase  $I_{LOAD}$  until the LED starts to turn on. (For  $PGA=1000$ ,  $I_{LOAD}$  is 10 mA to turn on LED.) Adjust  $R_9$  until  $V_{OUT}=0$ , which nulls the offset of the  $V_{LOAD}$  input to  $IC_2$ .
5. Finally, calibrate the gain. Set the  $PGA=100$ , the load=2k, and  $V_{LOAD}=25V$ . Adjust  $R_6$  until  $V_{OUT}$  matches the calculated power. (DI #2250)  $\epsilon$

To Vote For This Design, Circle No. 377

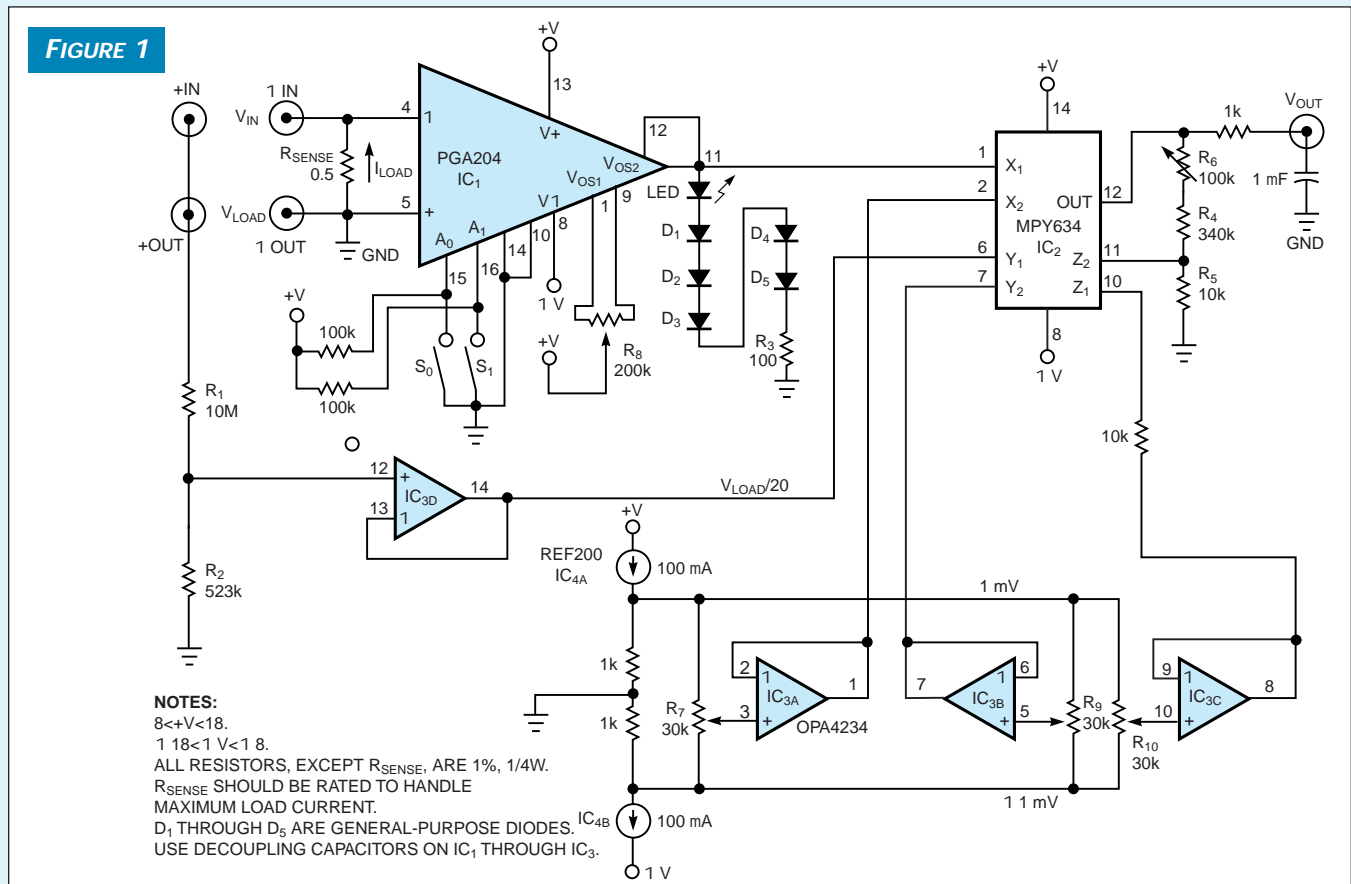

A programmable-gain amplifier, an analog multiplier, and a handful of other active and passive components implement a benchtop, multirange power meter.