

Two-chip ammeter measures currents down to picoamperes

by Douglas Modlin
Electrical Engineering Department, Stanford University, Stanford, Calif.

An ammeter circuit that can measure currents ranging from picoamperes to amperes may be built with two operational amplifiers, one having a low input bias current and offset voltage and the second having a high output-current capability. The accuracy of the meter is within 1%.

The basic configuration of the circuit (a) establishes A_1 as a field-effect-transistor input device that is internally compensated and A_2 as the power stage. The feedback arrangement of the circuit is technically possible but not practical because A_2 's gain-bandwidth product is much less than that of A_1 . This factor is due to A_2 's high-output capacity. As a consequence, the circuit is unstable and oscillates near the unity-gain crossover point of A_2 , because of a phase-shift around the feedback loop exceeding 360° .


Converting A_1 into an integrating comparator (b) stabilizes the circuit, thereby increasing the op amp's response time without introducing an additional phase shift to the feedback loop. Input current I_{in} flowing to the noninverting terminal of A_1 produces a positive voltage at its output and across integrating capacitor C_1 . A_2 , serving as an inverting, unity-gain amplifier, then raises its output to a voltage that causes I_f to equal I_{in} .

As a result, the output voltage corresponding to this input current is $V_o = I_{in}R_f$. The circuit accuracy is determined strictly by the tolerance of R_f . The input offset voltage of A_1 (1 millivolt maximum) and its correspondingly low offset current (0.15 picoampere maximum) have virtually no adverse effect on circuit accuracy. As for A_2 's output offset voltage, which is a maximum of 6 mV, it is canceled in the feedback loop. In order to maintain a virtual short at its input, A_1 develops a voltage across C_1 . When this voltage is applied to A_2 through R_2 , A_2 's offset voltage is canceled. This cancellation effect is independent of the second stage gain given by $A = -R_3/R_2$.

Feedback resistor R_f sets the cur-

rent range. To measure currents in the region of 1 pA for display on a $3\frac{1}{2}$ -digit digital voltmeter (resolution is 1 mV), R_f should be 10^9 ohms and be proportionally lower for higher currents. The circuit's input port A_1 , should be protected against leakage currents by Teflon stand-offs or otherwise be guarded. This measure also holds true for mounting the selectable resistor R_f .

The picovoltmeter in (c) is much the same as in (b), but is configured as a low-input bias current, low-offset buffer amplifier whose gain is established by $A = R_3/R_2$. This circuit takes advantage of the best features of both op amps but suppresses their limitations. Including resistor R_o in the circuit will stabilize the amplifier for capacitive loads. Incidentally, the LH0041 allows a user to select current limiting. The circuits discussed are not limited to the op amps listed in the figures. Any device with similar characteristics may be used. □

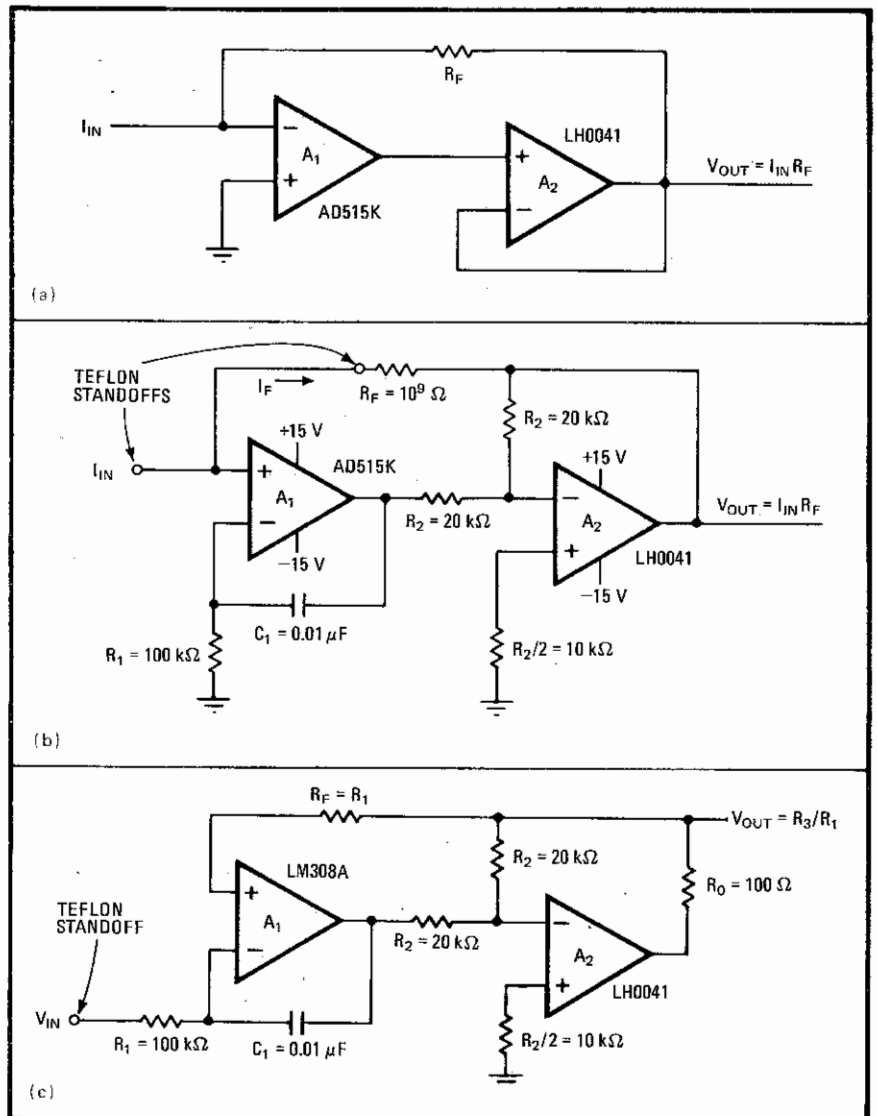

Infinitesimal. This ammeter, using one op amp having a low offset and another with a high-output driver, measures current from 1 pA to 1 A. Feedback resistor R_f determines the range of measurement. Based on the rudimentary circuit of (a), ammeter (b) is self-compensating and stable, providing accuracy to within 1%. Test currents are converted to corresponding voltage for display by $3\frac{1}{2}$ -digit digital voltmeter. A version for measuring low potentials (c) is similar. The LH0041 op amp allows users to select current limiting.