
64 Precision VOM Calibrator

□ Until now, most of the calibrator circuits appearing in hobby magazines could not be considered as primary reference standards. Instead, they were **transfer standards**, since the builder would be instructed to align his calibrator using a voltage reference of known accuracy. The obvious reaction of most readers was: "If I had

access to an accurate voltage reference to begin with, why would I want to build this calibrator?"

Our sentiments exactly. Now National Semiconductor comes to the rescue with a voltage reference IC, the LM185, having an output of 1.235 volts 1%. What's more, this voltage remains stable in the face of changing ambient

temperature and supply current.

The circuit diagrammed here produces six useful reference voltages from .100 V to 10.0 V. As noted above, the 1.235-volt output is accurate to within 1%. All of the other outputs are accurate to within 2% except for the 3-volt output, which has a tolerance of 4%. Reduced accuracy on all derived outputs is the result of errors introduced by the 1% resistor tolerances. Bear in mind,

however, that worst-case accuracies are quoted here.

Be certain that the input resistance of the instrument being calibrated greatly exceeds the resistance at the circuit node being read. Most of you who worry about calibration have high-impedance (10-megohm) FET voltmeters, the loading effects of which are negligible here.

PARTS LIST FOR PRECISION VOM CALIBRATOR

B1—ten AA cells in series to yield 15 volts

C1—100 μ F, 25 electrolytic capacitor

C2—.1 μ F ceramic disc capacitor

C3—.01 μ F polystyrene or mylar capacitor

IC1—LM185 1.235-volt reference IC (National Semiconductor)

IC2—3140A FET-input op amp (RCA) All Resistors $\frac{1}{2}$ w, 1% precision unless noted otherwise

R1—12,000-ohm, $\frac{1}{2}$ -watt 10% resistor

R2—1,180-ohm, $\frac{1}{2}$ -watt resistor

R3—3,480-ohm, $\frac{1}{2}$ -watt resistor

R4—1,000-ohm, $\frac{1}{2}$ -watt resistor

R5—499-ohm, $\frac{1}{2}$ -watt resistor

R6—162,000-ohm, $\frac{1}{2}$ -watt resistor

R7—115,000-ohm, $\frac{1}{2}$ -watt resistor

R8—2,150-ohm, $\frac{1}{2}$ -watt resistor

R9—4,990-ohm, $\frac{1}{2}$ -watt resistor

S1—SPST normally open pushbutton switch

