Build a

Diode Temperature Probe

Low-cost sensor gives temperature reading on a DMM



 \blacksquare (DMM), it can be made to give temperature readings for a small expenditure in parts and effort. When a small forward bias is applied to a conventional silicon diode, the voltage drop across the diode junction changes at a rate of about 1.25-mV/°F (2.24-mV/°C). Thus, a low-cost and readily available diode such as the 1N914 can be used as a temperature probe.

F YOU own a digital multimeter

The bridge circuit shown in Fig.1 works in conjunction with the sensor diode and a DMM on the 200-mV (low temperature) or 2-volt (high-temperature dc voltage ranges. The displayed digits are the temperature. Note that in Fig. 1, two values are shown for R2, R4, R6, and R7. The values in parenthesis are for Celsius operation, while the others are for Fahrenheit. Capacitor C1 is used to bypass stray signals that may be picked up on the leads.

Construction. The circuit can be assembled on a small printed-circuit or perforated board. The small circles at CI indicate the need for a pc pad, or WireWrap pin to make the connections to the remote diode.

To make the temperature probe safe for liquid immersion, the arrangement shown in Fig. 2 is used. Preform a short length of vinyl tubing, fill it with epoxy, and "thread" it up the diode leads to make contact with the diode body. Allow the epoxy to thoroughly cure. If desired, a length of heat-shrink tubing may be used. In either case, leave a short length of diode lead exposed for soldering to the flexible cable.

Slide a short length of heat-shrink tubing over the covered diode leads, solder each diode lead to the flexible cable, and then fit the tubing over the

Fig. 1. Diode is one leg of a Wheatstone bridge connected to DMM.

PARTS LIST

- C1—0.01- μ F disc capacitor D1—1N914 silicon diode
- $R1-33 k\Omega$, ¹/₂-W resistor
- R1-33 K12, 1/2-W resistor
- R2—82 k Ω (F) or 12 k Ω (C) ¹/₂-W resistor
- R3—1-k Ω pc-mount potentiometer
- R4—56 k Ω (F) or 68 k Ω (C) ¹/₂-W resistor
- R5— 10 k Ω pc-mount potentiometer
- R6—49 k Ω (F) or 120 k Ω (C) ¹/₂-W resistor Misc.—1.35-volt battery and holder, vinyl
- or heat-shrink tubing, flexible two-con-
- ductor cable, epoxy, solder, etc.



Fig. 2. To make probe immersible, vinyl tubing is added around leads.

solder joint. Shrink the tubing to make a tight fit.

Calibration. The resistance values for R2-R4 and R6-R7 are not critical, but their *ratios* are. Perform the following calibration tests before changing any resistance value.

Potentiometer R3 balances the bridge to indicate 32° F (0°C) at this temperature. Potentiometer R5 is used to reduce the 1.25 (2.24) mV/degree to exactly 1 mV/degree and is also used to set the upper range point.

With R3 and R5 at their center of rotation, immerse the diode probe in a container of finely shaved or crushed ice. Adjust R3 to produce a DMM indication of 32 (°F) or 0 (°C). Place the DMM in the 2-volt dc range, immerse the probe in a container of boiling water, and adjust R5 for a DMM indication of 212 (°F) or 100 (°C).

If you find that R3 is at one end of its rotation, add a parallel resistor in the megohm range across either R2 or R4, depending on the location of the wiper of R3. If R5 is at one end of its rotation, add a parallel resistor (also in the megohm range) across R6 or R7. If desired, a 10-turn trimmer potentiometer can be used for each of the fixed resistors and preset for the correct ratios.

Since the DMM will also indicate negative voltages, it will similarly indicate temperatures below those at which it is calibrated. Also, the diode can operate at temperatures above 212°F, which is about the limit for the plastic insulation used for the diode leads, so a plastic with a higher temperature rating can be used to liquid-proof the sensor. Or, without such protection, the sensor can be used for dry, or contact, temperature measurements.