

# Low-priced logic probe indicates levels with tones

by T. Kelly Butler

Applied Research Laboratories, University of Texas, Austin, Texas

Changes in sound tones are detected more readily than changes in light levels. Taking advantage of this fact, a penlite-size sound probe for troubleshooting digital circuits has been designed to provide an alternative to the conventional LED-type probe. The probe also checks continuity and is handy for testing cables and connectors. It is powered by two AA batteries mounted in the hand-held case, requires no on/off switch, and can be assembled easily from ordinary components.

The circuit emits these indications of logic levels:

- A low-pitched "boop" for a low TTL-logic level (0.8 volt or less).
- A high-pitched "beep" for a high TTL-logic level (3.0 v or more).
- No tone for an open or high-impedance connection.

It works like this: Transistors  $Q_4$  and  $Q_5$  (Fig. 1) form a relaxation oscillator whose frequency is roughly proportional to the charging current  $I$ . If logic LO is applied to the probe,  $Q_1$  conducts and charges  $C$  through the 220-kilohm resistor. The resulting current  $I_L$  causes  $Q_4$ - $Q_5$  to oscillate at a low frequency, producing the


"boop" sound. Logic HI will turn on  $Q_2$  and  $Q_3$ , causing  $I_H$  to flow through the 15-k $\Omega$  resistor. Since  $I_H$  is larger than  $I_L$ ,  $Q_4$ - $Q_5$  oscillates faster, producing the "beep" sound. A dead-band effect occurs if the probe tip is left open or if the applied voltage falls between the maximum value of  $V_{LO}$  and the minimum value of  $V_{HI}$  (i.e., between 0.8 v and 3.0 v for the circuit shown); all transistors remain off, and battery drain is almost zero.

The charging resistors can be adjusted to vary the pitch of the tones. The logic probe in Fig. 1 has  $f_{LO} = 60$  Hz and  $f_{HI} = 2,000$  Hz.


To modify the probe for logic families other than TTL, the voltage of battery  $B_1$  must be changed. This voltage should be  $[V_{LO(max)} + V_{HI(min)}]/2$ , but, of course, batteries come in standard sizes, so values of  $V_{HI(min)}$  and  $V_{LO(max)}$  are adjusted by use of diodes as shown in Fig. 2. For example, if  $B_1$  were a 2-v battery (instead of 1.5-v),  $V_{LO(max)}$  could be lowered back to 0.8 v by connecting one diode in series with the base of  $Q_1$ . (A diode would have to be removed from the base circuit of  $Q_2$  to leave  $V_{HI(min)}$  unchanged.)

The logic probe in Fig. 1 uses silicon transistor types 2N4401 (npn) and 2N4403 (pnp), but any transistors with a high gain and low leakage will serve.

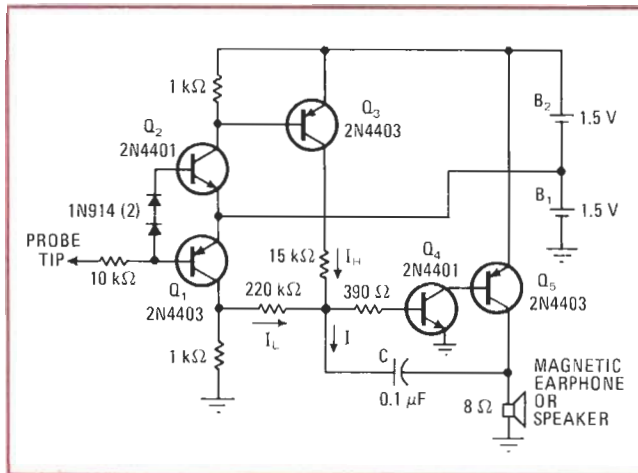Although a miniature speaker may be used for the output device, a small magnetic earphone works nicely and has enough volume to be heard across a room. □



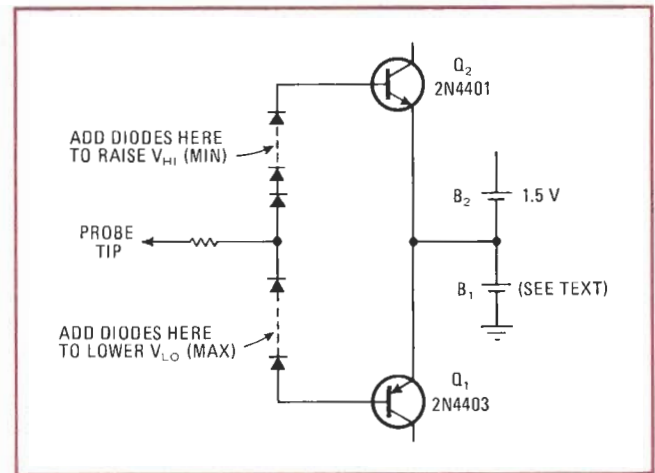**1. Sounds logical.** Handheld probe "boops" when tip touches a LO pin at logic LO, and "beeps" when tip touches a HI pin. Tones are generated by  $Q_4$ - $Q_5$  relaxation oscillator, with  $C$  charged through 220 k $\Omega$  if LO voltage is applied, or through 15 k $\Omega$  if HI voltage is applied. Voltages between  $V_{LO(max)}$  and  $V_{HI(min)}$  produce no output.



**2. Setting the gap.** Circuit of Fig. 1 can be modified by addition of diodes to change the maximum voltage for "boop" tone,  $V_{LO(max)}$ , and/or the minimum voltage for "beep" tone,  $V_{HI(min)}$ . Any silicon diodes can be used; the voltage drop is about 0.5 volt per diode at the low diode currents.

Engineer's Notebook is a regular feature in Electronics. We invite readers to submit original design shortcuts, calculation aids, measurement and test techniques, and other ideas for saving engineering time or cost. We'll pay \$50 for each item published.

and changes in beta are reflected in the value of  $V_{out}$  ( $\beta$  is inversely proportional to  $V_{out} - V_{BE}$ ). If the value of  $R_B$  is chosen to give a  $V_{out}$  of approximately 10 v, changes in  $V_{BE}$  can be neglected. Thus

$$\beta = (R_B/R_C)(V_{CC} - V_{set})/V_{out}$$

The useful range of operation of the circuit of Fig. 1 is limited by the input common-mode range of the op amp. For a op amp operating with a  $\pm 15$ -v power supply, the differential gain becomes smaller when the common-mode voltage exceeds approximately 8 v. With a 40J op amp, common-mode voltage as high as 12 v can be tolerated. In the circuit of Fig. 1, the maximum permissible value of  $V_{CE}$  can be extended to 27 v by referencing the emitter to the negative side of the amplifier power supply rather than the common ground. In this case,  $V_{CE} = V_{set} + 15$  v. This modification also allows larger values of  $R_B$  for a given base current and increases the system sensitivity to changes in beta. It cannot be used in power transistors when  $V_{CE}$

may be several hundred volts and a base drive of several hundred milliamperes may be required—far in excess of the current-handling capabilities of most op amps.

The circuit in Fig. 2 shows how the original circuit may be modified to maintain constant power in such cases. Instead of the direct connection of  $V_{CE}$  to the noninverting input of the operational amplifier, a fraction,  $\gamma V_{CE}$ , of this potential is tapped from a voltage divider chain to ground. The impedance level of this chain is kept high to minimize the current drain from the current flowing through  $R_C$ . A current amplifier is used in the base-drive circuit. In Fig. 2, an emitter follower is shown; the base current is given by the relationship  $I_B = (V_{out} - V_{BE1} - V_{BE2}) \times A_I/R_B$ , where  $A_I$  is the current gain of the emitter follower and  $V_{BE1}$  and  $V_{BE2}$  are the base-emitter-junction voltages of the transistor under test and the current amplifier, respectively. Thus changes in beta are reflected in changes of  $V_{out}$ , as in the original circuit.  $\square$