## Counter indicates when its probe is compensated

by Dale Carlton
Tektronix Inc., Beaverton, Ore.

Using a scope probe with a counter or other measuring instrument has a number of well-known benefits—namely, it ensures minimal source loading, physical ease of circuit connection, and minimum distortion of high-frequency signal components. Still, matching the probe to the counter's input impedance to secure wideband response can be troublesome, especially if the elements needed to perform the standard compensation procedure (a scope and a source of square waves) are not available and the input impedance of the scope and counter are not identical. Fortunately, the counter's own input-trigger circuit may be employed as a peak detector to indicate that proper probe compensation has been achieved.

The equivalent input circuit of the typical  $5 \times$  and  $10 \times$  (attenuating) probe appears as in (a), where  $C_1$  is the ac coupling capacitor and  $C_2$  represents the probe's compensating capacitance, cable capacitance, and the input capacitance of the measuring instrument.  $R_1$  is the dc coupling resistance.  $R_2$  is the instrument's input resistance. For flat response, the product of  $R_1$  and  $C_1$ 

**Match.** Universal counter's display or trigger LED is used to indicate that probe/circuit's elements  $R_1C_1C_2$  (a) are matched to input impedance ( $R_2$ ) of measuring device. Procedure used is to first position triggering region on roll-off of input-signal curve (b) with  $C_2$  and counter's trigger-level control. Probe will be compensated over a wide band after  $C_2$  is peaked (c) to detect high-frequency components of square wave.

should be equal to the product of  $R_2$  and  $C_2$ .

Compensation is achieved by applying to the probe/counter a 1-kilohertz square-wave signal having a rise time of less than 100 microseconds. The amplitude of the square wave should be as large as the counter's dynamic range will allow. The counter should be set to trigger on the low-frequency components of the square wave so that a reference level is established. Then the probe's compensating capacitor is adjusted so that the counter will trigger on the highest-frequency components of the signal.

Specifically, the counter should be set to the 1× position. The counter's function control is then set to the frequency, period, or event position, so that the counter's display or input-trigger LED will indicate triggering when the square wave is applied.

To establish the reference level, the probe is adjusted so that triggering occurs in the waveform's so-called roll-off region. This is done by setting  $C_2$  and the trigger level in turn so that triggering occurs at the peak of the acquired signal and at the minimum level required to ensure consistent operation. The point at which this occurs for a given trigger level is reached when an increase or decrease in  $C_2$  does not stop triggering. If the acquired signal could be observed, it would appear as in the illustration in (b).

For compensation at the high frequencies, the response of the probe must be flattened (c). This is achieved by setting the trigger level to a position where triggering just stops or is erratic.  $C_2$  is then adjusted to

