







▲  
On the inside. Showing construction of the project and how I mounted it inside the Unibox case. Note that one of the internal pillars is cut down to provide clearance for the transformer. Inset. The completed project.

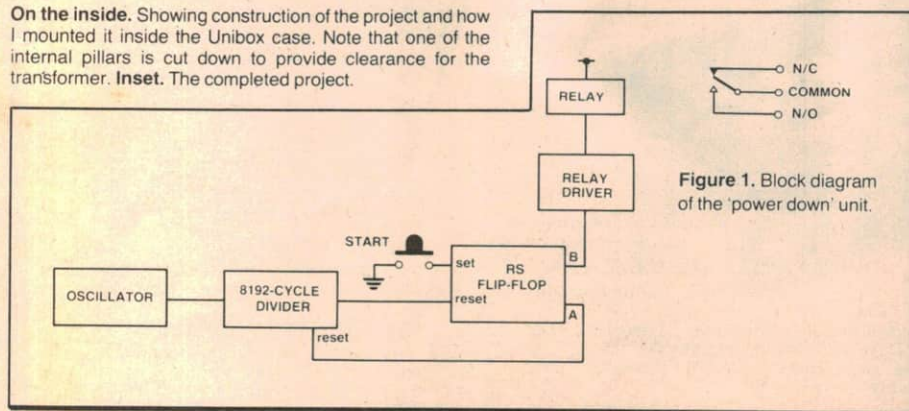


Figure 1. Block diagram of the 'power down' unit.

## HOW IT WORKS — ETI-265

The overall design of the project is discussed in the text, so this shall largely be a blow-by-blow description of how it works. Let us start at the 'rear end' first.

Two gates from the 4093, IC2a and b, form the reset-set (RS) flip-flop. This is in the SET state when pin 3 of IC2 is high and pin 4 is low. It is in the RESET state when pin 4 is high and pin 3 low.

When the flip-flop is SET, Q1 is turned on as the high on pin 3 of IC2 biases on its base via R4 and LED1, which lights, indicating the unit is 'active'.

A momentary low on pin 1 of IC2 will SET the flip-flop, while a momentary low on pin 6 will RESET it.

On power-up, C4 will look like a short circuit and keep pin 6 of IC2 low long enough to RESET the flip-flop. Thus, pin 4 of IC2 will be high and reset IC3, a 4020B 14-stage binary counter with a division ratio of 8192:1.

Pin 3 of IC3 (the stage 14 output) will be low after the IC is reset and IC2 will invert this, pin 10 driving pin 6 high, allowing the flip-flop to be set when PB1 is pushed momentarily.

As soon as PB1 is pushed, the counter begins to count cycles of the Schmitt gate oscillator comprising IC2d, R1, RV1 and C3. The frequency of the oscillator is determined by RV1, R1 and C3 and the threshold voltages of the inputs of IC2d. (See 'Why some CMOS circuits don't work as you expect', Lab Notes, in this issue.)

After 8192 cycles of the oscillator, pin 3 of IC3 goes high, thus resetting the flip-flop via IC2c. Pin 3 of IC2 will thus go low and the relay will drop out.

The oscillator works as follows: At power-up, pin 12 of IC2d will be low as C3 appears as a short circuit. Pin 13 will be high and thus pin 11 will be driven high. C3 will charge via R1 and RV1. When the voltage on C3 reaches the gate's upper threshold, pin 11 will go low and C3 begin to discharge via RV1 and R1. When the voltage on C3 falls to the gate's lower threshold, pin 11 will again go high and the cycle will be repeated.

The oscillator frequency is related to the timing interval (or period) as follows:

$$f_o = \frac{8192}{T}$$

where  $f_o$  is the oscillator frequency in Hertz, and T is the period in seconds. Expressing this in terms of the period:

$$T = \frac{8192}{f_o}$$

Table 1 allows you to set up the project for a particular timing interval. The range of adjustment provided should compensate for most of the variation in threshold voltages of the different manufacturers' 4093s. The time interval shown in the table refers to the prototype project. If you add the rotary switch to give four ranges, the longest interval will be as per the table, the next will be half that, then quarter that, etc.

The power supply is quite straightforward. Transformer T1 drops the mains voltage to 12.6 V RMS. This is rectified by a bridge diode comprising D1 to D4. Capacitor C1 is the rectifier reservoir. About 18 volts is developed across C1 and this is regulated to 12 V by a 7812 three-terminal regulator, IC1. Capacitor C2 ensures regulator stability.

Diode D5, across the relay, shorts the reverse-emf generated by the relay coil when Q1 switches off, preventing the high voltage generated from destroying Q1.



## Construction

I built one prototype and mounted it in a plastic case, which you see in the photographs here, and another unit which I mounted inside an appliance (ask no questions and...)

I used an all-plastic Unibox (P/N144) measuring 135 mm long by 100 mm wide by 50 mm deep. (Magraths in Melbourne are a major supplier of these.) It has ample room inside. You could use a UB-1 zippy box (50 x 90 x 150 mm), but an all-plastic case is recommended for safety's sake. Jaycar stock a range of smart, all-plastic (ABS) cases in various colours. The HB6150, 1, 2, 3 series (orange, grey, blue, black) would suit.

First thing to do is determine the mounting positions of the printed circuit board and transformer. Lay the unassembled pc board and the transformer in the base of whatever box you're using and mark the positions of the mounting holes.

Then mark out suitable positions for the mains cable entry, the pushbutton, the LED and the mains socket. For the mains cable entry, I used a Heyco clamp-type grommet to suit the mains cable I used (grommet #1210, SR-6P-4). There are plenty of similar types available. If you don't use a clamp-type grommet, then use an ordinary rubber grommet and a nylon cable clamp.

The mains socket requires holes to be drilled in the box to allow cables to the active, neutral and earth pins to pass through to the socket terminals. I first loosened the grub screws on the socket terminals, then positioned the socket where I wanted it and drilled pilot holes in the case through the terminals.

After drilling all the holes, mount the transformer, output socket, LED and pushbutton, but not the pc board — you've got to assemble that yet! To mount the transformer, I used insulating washers from a TO-3 power transistor mounting kit. An alternative is to use nylon bolts. The latter were used to mount the pc board.

Note that, if you wish, the section of the board on which the relay mounts can be severed from the rest of the board, allowing the relay to be mounted away from the main portion of the electronics.

Assembly of the board is pretty straightforward. Start with the smaller components. Solder all the resistors in place, then the five diodes, C2, C3 and C4. Watch the orientation of C3 and the diodes. Solder a link of tinned copper wire in the position shown, between C4 and R4. Now you can solder IC2 and IC3 in place.

These are CMOS ICs. Use an iron with an earthed tip and only handle the ICs with your thumb and forefinger gripping the ends of the package. Avoid touching the pins. When you have each in place, solder pins 7 and 14 of IC2 first and pins 8 and 16 of IC3 first, before going on to solder the other pins. If you wish, IC sockets may be used without affecting operation of the project.

Next solder Q1 in place. Its orientation can be ascertained from the pinout diagram and the component overlay.

Now solder the electrolytic, C1, in place, taking care to orientate it correctly, followed by IC1 (get it the right way round) and RV1. The relay can be soldered to the board last of all.

Wires are run from the pc board to the mains circuitry, the pushbutton and the LED. Only ordinary light hookup wire (10 x 0.12 mm) need be used to connect up the LED and the pushbutton. The 2851 transformer primary wires are generally coloured red and black. It has three secondary wires, two the same colour. These are wired to the rectifier diodes D1-D4, as shown in the overlay/wiring diagram.

Wire the transformer primary very carefully. The brown active wire from the mains input cable goes to a terminal connector, where it joins the red wire from the transformer. Take a length of brown mains wire and connect it between this terminal connector and the COMMON relay terminal pad on the pc board. Another length of brown mains wire is run from the normally open (N/O) relay contact pad on the pc board to the active terminal of the mains output socket.

The blue neutral wire runs from the mains input cable direct to the neutral terminal on the mains output socket, along with the black wire from the transformer.

The green and yellow striped earth wire from the mains input cable goes direct to the earth terminal on the mains output socket. This wire should be longer than the other two from the mains input cable for safety reasons. Should the mains cable be accidentally pulled out from the case, the earth wire will be the last to break.

All finished? Check everything thoroughly.

That's all there is to it. Next thing to do is test and calibrate it.

## Test and calibration

Set RV1 to the middle of its travel, then close the case so that you can't accidentally come in contact with the lethal mains voltage present.

Plug a bedside lamp into the output socket, plug the project into the mains and switch on. Nothing should happen. If all's well, press the pushbutton and the lamp should light. Now time how long it remains on (if it's 50 hours or more, you're going to need a lot of patience!).

If you have access to a frequency counter, then setting the timer is much easier. Just attach the frequency counter to pin 11 of IC2. The oscillator frequency is related to the timing period as follows:

$$\text{Frequency} = 8192 / T$$

where T is the desired period in seconds and the frequency is in Hertz.


For a timing period of ten minutes, the frequency should be 13.65 Hz. For really long times, you're better off measuring the period of the oscillator output.

All you need do is to adjust RV1 for the correct frequency.
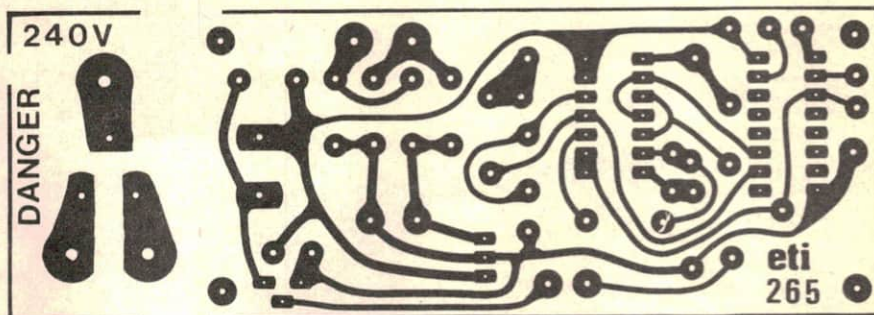
## Binary periods

As mentioned earlier, the simple addition of a switch can give you binary (half, quarter, eighth) segments of the basic period. Details are shown in Figure 2.

Cut the track that runs beneath the body of IC3, then wire a single-pole, four-position switch as shown. Position 4 gives you the full period. Position 3 gives the half period, position 2 one-quarter and position 1 gives one-eighth the period. ●



## PARTS LIST — ETI-265

<b>Resistors</b>	all ¼ W, 5% unless noted
R1	47k
R2	100k
R3	470k
R4	2k2
<b>Capacitors</b>	
C1	470u/25 V single-ended electro.
C2, C4	100n greencap
C3	1u/16 V tantalum
<b>Semiconductors</b>	
D1-D4	1N4001, 1N4002 or similar
D5	1N914, 1N4148
IC1	7812
IC2	4093B
IC3	4020B

LED1	TIL220R red LED
Q1	BC548
<b>Miscellaneous</b>	
PB1	momentary action pushbutton, large (e.g. D.S.E. no. S-1199 or similar)
RL1	pc mount relay, 12 V coil SPDT/5 A contacts (e.g. D.S.E. S-7125, or similar)
T1	2851 transformer, 12.6 V CT @ 150 mA
ETI-265 pc board; case to suit (e.g. Unibox P/N 144, 100 x 135 x 50 mm, or similar); LED mount; 240 V wall socket; mains cable plug, cable and clamp; wire, etc.	

**Price estimate \$32-\$37**



