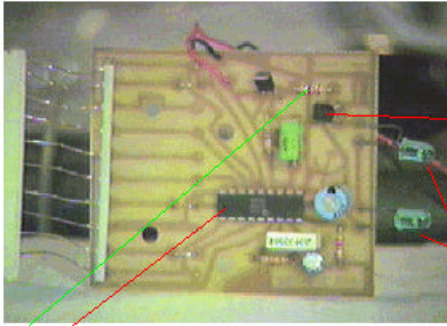


## JERROLD REMOTES.



If transistor is bad DO NOT replace with a 2N3904. Use a 2N4401 or a 2N2222. Get more range with these.

LED's go bad. Check with ohm meter.

IC goes bad because battery touches clip in the wrong polarity. Replace with SL490, UAA4000, ECG1755.

Replace drive resistor with a 100 ohm to increase drive.