

SOUND ENGINEERING — No. 25

This department is conducted for the benefit of RADIO-CRAFT subscribers. All design, engineering, or theoretical questions of general interest on PA installation, sound equipment, and audio amplifier design will be answered in this section. No circuit diagrams can be supplied by mail, all answers being printed in order of their receipt.

(Note: when questions refer to circuit diagrams published in past issues of technical literature, the original, or a copy of the circuit should be supplied in order to facilitate reply.)

PRE-AMPLIFIER

The Question

I am enclosing stamped self-addressed envelope and circuit diagram (Fig. 1) of a pre-amplifier I wish to build. It is actually an old single stage unit, rebuilt, with separate power supply. I wish to

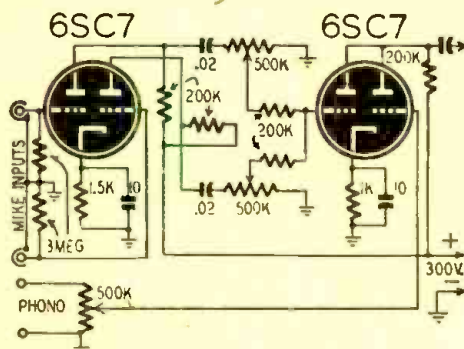


Fig. 1—Original circuit of a pre-amplifier.

use the old power supply with the new unit.

The new unit is to feed into the phono jack of my present amplifier which uses a 1612 in the first stage. Will you kindly have your Sound Department check part values on enclosed diagram and finish output circuit, to feed former phono input?

RALPH LEBRUN
Geneva, New York

The Answer

I am sorry that questions to this department cannot be answered by mail. They can only be answered through publication in this section. A corrected cir-

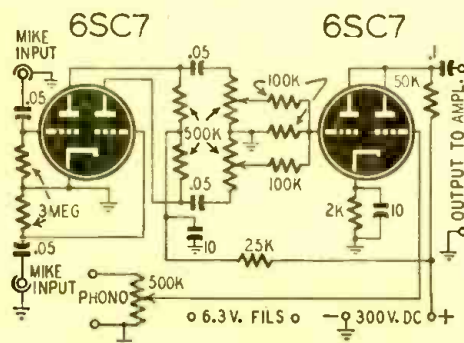


Fig. 2—Circuit of Fig. 1 with improvements.

cuit diagram of the type of pre-amplifier you are interested in is indicated in Fig. 2. You will note that six major changes have been incorporated, which will insure satisfactory operation. The cathode resistor and by-pass condenser in the first stage have been eliminated to avoid excessive hum and noise pick-up. The mixer circuit has been altered to keep inter-action between controls at a minimum. In the circuit indicated, approximately 2-db change will be noted in the level of one microphone circuit when the remaining "mike" control is varied from minimum to maximum. Your original circuit produced a change of approximately 6 db. The bias of the second 6SC7 has been increased to enable this stage to handle 1 volt input adequately without introducing excessive distortion. A decoupling resistor has been inserted between the two stages to avoid possibility of motor-boating. The plate load of the first stage has been increased from 200,000 ohms to 500,000 ohms to provide increased gain and to limit plate current as the stage is operating under a "no bias" condition. The coupling condensers between stages have been increased from .02 to .05 μ f to provide a better low frequency response.

MIDGET AMPLIFIER

The Question

I intend to build the Midget Amplifier as shown on the enclosed diagram (Fig. 3). But, I am not sure about the voltage ratings of the condensers and wattage ratings of the resistors. Also, the two 20 μ f units, 10 μ f unit, and the 40 μ f unit. Must they be electrolytic condensers? I am under the impression that the two 20 μ f units are bypass condensers.

Please send me a complete parts list giving the wattage of resistors and voltage rating of condensers. Also, I would like to know if this amplifier would handle an 8-inch PM speaker as well as a 3- or 4-inch. Inform me whether the high frequency cut is an ordinary 0.5 megohm tone control, or whether it is a special control.

Thanking you kindly.

DEAN HORN
Columbus, Indiana

The Answer

The voltage rating of the condensers and the wattage rating of the resistors follow:

Condensers	Resistors
40 μ f—200 v	500,000 ohms— $\frac{1}{2}$ watt
20 — 25 v	250,000 — $\frac{1}{2}$ watt
20 — 25 v	25,000 — 1 watt
10 — 150 v	3,000 — 2 watt
0.1 — 200 v	1,000 — 1 watt
0.1 — 200 v	200 — 2 watt
.003—200 v	50 — $\frac{1}{2}$ watt

The power output of the amplifier will be approximately 2 watts. This should be adequate to operate an 8-inch speak-

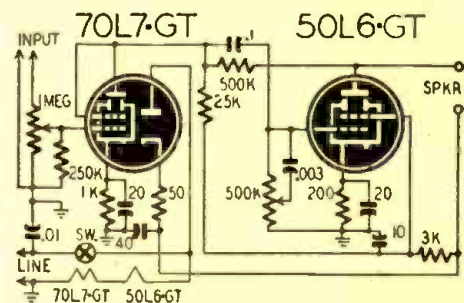


Fig. 3—The 2-tube Midget Amplifier circuit.

er. However, a 3- or 4-inch speaker, if operated at low levels, will probably provide better frequency response. The high-frequency control may employ an ordinary $\frac{1}{2}$ -meg potentiometer. One with an audio grid taper will probably provide smoother high-frequency cut-off action.

TRANSFORMER DATA

The Question

Will you kindly tell me what should be the a.c. RMS voltage of the two plate transformer windings for the Direct-Coupled Recording Playback Amplifier described in the November 1940 issue of RADIO-CRAFT? Also, I would like to know the current rating for the winding supplying the plates of the 5U4-G rectifier tube.

WARREN E. HAIGHT
Wilmington, Delaware

The Answer

The loaded a.c. RMS voltages of the transformer windings together with their indicated current carrying capacities are listed below:

1. High Voltage Secondary—380 volts each side of center tap at 250 mils.
2. Bias Secondary—187 volts each side of center tap at 250 mils. The voltage and current ratings of the remaining windings also follow:

- 5U4G filament—5 volts at 3 amp.
- 5V4G filament—rated at 5 volts at 2 amp.

(Continued on page 63)

SOUND ENGINEERING (Continued from page 31)

6.3-volt heater winding for the 6L6G output tubes—2 amps.

The remaining 6.3-volt winding is rated at 3 amps.

If you have any difficulty in locating a transformer with these secondary voltages, you might be able to construct one yourself or possibly have it built in accordance with the following manufacturing specifications:

Transformer Core—1½ x 2¼-inch Transformer Grade.

Primary—218 turns of No. 19 wire. Electrostatic Shield.

High-Voltage Secondary—1520 turns center-tapped No. 30 wire.

Bias Secondary—750 turns center-tapped No. 30 wire.

5-volt 3-amp. winding—10 turns center-tapped No. 16 wire.

6.3-volt 3-amp. winding — 13 turns center-tapped No. 16 wire.

5-volt 2-amp. winding — 10 turns center-tapped No. 18 wire.

6.3-volt 2-amp. winding — 13 turns center-tapped No. 18 wire.

The high voltage winding should be insulated from other windings and core to withstand 1750 volts RMS 60 cycles. The bias winding should withstand 1500 volts. The 5-volt 3-amp winding should withstand 2,000 volts.

HUM PICKUP, LINE IMPEDANCE

The Question

I am operating a sound moving picture system in an auditorium and have considerable trouble with hum at the loud-speaker and boominess. The room is not treated acoustically but some portable machines that have been operated there give satisfactory results.

The output of the amplifier (push-pull 2A3's) is coupled to the line through a "2A3 P-P to 500-ohm" transformer. The line is made up of a pair of No. 14 flexible wires, twisted, with heavy insulation, and is about 250 feet long. It terminates in the primary of a 500-ohm-to-voice-coil transformer. The line is unshielded and the speaker, when plugged in at the amplifier, shows no sign of hum. The amplifier is well grounded. The monitor speaker, a pm dynamic, shows lots of hum also when the main speaker is coupled to the other end of the line.

I am at present experimenting with the input end, photocell lines, etc., to see how much hum is originating there.

In connection with the output end, I would like to know how the impedance of an audio frequency line may be computed. Have tried feeding the line with and terminating it in 250-ohm transformers but did not get as good results as with 500-ohm terminations.

GEORGE F. SWARTZ
San Francisco, Calif.

The Answer

The excessive boominess you mention is undoubtedly caused by an extended
(Continued on page 64)

RADIO-CRAFT for NOVEMBER, 1946

Mr. Radioman—

What are
your
Qualifications?

EMPLOYERS ARE CHOOSEY!



PREPARE FOR HIGH-LEVEL EMPLOYMENT WITH THESE CLEVELAND INSTITUTE HOME STUDY COURSES . . .

1. Mathematics for Radio and Communication Engineering.
2. Advanced Course in Radio Communication Engineering.
A college-level Radio Engineering Course.
3. Master Course in Radio Communication.
Covers fundamentals of Radio and includes complete preparation for FCC Commercial License Examinations.
4. Specialized Television Engineering.
Including post-war Television Techniques.

All Courses Include

The Remarkable Workbooks of Instructional Aids, prepared by the instructing staff of Cleveland Institute.

Choose the course best suited to your needs—Start with the section you are qualified to enter—Use the economical CIRE "Pay-As-You-Go Plan."

Write for descriptive folder • No obligation

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Successors to

NILSON RADIO SCHOOL
Founded 1939

SMITH PRACTICAL RADIO INSTITUTE
Founded 1934

RC-11 TERMINAL TOWER, CLEVELAND 13, OHIO

Approved for Veteran Training Under "G.I. Bill of Rights"

(MAIL THIS COUPON)

Cleveland Institute of Radio Electronics, RC-11 Terminal Tower, Cleveland 13, Ohio.
Gentlemen: Please send information about your home study courses in Radio Electronics.

NAME
ADDRESS
CITY
ZONE STATE

I desire training in
I have had experience in broadcasting ☐ servicing ☐
operating ☐ mfr. ☐ CAA ☐ Army-Navy ☐
amateur ☐ other I am a
High School Grad. ☐ College ☐ Degree
☐ Check here for Veteran Enrollment Information.

PREPARED ASSORTMENTS

GUARANTEED FIRST QUALITY

100	1/3 Watt Resistors All Insulated	\$2.98
100	1/2 Watt Resistors All Insulated	3.98
100	1 Watt Resistors All Insulated	4.48
50	2 Watt Resistors All Insulated	3.98
50	200 Volt Paper Condensers	2.48
50	Mica Condensers	2.98
50	Dry Electrolytic Filter Condensers	6.75
10	25 ft. Rolls Hookup Wire—Assorted colors	1.98
10	Volume and Tone Controls—No Switches	1.98
100	R. Spaghetti and Vinylite98
10	Collis I.F., R.F. Ant. and Osc.	3.98
20	Wafer and Ceramic Band Switches	3.98
20	Auto Suppressors	2.98
50	Electrical Wiring Devices, Plugs, Tabs, Bases, Elements, Fuses, etc.	5.00

SEND FOR TRUTONE COMPLETE RADIO AND ELECTRICAL LIST

Terms: 25% deposit required with order. Balance C.O.D. Merchandise sent prepaid if full remittance accompanies order.

TRUTONE PRODUCTS CO.,

303 W. 42nd St. Dept. C New York 18, N. Y.

When writing advertisers, please mention that you saw it in RADIO-CRAFT.

MINE DETECTORS

YOU CAN NOW BECOME A PROSPECTOR—HERE IS ONE OF THE WAR'S TOP SECRETS:

ARMY MINE DETECTORS



NEW, in original cases; portable. Will detect METALLIC and NON-METALLIC objects. Very sensitive; using 955 tube in detecting head. Two-tube amplifier using two 1N5GT; headset; or microphone; also 150 micro meter. Power supply—3 45v, 1 6v or 2 3v batteries. Complete with instructions. See "How Mine Detectors Work" in July, 1946, Radio-Craft. Shipping weight 108 pounds. F.O.B. N.Y. Special, less batteries. **\$17.50**

SEND ORDER TO

HIGHBRIDGE RADIO-TELEVISION AND APPLIANCE CO.


340 Canal Street

New York 13, N. Y.

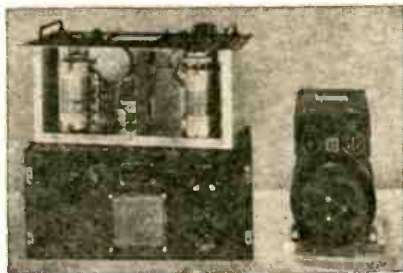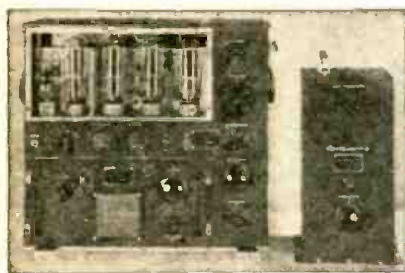


General Electric 150 Watt Transmitter—Brand New! Due to the drastic reduction given us on the cost of these units by the Government, we are now able to place these transmitters on sale for only \$67.60!!! These units certainly will not last at this price so get your order in immediately. This unit consists of Transmitter complete with tubes, seven plug-in tuning units which cover the entire frequency range, antenna tuning unit, and dynamotor. All cables and plugs along with Army Instruction Manual, and also instruction booklet on how to convert to 110V AC, are included with this stupendous buy. Don't forget the price exclusive of transportation charges is only \$67.50 while they last.

Here is a set adaptable for all amateur, experimental, marine, aircraft, police, and mobile applications. A 7-tube receiver featuring an RF stage, four double-tuned 455 KC iron-core IF transformers, 2 audio stages, and a beat frequency oscillator for CW reception. The transmitter employs a calibrated crystal oscillator, a buffer amplifier, and a pair of RK-75 tubes in the final amplifier stage. The transmitter plates are supplied by a 500V 160 MA dynamotor which operates from a 6 or 12 Volt automobile battery. The frequency range is 3760-5825 KC. Circuit diagrams are furnished. These units are priced at \$39.95, complete with set of 13 tubes and crystal. The dynamotor which must be used, if it is not desired to use 110V AC, is \$15.00 additional.

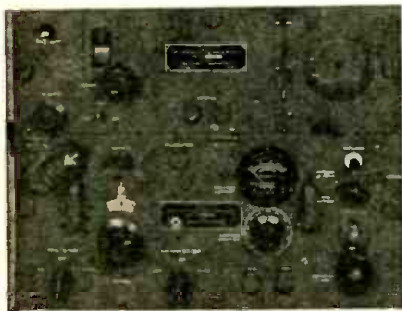

ANOTHER NEW ADDITION TO OUR ARMY SURPLUS LINE!

General Electric RT-1248 15 tube transmitter-receiver with TERRIFIC POWER (20 watts) on any 2 instantly selected, easily pre-adjusted frequencies from 435 to 500 Megacycles. Transmitter uses 5 tubes including a Western Electric 316 A as final. Receiver uses 10 tubes including 2-955's as first detector and oscillator, and 3-7H7's as IF's, with 4 slug-tuned 40 MC. IF transformers, plus a 7H7, 2-7E6's and 2-7F7's. In addition unit contains 6 relays designed to operate any sort of external equipment when actuated by a received signal from a similar set elsewhere. Originally designed for 12 volt operation, power supply is not included, as it is a cinch for any amateur to connect this unit for 110V AC, using any supply capable of 400V DC at 135 MA. The ideal unit for telephone use as in a taxicab, or for any kind of remote control applications, as with drone airplanes. Supplied with 15 tubes in original factory packing. Priced at only \$29.95. 10% less if ordered in quantities of two or more.

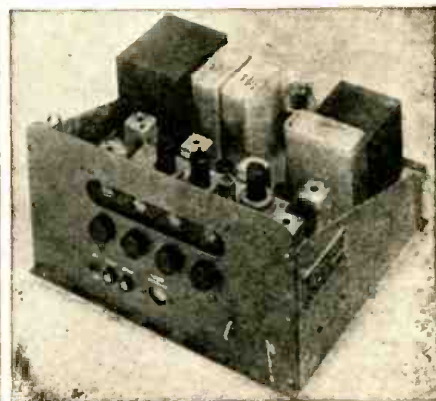

15 tube beautifully built Signal Corps Receiver is one of the most sensitive sets ever manufactured. It operates directly from 110V60 Cycles. Has two tuned RF stages, tuned converter and oscillator, five IF stages, using iron core IF's, a diode detector, tuning eye, and a two stage amplifier that will drive a speaker or phones. Easily converted from its 155 to 212 MC. band to any desired frequency. This 15 tube receiver cost the government about \$700, but is priced to sell now for only \$39.95.

famous for GREAT VALUES

OUTSTANDING OFFERINGS OF NEW KITS

H-101 Five Tube Superheterodyne Kit

Small Bakelite cabinet approximate size 9"x5"x6", complete parts except wire and solder for the construction of a standard superheterodyne receiver using 50L6, 35Z5, 12SA7, 12SQ7, and 12SK7. A simplified circuit diagram included in this kit enables any one with a slight knowledge of radio to construct a highly efficient receiver. **\$10.75**
Price not including tubes

H-105 Automatic Record Changer Kit

Consists of 1 Automatic Record changer, single post; 1 Portable leatherette cabinet for above; 1 Crystal pick up; 1 5" P.M. and output transformer; 1 complete kit of parts including tubes but excluding wire and solder, to construct a 3-tube amplifier using 1-50L6, 1-35Z5, and 1-12SQ7. Price complete **\$36.95**

All prices are F.O.B. New York City.

Write for our new catalogue showing new test equipment, tubes and a large variety of new replacement parts. We ship anywhere in the U.S.A.—promptly.

**RADIO DEALERS
SUPPLY COMPANY**

135 LIBERTY ST., NEW YORK 6, N.Y.

SOUND ENGINEERING

(Continued from page 63)

low-frequency response in the entire reproducing system. If other machines operate satisfactorily in the same auditorium, you undoubtedly can correct the trouble with your particular machine, by reducing the low frequency response of either the amplifier or the loud-speaker.

The hum may be picked either by the long unshielded line, particularly if it runs parallel to some power line carrying high currents, or, the coupling transformer at the speaker may be picking up hum from some hum-producing equipment on the stage of the auditorium. The fact that no hum is noticed in the monitor speaker when the auditorium speaker is connected directly at the amplifier, indicates that the hum is not being produced at the input end of the amplifier. An increase of hum in the PM speaker (at the amplifier) when the stage speaker is connected at the remote end of the line, clearly indicates that the line circuit is involved in the hum pickup. You can check if the speaker coupling transformer is picking up the hum by orienting the speaker while it is on the stage to see if the hum is reduced. If not, I suggest that you either shield the line or re-locate it so as to keep it away from high-current-carrying power lines.

The impedance of a terminated audio

Free Radionic Catalog



RADIONIC EQUIPMENT CO.
170 Nassau St., Dept. 1011, New York 7, N. Y.

Please send me a FREE copy of your 1947 Catalog. I understand it has thousands of items illustrated, described and priced and will be a great help to me in my search for "hard-to-find" radio equipment.

Name

Address

City State

frequency line may be checked with a power output level indicator. This device should be connected at the remote end of the line and adjusted so that maximum transfer of power takes place. The impedance setting of the indicator shows the proper terminal impedance.

The impedance of a non-terminated line is a function of its distributed capacity, inductance, d.c. resistance and insulation characteristics. For rough approximations, the impedance of a line should be at least twenty times its d.c. resistance. The distributed capacity of the line should have a capacitive reactance, at the highest frequency which the line is to transmit, of at least ten times the impedance of the source. The 250-foot line that you describe should be suitable for impedances ranging from 25 to 250 ohms, if 10,000 cycles is the upper frequency limit of transmission, or 25 to 500 ohms, if 5,000 cycles is the upper frequency limit.


The fact that you did not get as good results with 250-ohm terminations should not lead you to any false conclusions. The 250-ohm termination may have added some undesirable high frequency response in the system, and possibly provided less pleasing results. On the other hand, the 500-ohm transformers may have been much more efficient.

A Handy SALESKIT FOR RADIO SERVICEMEN

A real saleshelp exclusively for Radio Servicemen... the Jensen Phonograph Needle Saleskit is just the thing for demonstrating fine needles. What's more, Jensen needles augment your work, assure full, clear tone of the instruments you repair, make all records sound better.

Colorful, convenient, compact... the Saleskit slips easily into your pocket. Take it on service calls. It contains 3 Jensen Concert Needles retailing at \$1 each and 3 Jensen Genuine Sapphire Needles at \$2.50 each.

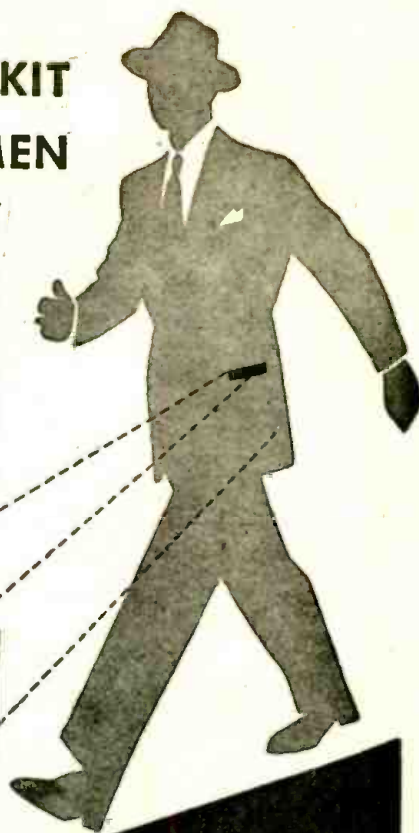Available NOW at your jobber. WRITE TO: DAY for complete details and our better than usual discount to servicemen.



JENSEN INDUSTRIES, INC.
327 SOUTH WOOD STREET
CHICAGO 12 ILLINOIS

HAM SPECIALS

From Ham Headquarters

Order	Net Price
— Panoramic Adapter (PCA2)	\$99.75 Ea.
— Cabinet: 24 1/2" Wide, 29 1/2" Deep, 7 1/2" High, Gray Crackle Finish. Ideal for Transmitter	90.00 Ea.
— Choke: 300 MA. Swing 9-19 Henry. Smooth 11-Henry	7.50 Pr.
— Choke: 2 1/2 M.H. R.F.C.19 Ea.
— Code Oscillator: Complete with Speaker, Telegraph Operator, MS-700	9.95 Ea.
— Coil Assembly: R.F. from Army Receiver BC-224M75 Ea.
— Condenser: 12x1x1 Mfd. 600-Volt Tobe Metal Case, Bathtub49 Ea.
— Condenser: .5 and .2 Mfd. 600-Volt Bathtub19 Ea.
— Condenser: 2 Mfd. 600-Volt Solar DC Aluminum Can, Oil Filled89 Ea.
— Condenser: 100 MMF. Midget Variable50 Ea.
— Condenser: 2 Mfd. 1000-Volt, Oil Filled, Round C.D.	1.50 Ea.
— Condenser: 10 Mfd. 1400-Volt, Oil Filled, Rectangular Type	0.75 Ea.
— Condenser: 10 Mfd. 1000-Volt, Oil Filled, Rectangular Type	0.75 Ea.
— Condenser: 3 Mfd. 2000-Volt, Oil Filled, Rectangular Type	3.25 Ea.
— Condenser: 50 MMF.50 Ea.
— Condenser: 8 Mfd. 600-Volt C.D. Aluminum Can, Oil Filled	2.75 Ea.
— Condenser: .001 Mfd. 5000-Volt Mica	2.40 Ea.
— Condenser: 6 Mfd. 600-Volt Oil Filled75 Ea.
— Condenser: 3x3 Mfd. 600-Volt Oil Filled, Rectangular Type99 Ea.
— Condenser: 4 Mfd. 600-Volt C.D. Aluminum Can, Oil Filled	1.50 Ea.
— Converter: Gonset 4-tube, supplied for either 10 or 6-Meter band	39.95 Ea.
— Crystals: IN27 Sylvania Diode50 Ea.
— Handy Talkie: Complete with Batteries, 3885 K.C. Frequency	49.50 Ea.
— Chassis: for Handy Talkie	10.00 Ea.
— Insulator: 3" Feed Through	1.00 Ea.
— Meter: Westinghouse 2" D.C. MA. 0-10-25-50-100-150-200-250-300-400-500	3.50 Ea.
— Meter: Burlington, 2" A.C. 0-150	2.25 Ea.
— Meter: 2" Round	3.50 Ea.
— Meter: Time Hour 110-Volt 60-Cycle	

Order	Net Price
— Mike: Breast Mike	1.95 Ea.
— Mike: T17B Carbon Hand Mike	2.50 Ea.
— Plug: PL-55 Army Type Plug (100-Lots - \$25 Ea.)35 Ea.
— Receiver: BC-42 Frequency 200 to 500 KC-1500 KC-20 MC as is	60.00 Ea.
— Relay: D.P.D.T. 6-Volt D.C. Coil	1.75 Ea.
— Leach 1/4" Silver Contact12 Ea.
— Shield: 6C4 Tube Shield49 Ea.
— Transformer: 5.3 M.C. I.F. Iron Core Interstage49 Ea.
— Transformer: 5.3 M.C. I.F. Iron Core Diode49 Ea.
— Transformer: G.E. Modulation-200 Watts for 811a to 813	6.00 Ea.
— Transformer: 2.88 M.C. I.F.29 Ea.
— Transformer: Filament, 6.3 Volt at 1 3/5 Amps Small Round	1.20 Ea.
— Transmitter: BC-223 Frequency 2000 to 3000 K.C.	25.00 Ea.
— Transmitter and Receiver: BC-1335 F.M. Ideal for 10 Meter Mobile Operation 6 or 12-Volt Input 2 1/4 Watts Output. Dimensions 12 1/2" Long, 13 3/4" Deep, 6 3/4" High. Ready to go with Telephone Headset and (3) Crystals for 10-Meter Band	53.00 Ea.
— Trimmer: Air, 15 Mmfd.25 Ea.
— Trimmer: 3-3015 Ea.
— Wire: Bronze Strand Wire (250 Ft. Rolls) Heavy	3.50 /Rl.

Mail Orders Promptly Filled
Amateurs to Serve You
(20% Must Accompany All C.O.D. Orders)
Write Dept. RC
W6SCQ—W6UXN—W6NAT—
W6VHZ—W6VIW
WRITE FOR FREE BULLETIN 29

Radio Products Sales Company

238 WEST 15TH STREET
LOS ANGELES 15, CALIFORNIA
Prospect 7471