

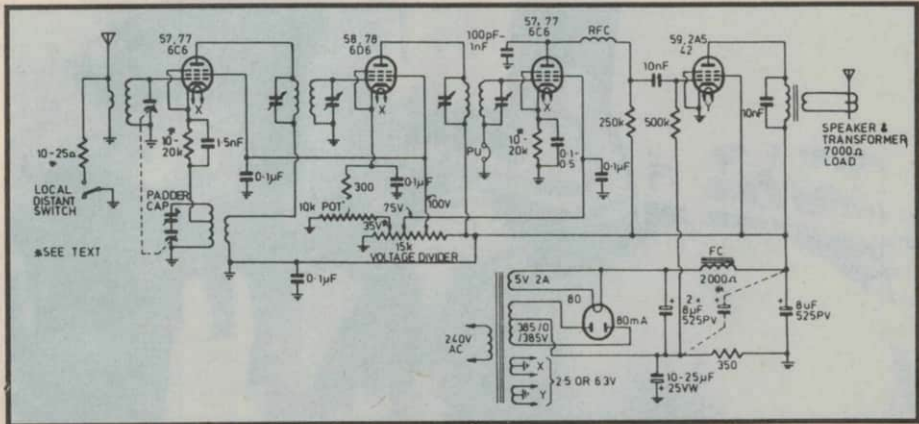


Fig.2: The circuit of a typical 1930's style autodyne superhet. At 'Radiovision' Lay Cranch and Howard Love pinpointed the need to avoid a high L/C ratio in the primary winding of the first IF transformer.