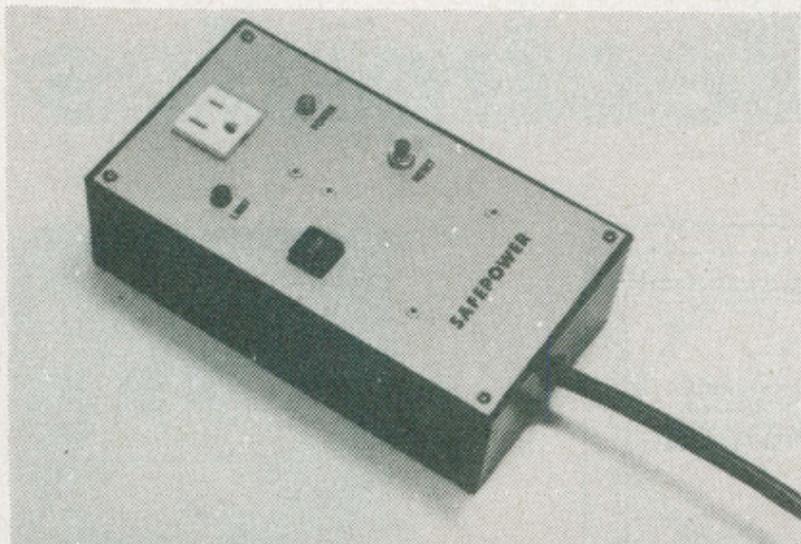


ADDITIONS TO POWERLINE TRANSIENT SUPPRESSOR

I'd like to congratulate Mr. Herb Friedman on a fine article, "Build this Powerline Transient Suppressor", in the September 1983 issue.



My two units (for two computers) are built inside a surplus Executone telephone desktop machine. I made two small additions: a) added MOV's from "hot" 115-volts AC to ground and from "neutral" to ground, to guard against transients. b) added a 4-amp fuse in series with the power-input line.

My units have been up and running for 4 months without incident, and have worked beautifully under field conditions. Total cost \$25.00. Keep up the good work.

WEI-I LI

Seattle, WA