

## Further notes on the self-setting time code clock

The following list of corrections and explanations will be helpful to readers of the time code clock articles in the August, September and October issues.

### Receiver Fig. 1.

The ten turn potentiometer can be a 200 or 500 ohm cermet type. Signal strength meter movement should be  $100\mu\text{A}$  .f.s.d. The capacitor across  $T_1$  primary should be 4,700pF not 47n.

### Decoder Fig. 4.

The capacitor across pins 10 and 11 of  $IC_7$ , and  $C_2$  should be non polarized types.  $IC_{12b}$  is half of a 7420 and not a 7470 also, pin 11 should be pin 13. Emitter resistor of  $Tr_5$  should be 4k7 and not  $47k\Omega$  as shown. The resistor on pin 2 of  $IC_{9d}$  is  $1k\Omega$ .

### Seconds counter Fig. 6.

The transistor on pin 5 of  $IC_{15}$ , and  $Tr_9$  are both BC182 types.  $IC_{17}$  is a 7400. Two gates are marked  $IC_{17a}$ , but pins 11, 12 and 13 should be 17d.  $C_4$  and the capacitor between pins 10 and 11 of  $IC_{15}$  are both tantalum. On the last-mentioned the positive end goes to pin 11. The pin numbering of the 747 displays is incorrect. Connections as shown in Fig. 11 should be followed.

### GMT to BST converter Fig. 9.

The i.c. numbering does not follow on from previous diagrams.  $IC_{23}$  is a 7400,  $IC_{24}$  a 7408,  $IC_{25}$  a 7432,  $IC_{26}$  a 7486, and  $IC_{27}$  is a 7240.

### Components list

IC marked SN7412N should be 74121.

Because the op-amps in the receiver are used with an unconventional supply it is possible that  $IC_3$  will not fall below 2V in the no signal condition. This produces a permanent a.g.c. voltage on the emitter of  $Tr_1$  and, hence, a reduction in gain. Several popular brands have been tried successfully in the design but Texas types are recommended throughout. Alternatively, the bias on  $Tr_1$  can be altered to increase the base voltage to around 3V.